

Circuit Ideas for IC Converters

by Walter Jung,¹ Jeff Riskin, and Lew Counts

The alert circuit designer is constantly on the lookout for new devices and new ways to use existing devices to realize needed functions more efficiently, at lower cost, or in ways not previously practical. Some recently introduced analog-digital-conversion integrated circuits fit in this class. In these pages, we offer a few circuit ideas, either for direct application, or to stimulate the Reader's thinking about related possibilities.

Included in the discussion are such devices* as the AD537 V/f converter, the AD1408, AD561, and AD7520 d/a converters, and the AD581 reference, as well as some older devices, in a variety of circuits suited for instrumentation, data-acquisition, and process-control applications. All these ideas are workable; a few of them are ready to hook up and use as they stand. The others are useful to illustrate concepts and are ripe for adaptation and further modification for specific applications.

OHMS-TO-FREQUENCY CONVERTER

Ohms-to-volts conversion is a familiar property of many digital voltmeters. However, ohms-to-frequency conversion provides added flexibility, since it facilitates remote measurements, averaged measurements, and optional a/d or f/V conversion at the destination.

In the circuit of Figure 1, the 1V reference voltage available at the AD537 is unloaded by buffer amplifier A1, which drives a reference current into the resistor under test in the feedback circuit of amplifier A2. The output voltage, proportional to resistance, develops a current at the input of the V/f converter, which generates a square wave at a frequency proportional to current, and hence to R_X . Since the reference for the measurement is the same as the reference for the conversion, ratiometric operation minimizes the effects of variation of the AD537's reference with temperature.

A counter can be used to read resistance directly. Typical laboratory counters have more than adequate resolution; models with adjustable gate time permit the decimal place

to be located as appropriate for the resistance range being measured. For example, a gate time of 1s will provide a readout in Hz, and the central measurement range will provide a direct readout, 1 Ω /Hz, or 1k Ω /kHz, up to the 100kHz full-scale range.

In this application, we are taking advantage of the typically wide dynamic range of V/f conversion to provide a readout of the most-frequently used resistance values on a single range. After calibration at 100kHz full-scale, with a 100k Ω standard, (R_2 is adjusted), and at 100Hz low-scale, with a 100 Ω standard, (R_4 is adjusted), the linearity error will typically be no more than $\pm 0.06\%$.

R_S and R_1 - R_2 should be stable precision types, and C_T an NPO ceramic, for best stability and repeatability. C_1 and C_2 serve as noise bypasses, but C_2 should have low leakage (polystyrene), since it is effectively in parallel with R_X .

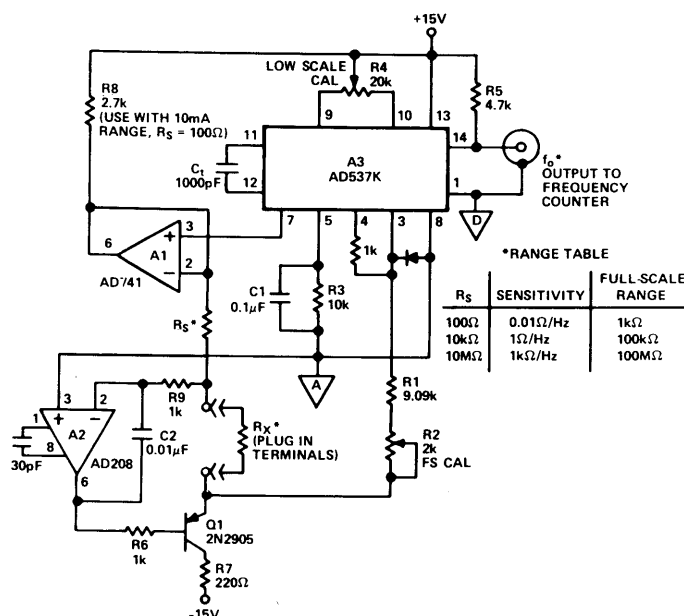


Figure 1. Ohms-to-Frequency Converter

As the chart notes, two additional ranges are suggested. The 0.01 Ω /Hz range has greater resolution and accuracy, for $R_X < 1k\Omega$, with a 1k Ω (= 100kHz) full-scale limit. Resistances

¹This article is adapted from portions of Walter Jung's *IC Converter Cookbook*, published by Howard W. Sams & Co., Indianapolis, Indiana (1978).

less than 0.1 ohm can be resolved on this scale. A pullup resistor, R8, should be used on this range, to minimize loading on A1, since $R_s (= 100\Omega)$ will draw 10mA.

The highest scale range (1kΩ/Hz) allows resistances in the tens of megohms to be read. A low-bias-current amplifier, such as the AD208 (or the AD517, or a FET-input amplifier) should be used to minimize errors due to the flow of bias current in R_s .

ALGEBRAIC MANIPULATIONS – QUOTIENTS OF DIGITAL INPUTS

Since d/a converters multiply analog inputs by digital numbers, devices that permit a wide range of analog variation can perform a variety of algebraic manipulations involving multiplication or division of analog and digital quantities.^{2,3} An example of the technique can be seen in Figure 2, a circuit that produces an analog quotient of two digital words, multiplied by a constant or variable reference.

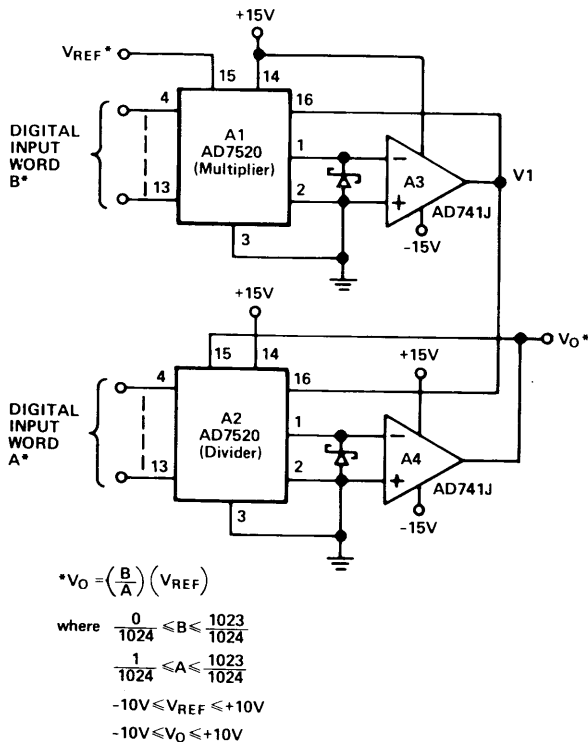


Figure 2. Algebraic manipulations – Analog quotient of two digital words.

In this circuit, two CMOS d/a converters are used. Converter A1 is connected in the forward path of op amp A3, producing an output, $V_1 = -B V_{REF}$, where B is the fractional binary value corresponding to the input code. Converter A2 is connected in the feedback path of op amp A4, producing an output, $V_O = -V_1/A$, where A is the fractional binary value associated with A2's input code. The overall relationship, therefore, is

$$V_O = \frac{B}{A} V_{REF} \quad (1)$$

V_{REF} may be of any value in the range $\pm 10V$, B may be any

²Analog-Digital Conversion Handbook, D.H. Sheingold, ed. [3rd edition (1986), published by Prentice Hall. Available from Analog Devices, Inc., Norwood MA, 02062 P.O. Box 796.]

³"Application Ideas for Multiplying DACs," Analog Dialogue 12-1, 1978.

number from 0 to 1023/1024, in steps of 1/1024, and A may be any such number from 1/1024 to 1023/1024. Naturally, the ratio is limited to values for which the output, V_O , is within bounds. V_{REF} may be positive or negative, ac or dc, and the output will be of the same polarity.

Like analog division circuits, this circuit has an output error-characteristic inversely proportional to the denominator, A.

8-BIT-PROGRAMMABLE SQUARE-WAVE OSCILLATOR

Programmability is an important new degree of freedom in analog circuit and system design. Virtually any circuit parameter can be made digitally controllable with little difficulty, using a/d and d/a conversion devices. It is important to be aware that "digitally controllable" doesn't necessarily mean that programmed circuits *must* interface with computers, processors, or even digital systems. In many cases, the digital input can be provided by manually operated switches, which need not be fancy, since they need only to switch binary levels. This circuit and those that follow illustrate a variety of practical examples of programmable circuits.

Figure 3 shows an 8-bit (255-frequency) programmable oscillator with square-wave output. The circuit comprises a current-output d/a converter (AD1408 family) and a current-to-frequency converter (AD537 family). The digital input produces a linearly related current from the DAC; this current, driven directly to the input of the VFC, produces a square-wave that has a frequency proportional to the numerical value of the digital input word.

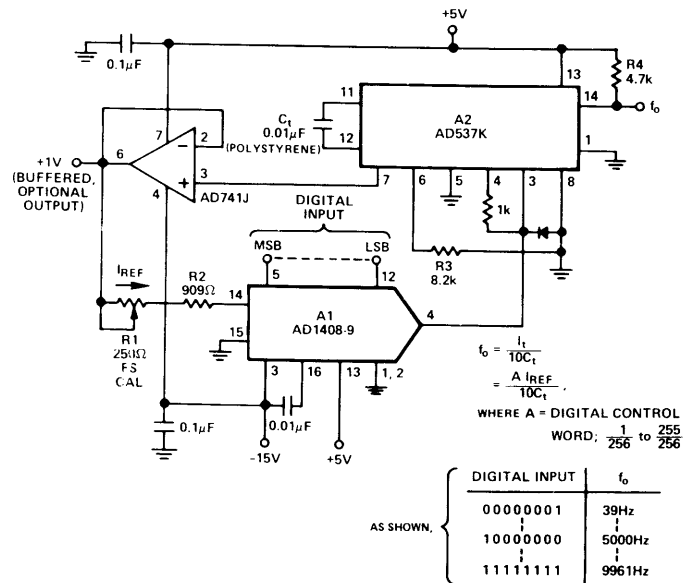


Figure 3. 8-bit programmable oscillator, square-wave output.

The AD1408-9 (9-bit-linearity) DAC is scaled for 1mA full-scale current output, to match the 1mA full-scale input of the AD537K. The 1mA reference current for the DAC is derived from the 1V reference output of the AD537, buffered by the AD741 follower-connected op amp. Since the basic reference source is common to both devices, errors due to its drift tend to cancel out.

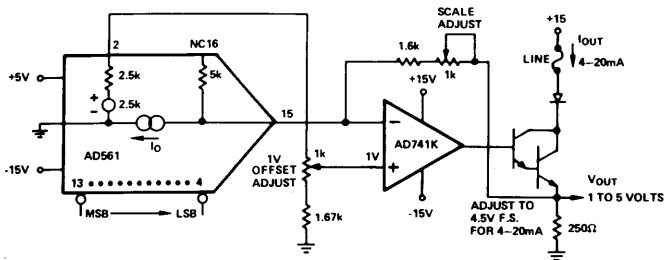


Figure 6. Process control current source.

Figure 6 shows a circuit to accomplish this with 10-bit resolution. An AD561 is used, in conjunction with an op amp and a Darlington transistor. With an all-0's digital input, the $1\text{k}\Omega$ offset pot is adjusted for 4mA of output current. With all 1's, the scale-adjust pot is set for 20mA (or 19.98mA) of output current.

Although the load is shown here as being referred to a +15V supply, it may—in general—be returned to any positive voltage within the breakdown rating of the transistor used. The diode protects against reverse-polarity faults, the fuse against shorts.