

Designing with HV Microcontrollers

Author: Keith Curtis
Microchip Technology Inc.

INTRODUCTION

When designing embedded microcontroller applications, one of the greatest challenges can be the creation of the power supply for the microcontroller. Particularly when the only supply voltage available is significantly higher than the microcontroller's maximum V_{DD} .

To help simplify embedded design, Microchip has introduced a new feature in a select group of new microcontroller offerings, a 5V shunt regulator. This on-chip regulator allows the microcontroller to operate from a wide variety of supply voltages. As an added bonus, the shunt regulator topology also allows the connection of other circuitry, external to the microcontroller, to be powered by the V_{DD} pin.

This application note discusses the design of power supply circuits using the new shunt regulator, and presents some Tips 'n Tricks for extending the regulator's capabilities.


THEORY OF OPERATION

A shunt regulator generates a specific supply voltage by creating a voltage drop across a pass resistor R_{SER} . The voltage at the V_{DD} pin of the microcontroller is monitored and compared to an internal voltage reference. The current through the resistor is then adjusted, based on the result of the comparison, to produce a voltage drop equal to the difference between the supply voltage V_{UNREG} and the V_{DD} of the microcontroller.

The advantage to a shunt regulator is that the supply voltage, V_{UNREG} , is only limited by the power dissipation and breakdown voltage of the external resistor, R_{SER} , not the power or breakdown characteristics of the regulator. The challenge in designing a shunt regulator circuit is choosing an appropriate value for the resistor such that the range of currents over which the regulator has control will produce the correct voltage drop needed to produce a 5.0 VDC supply.

So, all we really need to know to design with a shunt regulator is Ohm's Law. The problem is that the supply voltage, V_{UNREG} , is not constant and neither is the load current. In addition, the range of current over which the regulator has control, is also limited. So the choice of R_{SER} really becomes a balancing act, trying to find a resistance that will meet all three requirements.

FIGURE 1: SHUNT REGULATOR BLOCK DIAGRAM

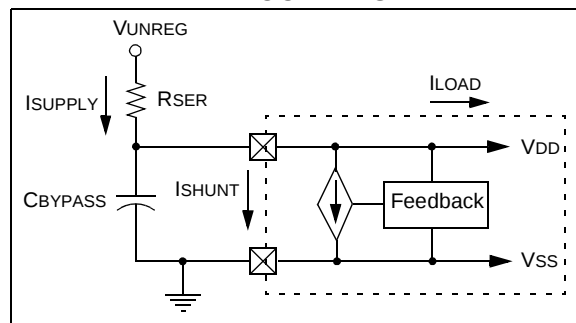

DESIGN

The best place to start in the design process is to catalog the variations possible in the supply voltage and the load current. For our purposes, the following definitions will be used:

- V_{U_MIN} is the minimum supply voltage to the system.
- V_{U_MAX} is the maximum supply voltage to the system.
- I_{LOAD_MIN} is the minimum load current, excluding the regulator.
- I_{LOAD_MAX} is the maximum load current, excluding the regulator.

Given these values, it is now possible to determine the minimum and maximum pass resistor values for the circuit. Equation 1 and Equation 2 are used to calculate these values.

Note: The constant 5.0 refers to the V_{DD} voltage of the regulator, the 4 mA constant is the minimum regulation current for the regulator and the 50 mA constant is the maximum regulation current for the regulator.

EQUATION 1:

$$R_{MAX} = \frac{(V_{U_MIN} - 5.0)}{1.05 \cdot (I_{LOAD_MAX} + 4 \text{ mA})}$$

EQUATION 2:

$$R_{MIN} = \frac{(V_{U_MAX} - 5.0)}{0.95 \cdot (I_{LOAD_MIN} + 50 \text{ mA})}$$

These values, R_{MIN} and R_{MAX} , represent the limits for the resistance of the pass resistor.

Note: If the minimum resistor value is greater than the maximum, then the combination of supply voltage variation and load current variation can not be supported by a single resistor. To correct the problem, either;

1. The variation in current drawn by the circuit must be reduced.
2. A system for varying the pass resistor is required.
3. The variation in V_{UNREG} must be reduced.

The “**Tips ‘n Tricks**” section of this document demonstrates methods for accomplishing all three options.

If the minimum value is less than the maximum value, a final pass resistor value can be chosen between the two limits. Good design practice is to then check the minimum and maximum regulator currents. Equation 3 and Equation 4 show how these values are calculated.

EQUATION 3:

$$I_{REG_MAX} = \frac{(V_{U_MAX} - 5.0)}{R_{SER}} - I_{LOAD_MIN}$$

EQUATION 4:

$$I_{REG_MIN} = \frac{(V_{U_MIN} - 5.0)}{R_{SER}} - I_{LOAD_MAX}$$

The minimum regulator current must be less than the maximum load current and the difference must be less than the maximum regulator current of 50 mA. If not, then check the calculations for the pass resistor value.

The minimum power rating of the pass resistor can now be calculated using Equation 5. Remember to allow for adequate cooling and an appropriate amount of margin when deciding on the final power rating.

EQUATION 5:

$$POWER = \frac{(V_{U_MAX} - 5.0)^2}{R_{SER}}$$

The next step is to determine the appropriate size bypass capacitor for the design. While most microcontroller applications can use “rule-of-thumb” values for their bypass capacitors, the unique nature of the shunt regulator complicates the selection.

First of all, the combination of the pass resistor and the bypass capacitor form an unintended RC time constant that limits the rise time of the microcontroller V_{DD} . Therefore, it is necessary to limit the size of the capacitor such that the resulting rise time for the V_{DD} supply is faster than the specified minimum rise time for the microcontroller's V_{DD} . The minimum rise time for a Microchip microcontroller's V_{DD} is 0.5V/mS, until the supply voltage exceeds 2.1V (Power-on Reset trip point). So, the supply must exceed 2.1 volts within 42 mS, (2.1V/0.5V/ms). Using this information and Equation 6, the maximum capacitor value can be determined.

EQUATION 6:

$$C_{MAX} = - \frac{42 \text{ MS}}{R_{SER} \cdot \ln\left(\frac{2.1}{5.0}\right)}$$

So, the bypass capacitor must be less than the value specified by Equation 6 to meet the power-up requirements of the Power-on Reset, and greater than 0.1 μF /.047 μF for noise suppression. Typically, the value is chosen to be closer to the 0.1 μF value for convenience.

Note: The “**Tips ‘n Tricks**” section discusses an example in which larger bypass values may be needed to handle severe transient current requirements.


TIPS ‘N TRICKS

As mentioned in the previous section, it is often necessary to create a variable pass resistance, reduce the variation in load current, or reduce variations in V_{UNREG} to find a pass resistor's values that will work for all load and supply conditions. This section contains examples for all three.

TIP #1 LOAD RESISTORS

One method for decreasing variations in the load current is to add load resistors to unused microcontroller outputs (see Figure 2). The outputs are set high to increase the load current at times when other portions of the circuit are only drawing minimal currents and pull low to free up load current when the circuit needs more operating current elsewhere. This allows the microcontroller to manage the load, reducing variations in the load current.

FIGURE 2: LOAD DAC SCHEMATIC

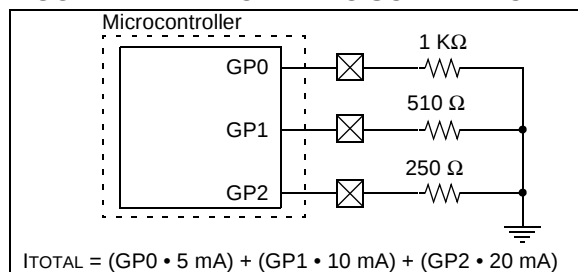


TIP #2 OPEN COLLECTOR DRIVES

Another method for decreasing load current variation is to drive higher current loads with open collector low-side drives (see Figure 3). This removes the drive current requirement from the V_{DD} supply and pushes it into the higher supply voltage, reducing variations in the load current.

Note: The base current required to bias the transistor is still sourced from the V_{DD} supply. However, the current gain of the transistor makes the required base current only 1/10 – 1/100th of the actual load current.

FIGURE 3: OPEN COLLECTOR DRIVER SCHEMATIC

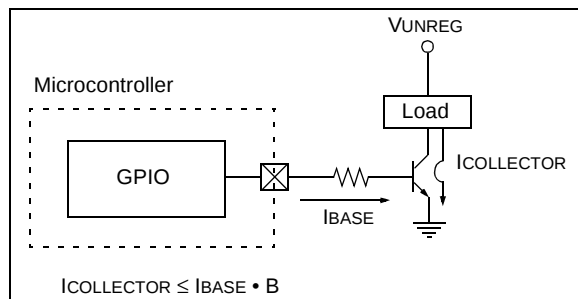


TIP #3 OPEN DRAIN DRIVES

This method for decreasing the maximum load current is basically the same as TIP #2, with the exception that the gate drive of the MOSFET does not require a continuous bias current (see Figure 4). In addition, the ON voltage drop across the MOSFET is significantly lower than a BJT. Avoiding a continuous base bias current further reduces the load current on the system, and lowering the ON voltage of the drive means that more of the energy is actually delivered to the output.

However, there is a drawback to using a MOSFET transistor. A current is required to charge or discharge the gate capacitance each time the transistor is turned on/off. Depending upon the switching speed required, the current needed to charge or discharge the gate capacitance can be as high as several amps. This requires a MOSFET driver, which further increases the current requirements of the circuit. Therefore, the decision to use a BJT versus a MOSFET should be based on the trade off between the bias current/on voltage advantages and the additional current requirements for switching the MOSFET.

FIGURE 4: OPEN DRAIN DRIVER SCHEMATIC

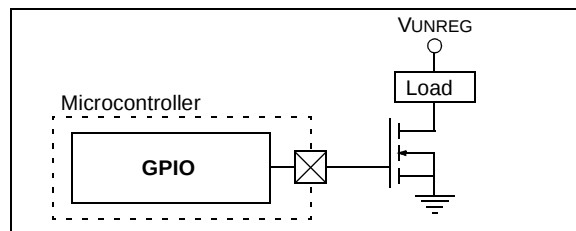

For more information concerning driving MOSFET transistors, refer to Application Note AN786, "Considerations for Driving Power MOSFET in High-Current, Switch Mode Regulators" (DS00786) and AN898, "Determining MOSFET Driver Needs for Motor Drive Applications" (DS00898).


TIP #4 TRIAC DRIVES

In systems controlling AC powered loads, a TRIAC is often employed as the output drive (see Figure 4). However, while TRIACs have been available for many, many years, some engineers are still unfamiliar with their operation and do not take full advantage of recent improvements in their design.

One of the most significant improvements in the TRIAC design is the introduction of "sensitive gate" TRIACs. These devices are designed to trigger on a much smaller gate drive current than traditional devices. The reduced drive current also means that these new TRIACs will work well, not only in quadrants 1 and 3, but also in quadrants 2 and 4, expanding the drive options open to the designer (see Figure 5).

Another improvement has been a reduction in the holding current specification for the device. The holding current is the minimum load current at which the TRIAC will latch on, removing the requirement for a continuous gate current.

FIGURE 5: TRIAC CONDUCTION QUADRANTS

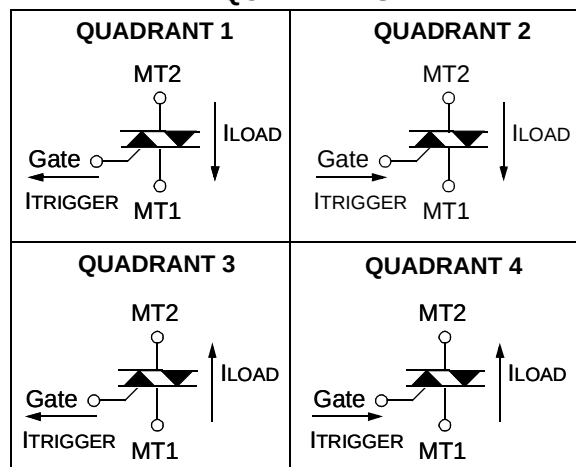

- Lower gate drive currents reduce the current that the microcontroller must source or sink to turn on the TRIAC.
- Lower holding currents reduce the time the microcontroller must hold the gate drive during each AC cycle.
- Operation in all four quadrants allow the microcontroller to use either positive or negative gate drive currents to trigger the TRIAC.

In systems with an external circuitry, it is often advantageous to be able to power-down unused circuitry to reduce current consumption. If the current requirement for a given section is less than the drive limitation of a GPIO (typically 20 mA), then the power for the circuitry can be supplied through a GPIO pin (see Figure 6). This puts control of the circuitry power under software control, which can then power the section only when needed and turn it off when the circuit is idle.

Another option is to use the GPIO to control the Shutdown or Enable input of the active devices in the circuit (op amps, ADCs, Filters or DACs).

The block diagram illustrates the system architecture. A Microcontroller (dashed box) contains three general-purpose ports: GP0, GP1, and GP2. GP0 is connected to the input of the MCP4821 DAC. GP1 is connected to the non-inverting input (+) of the MCP6546 op-amp. GP2 is connected to the inverting input (-) of the MCP6546 op-amp. The MCP4821 DAC has an 'Analog Output' terminal. The MCP6546 op-amp is configured with its non-inverting input (+) connected to GP1, its inverting input (-) connected to GP2, and its output connected to the 'Analog Output' of the MCP4821 DAC. The op-amp also has a feedback network consisting of a resistor and a capacitor connected between its output and its inverting input. The Display Module is connected to the output of the MCP6546 op-amp. The system is powered by a VDD supply, which is connected to the Microcontroller and the Display Module. Ground connections are shown for various components.

Some transient current requirements can be handled by temporarily overloading the VDD supply. In this scenario, a temporary output drive, which exceeds the current capacity of the system power supply, is enabled. The additional current required to supply the output is drawn from the bypass capacitor in the power supply and the power supply voltage momentarily sags. Once the output is disabled, the current draw is removed and the bypass capacitor charges to 5V again.

Note: This will also increase the amount of time required for the system to recover from the over load. The challenge is to balance the amount of droop against the recovery time. Equation 7 is used to determine the amount of droop the system will experience, and Equation 8 is used to determine the amount of time required for the system to recover from a drop in supply voltage.


$$VU_MIN = 5.0 - \frac{ISURGE \cdot TSURGE}{CBY_PASS}$$
$$T_{RECOVER} = \frac{(5.0V - V_{SS_MIN}) \cdot C_{BY_PASS}}{(I_{MAX} - I_{NOMINAL})}$$

In the example, the pass resistor is bypassed by a lower value resistance under software control. When the GPIO is set high, the open collector drive (Q1) pulls the base of Q2 low, which turns on Q2 and bypasses the pass resistor R1 with a lower value resistance R2.

The system is designed as two separate power supplies, one using the minimum and maximum current at the lower Current mode. The second uses the minimum and maximum current at the higher Current mode. The resistor value selected for the lower Current mode is used for R1. R2 is chosen to create a parallel combination that is equal to the pass resistor value selected for the higher Current mode.

This system is a good solution to the problem of a single pass resistor which has a higher minimum value than the desired maximum value.

FIGURE 7: DUAL VALUE PASS RESISTOR SCHEMATIC

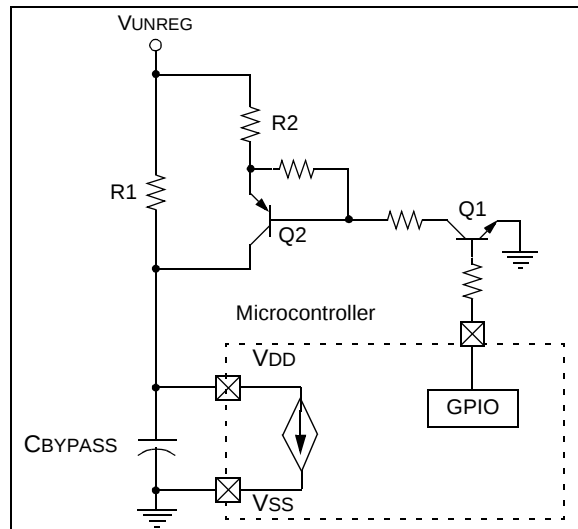


Note: The breakdown voltage of Q1 and Q2 must be greater than VUNREG.

TIP #8 INCREASING CURRENT WITH A SERIES PASS TRANSISTOR

An external pass transistor, driven by the microcontroller shunt regulator, can produce a higher current power source for external circuitry (see Figure 8). In the example, the pass transistor acts as a series regulator taking its reference from the microcontroller VDD, plus the forward voltage of the diode and providing a 4.9-5.2V power supply. The only requirement on the pass transistor is that the device must have a sufficient breakdown voltage specification to handle the supply voltage and sufficient power handling capability to deal with the power dissipated while the supply generates the full output control.

FIGURE 8: PASS RESISTOR SCHEMATIC

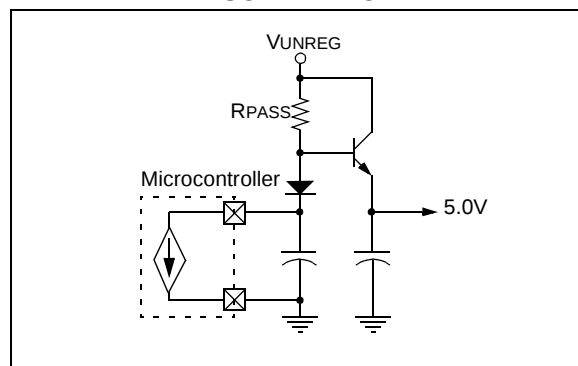


TIP #9 DECREASING VARIATIONS IN VUNREG WITH A SECONDARY DISCRETE SHUNT REGULATOR

In the previous tips, we have examined methods for reducing variations in the load current and methods for varying the value of the pass resistor. The only other variable in the design equations is variation in the supply voltage VUNREG, so, this final tip demonstrates a method for limiting the variation between VU_MIN and VU_MAX.

This is accomplished by regulating the high voltage side of VSER with another shunt regulator, this time in the form of a Zener diode. Figure 10 shows an example circuit. The two resistors, RH1 and RSER, form a voltage divider with the mid-point voltage clamped by the Zener voltage of the diode. If VUNREG increases, the Zener diode conducts additional current-to-ground causing the voltage drop across RH1 to increase while holding the mid-point voltage relatively constant. This reduces the variation seen by RSER and the second shunt regulator in the microcontroller, simplifying the choice for RSER.

FIGURE 9: SECONDARY SHUNT REGULATOR

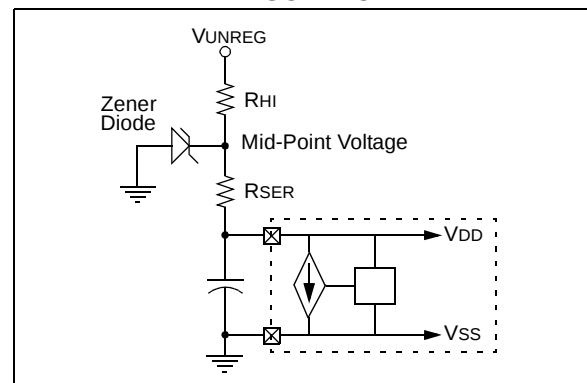

The design for the high-voltage shunt regulator follows the same procedure as the original regulator in the microcontroller. The high and low variations in VUNREG are documented, as are the high and low load currents required for the load (microcontroller, shunt regulator and additional loads). A Zener diode is selected based on a Zener voltage roughly half way between VUNREG_MIN and VDD.

Note: The current range of the Zener diode should be large enough to put the Zener diode beyond the knee in the diode curve, (see Figure 10), but still well within the maximum power rating for the device. The maximum diode current should also be determined and documented.

Once this information is collected, a minimum and maximum value for RH1 can be calculated. Equation 8 and Equation 9 are just variations of Equation 1 and Equation 2 with the Zener voltage substituted for VDD.

EQUATION 9:

$$R_{HI_MAX} = \frac{(V_{U_MIN} - V_{ZENER})}{1.05 \cdot (I_{LOAD_MAX} + I_{ZENER_MIN})}$$

EQUATION 10:

$$R_{HI_MIN} = \frac{(V_{U_MAX} - V_{ZENER})}{0.95 \cdot (I_{LOAD_MIN} + I_{ZENER_MAX})}$$

If the value can not be found that falls between the two limits, select a higher power Zener, which will increase I_{ZENER_MAX} or lower the Zener voltage to a value closer to V_{DD} . If a value can not be found, or if the power dissipated by the Zener or R_{HI} is too large, and the other tips in this application note can not provide any relief for the problem, then a switching regulator may be needed to ultimately solve the problem.

However, if a value is found for R_{HI} and the Zener diode, the next step is to determine the variation in I_{ZENER} based on V_{UNREG} and R_{HI} . Equation 11 and Equation 12 are used to determine both the high and low Zener diode current.

EQUATION 11:

$$I_{ZENER_MAX} = \frac{(V_{U_MAX} - V_{ZENER})}{R_{HI} \cdot 0.95} - I_{LOAD_MIN}$$


EQUATION 12:

$$I_{ZENER_MIN} = \frac{(V_{U_MIN} - V_{ZENER})}{R_{HI} \cdot 1.05} - I_{LOAD_MAX}$$

Given the minimum and maximum Zener diode currents, the minimum and maximum mid-point voltage can be found from the I-V chart for the Zener diode. See Figure 10 for an example I-V chart. To find the minimum value, scale the curve such that the Zener voltage is equal to the minimum Zener voltage value specified for the diode and take the value from the minimum Zener current estimate. To find the maximum voltage, scale the curve such that the Zener voltage is equal to the maximum specified Zener voltage and take the voltage value based on the maximum current.

The maximum and minimum mid-point voltages are then used for V_{U_MIN} and V_{U_MAX} in the original design Equation 1 and Equation 2 to calculate R_{SER} . The remainder of the design then follows the original procedure from the beginning of this document.

FIGURE 10: I-V CURVE FOR A ZENER DIODE

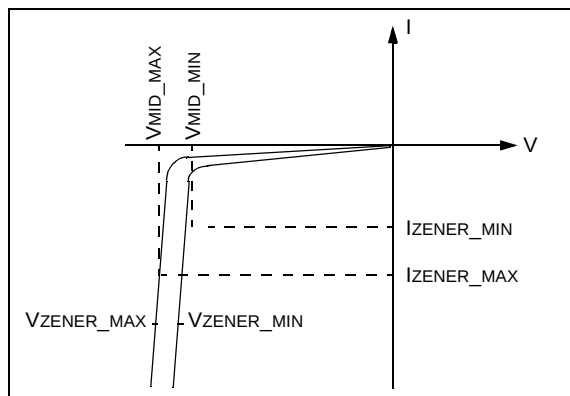

Note: The Zener diode power rating will limit the maximum current that the diode can sink when clamping the mid-point voltage. However, most Zener diodes also specify a maximum surge power, which extends the power rating of the device for transient power dissipation. If the maximum value for V_{UNREG} is based on transient jumps in the voltage due to noise or switching of other systems, then a smaller Zener diode may be used provided the transient is within maximum power surge power rating for the diode.

CONCLUSIONS

The inclusion of a shunt regulator can simplify the design of control circuits which must operate from voltages above the normal range of the microcontroller's supply voltage. The circuit can even act as a supply for other active devices in the circuit. All that is required is a little careful design and component selection.

MEMORY USAGE

Not applicable

REFERENCE DOCUMENTATION

- AN786, "Considerations for Driving MOSFETs in High-Current, Switch Mode Regulators" (DS00786).
- AN898, "Determining MOSFET Driver Needs for Motor Drive Applications" (DS00898).

Note the following details of the code protection feature on Microchip devices:

- Microchip products meet the specification contained in their particular Microchip Data Sheet.
- Microchip believes that its family of products is one of the most secure families of its kind on the market today, when used in the intended manner and under normal conditions.
- There are dishonest and possibly illegal methods used to breach the code protection feature. All of these methods, to our knowledge, require using the Microchip products in a manner outside the operating specifications contained in Microchip's Data Sheets. Most likely, the person doing so is engaged in theft of intellectual property.
- Microchip is willing to work with the customer who is concerned about the integrity of their code.
- Neither Microchip nor any other semiconductor manufacturer can guarantee the security of their code. Code protection does not mean that we are guaranteeing the product as "unbreakable."

Code protection is constantly evolving. We at Microchip are committed to continuously improving the code protection features of our products. Attempts to break Microchip's code protection feature may be a violation of the Digital Millennium Copyright Act. If such acts allow unauthorized access to your software or other copyrighted work, you may have a right to sue for relief under that Act.

Information contained in this publication regarding device applications and the like is provided only for your convenience and may be superseded by updates. It is your responsibility to ensure that your application meets with your specifications. MICROCHIP MAKES NO REPRESENTATIONS OR WARRANTIES OF ANY KIND WHETHER EXPRESS OR IMPLIED, WRITTEN OR ORAL, STATUTORY OR OTHERWISE, RELATED TO THE INFORMATION, INCLUDING BUT NOT LIMITED TO ITS CONDITION, QUALITY, PERFORMANCE, MERCHANTABILITY OR FITNESS FOR PURPOSE. Microchip disclaims all liability arising from this information and its use. Use of Microchip devices in life support and/or safety applications is entirely at the buyer's risk, and the buyer agrees to defend, indemnify and hold harmless Microchip from any and all damages, claims, suits, or expenses resulting from such use. No licenses are conveyed, implicitly or otherwise, under any Microchip intellectual property rights.

Trademarks

The Microchip name and logo, the Microchip logo, Accuron, dsPIC, KEELoQ, microID, MPLAB, PIC, PICmicro, PICSTART, PRO MATE, PowerSmart, rfPIC, and SmartShunt are registered trademarks of Microchip Technology Incorporated in the U.S.A. and other countries.

AmpLab, FilterLab, Migratable Memory, MXDEV, MXLAB, SEEVAL, SmartSensor and The Embedded Control Solutions Company are registered trademarks of Microchip Technology Incorporated in the U.S.A.

Analog-for-the-Digital Age, Application Maestro, dsPICDEM, dsPICDEM.net, dsPICworks, ECAN, ECONOMONITOR, FanSense, FlexROM, fuzzyLAB, In-Circuit Serial Programming, ICSP, ICEPIC, Linear Active Thermistor, MPASM, MPLIB, MPLINK, MPSIM, PICKIT, PICDEM, PICDEM.net, PICLAB, PICtail, PowerCal, PowerInfo, PowerMate, PowerTool, REAL ICE, rLAB, rfPICDEM, Select Mode, Smart Serial, SmartTel, Total Endurance, UNI/O, WiperLock and ZENA are trademarks of Microchip Technology Incorporated in the U.S.A. and other countries.

SQTP is a service mark of Microchip Technology Incorporated in the U.S.A.

All other trademarks mentioned herein are property of their respective companies.

© 2006, Microchip Technology Incorporated, Printed in the U.S.A., All Rights Reserved.

 Printed on recycled paper.

QUALITY MANAGEMENT SYSTEM
CERTIFIED BY DNV
== ISO/TS 16949:2002 ==

Microchip received ISO/TS-16949:2002 quality system certification for its worldwide headquarters, design and wafer fabrication facilities in Chandler and Tempe, Arizona and Mountain View, California in October 2003. The Company's quality system processes and procedures are for its PICmicro® 8-bit MCUs, KEELoQ® code hopping devices, Serial EEPROMs, microperipherals, nonvolatile memory and analog products. In addition, Microchip's quality system for the design and manufacture of development systems is ISO 9001:2000 certified.



WORLDWIDE SALES AND SERVICE

AMERICAS

Corporate Office
2355 West Chandler Blvd.
Chandler, AZ 85224-6199
Tel: 480-792-7200
Fax: 480-792-7277
Technical Support:
<http://support.microchip.com>
Web Address:
www.microchip.com

Atlanta

Alpharetta, GA
Tel: 770-640-0034
Fax: 770-640-0307

Boston

Westborough, MA
Tel: 774-760-0087
Fax: 774-760-0088

Chicago

Itasca, IL
Tel: 630-285-0071
Fax: 630-285-0075

Dallas

Addison, TX
Tel: 972-818-7423
Fax: 972-818-2924

Detroit

Farmington Hills, MI
Tel: 248-538-2250
Fax: 248-538-2260

Kokomo

Kokomo, IN
Tel: 765-864-8360
Fax: 765-864-8387

Los Angeles

Mission Viejo, CA
Tel: 949-462-9523
Fax: 949-462-9608

San Jose

Mountain View, CA
Tel: 650-215-1444
Fax: 650-961-0286

Toronto

Mississauga, Ontario,
Canada
Tel: 905-673-0699
Fax: 905-673-6509

ASIA/PACIFIC

Australia - Sydney
Tel: 61-2-9868-6733
Fax: 61-2-9868-6755

China - Beijing
Tel: 86-10-8528-2100
Fax: 86-10-8528-2104

China - Chengdu
Tel: 86-28-8676-6200
Fax: 86-28-8676-6599

China - Fuzhou
Tel: 86-591-8750-3506
Fax: 86-591-8750-3521

China - Hong Kong SAR
Tel: 852-2401-1200
Fax: 852-2401-3431

China - Qingdao
Tel: 86-532-8502-7355
Fax: 86-532-8502-7205

China - Shanghai
Tel: 86-21-5407-5533
Fax: 86-21-5407-5066

China - Shenyang
Tel: 86-24-2334-2829
Fax: 86-24-2334-2393

China - Shenzhen
Tel: 86-755-8203-2660
Fax: 86-755-8203-1760

China - Shunde
Tel: 86-757-2839-5507
Fax: 86-757-2839-5571

China - Wuhan
Tel: 86-27-5980-5300
Fax: 86-27-5980-5118

China - Xian
Tel: 86-29-8833-7250
Fax: 86-29-8833-7256

ASIA/PACIFIC

India - Bangalore
Tel: 91-80-4182-8400
Fax: 91-80-4182-8422

India - New Delhi
Tel: 91-11-5160-8631
Fax: 91-11-5160-8632

India - Pune
Tel: 91-20-2566-1512
Fax: 91-20-2566-1513

Japan - Yokohama
Tel: 81-45-471- 6166
Fax: 81-45-471-6122

Korea - Gumi
Tel: 82-54-473-4301
Fax: 82-54-473-4302

Korea - Seoul
Tel: 82-2-554-7200
Fax: 82-2-558-5932 or
82-2-558-5934

Malaysia - Penang
Tel: 60-4-646-8870
Fax: 60-4-646-5086

Philippines - Manila
Tel: 63-2-634-9065
Fax: 63-2-634-9069

Singapore
Tel: 65-6334-8870
Fax: 65-6334-8850

Taiwan - Hsin Chu
Tel: 886-3-572-9526
Fax: 886-3-572-6459

Taiwan - Kaohsiung
Tel: 886-7-536-4818
Fax: 886-7-536-4803

Taiwan - Taipei
Tel: 886-2-2500-6610
Fax: 886-2-2508-0102

Thailand - Bangkok
Tel: 66-2-694-1351
Fax: 66-2-694-1350

EUROPE

Austria - Wels
Tel: 43-7242-2244-399
Fax: 43-7242-2244-393

Denmark - Copenhagen
Tel: 45-4450-2828
Fax: 45-4485-2829

France - Paris
Tel: 33-1-69-53-63-20
Fax: 33-1-69-30-90-79

Germany - Munich
Tel: 49-89-627-144-0
Fax: 49-89-627-144-44

Italy - Milan
Tel: 39-0331-742611
Fax: 39-0331-466781

Netherlands - Drunen
Tel: 31-416-690399
Fax: 31-416-690340

Spain - Madrid
Tel: 34-91-708-08-90
Fax: 34-91-708-08-91

UK - Wokingham
Tel: 44-118-921-5869
Fax: 44-118-921-5820