

Bridge Sensing with the MCP6S2X PGAs

Author: Bonnie C. Baker
Microchip Technology Inc.

INTRODUCTION

Resistive sensors configured as Wheatstone bridges are primarily used to sense pressure, temperature or loads. An external A/D converter (ADC) and a digitally Programmable Gain Amplifier (PGA) can easily be used to convert the difference voltage from these resistor bridge sensors to usable digital words for manipulation by the microcontroller. When the PGA is used in this system, the other channels of the MCP6S2X can be used for other sensors without an increase in signal conditioning hardware or PICmicro® microcontroller I/O pin consumption. The multiplexer and high-speed conversion response of the PGA/Analog-to-Digital (A/D) conversion allows a differential input signal to be sampled and converted in the analog domain and then subtracted in the digital domain with the microcontroller.

BRIDGE DATA ACQUISITION SYSTEM

An application circuit for this type of sensor environment is shown in Figure 1.

In this circuit, the bridge is excited by a voltage source (V_{SEN}). This reference voltage can be V_{DD} , generated using a current source or provided by a voltage reference device. Regardless of the approach used to generate this source, it is utilized across the circuit in order to provide a ratiometric digital result. The two outputs of the sensor are connected to the internal multiplexor of the MCP6S26 PGA. The PGA is controlled digitally for gain, as well as toggling between CH0 and CH1. The gain options for the PGA are: 1, 2, 4, 5, 8, 10, 16 and 32 V/V.

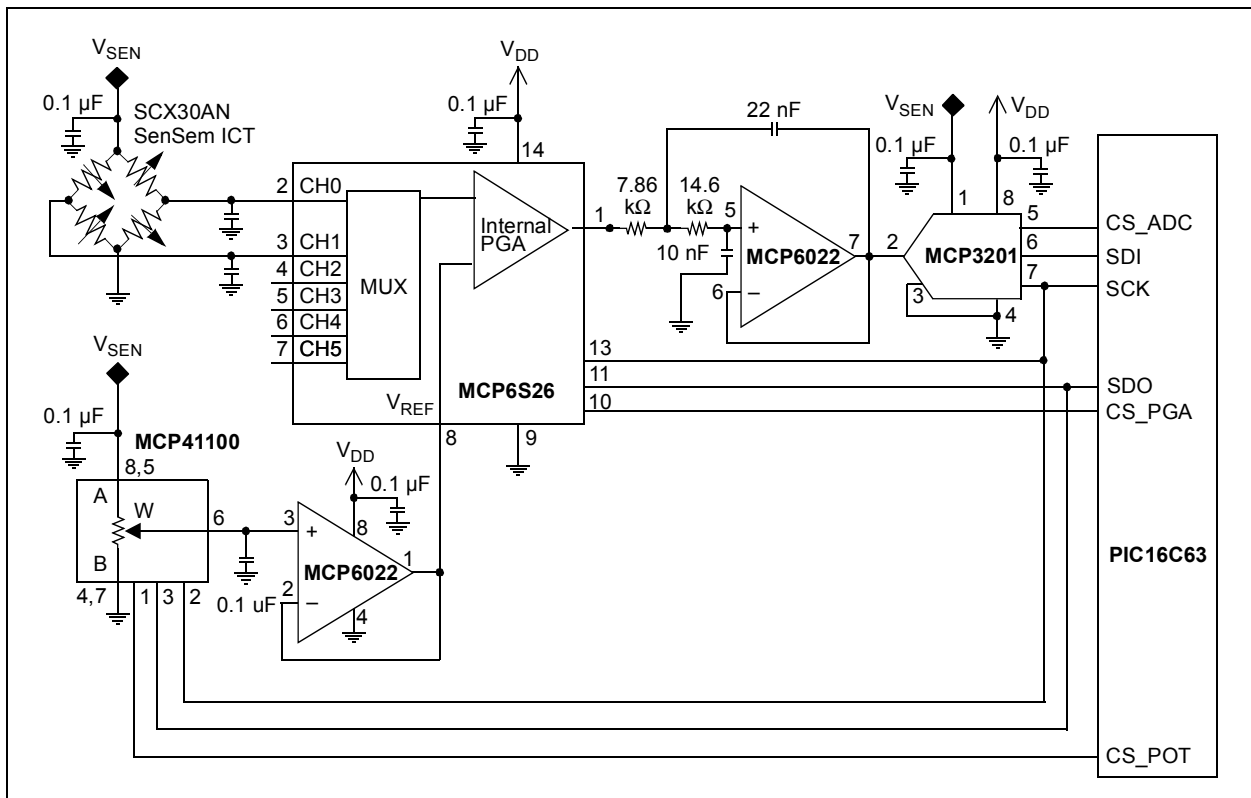


FIGURE 1: A resistive bridge output voltage is gained and converted to a 12-bit word using the MCP6S26, six-channel PGA for analog gain and a 12-bit ADC (MCP3201).

The reference to the PGA in Figure 1 (MCP6S26, pin 8) is provided by the digital potentiometer, MCP41100. Alternatively, the voltage reference pin of the PGA can be driven with a D/A voltage-out converter, a dedicated voltage reference chip, a resistive divider circuit or tied to ground or V_{DD} . In all cases, the voltage reference source should be low-impedance. A variable voltage reference may be required because of the various requirements on other channels of the PGA. If a variable voltage reference is required, the circuit in Figure 1 can be used.

The potentiometer in Figure 1 (MCP41100) is a 100 k Ω element that can be programmed in $V_{SEN}/256$ step sizes. For this application, the digital potentiometer should be programmed approximately at the center voltage of the bridge outputs, or approximately $V_{SEN}/2$. For more detailed information on the determination of the reference voltage value, refer to the "PGA Reference Voltage" section. If this circuit is used to sense additional inputs on CH2 through CH5, the digital potentiometer could be used to adjust each input. If this circuit is only used to measure a bridge, a resistor divider could be used instead. The output of the MCP41100 is buffered with the MCP6022 operational amplifier (op amp). This amplifier is selected to isolate the digital potentiometer from the PGA and was specifically chosen to match the speed of the MCP6S26. The MCP6022 is a CMOS, 10 MHz unity gain stable op amp. This device is capable of responding to any fast current requirements to drive the resistor array in the MCP6S26 during ac operation.

At the output of the PGA, an anti-aliasing filter is inserted. This is done prior to the A/D conversion in order to reduce noise. The anti-aliasing filter can be designed with a gain of one or higher, depending on the circuit requirements. Again, the MCP6022 op amp is used to match the frequency response of the PGA. Microchip's FilterLab[®] software can be used to easily design this filter's frequency cut-off and gain.

The anti-aliasing filter in this circuit is a Sallen-Key (non-inverting configuration) with a cut-off frequency of 1 kHz. Generally speaking, the corner frequency of this filter should be designed to complement all of the input signals to the multiplexer in your specific design. For more information regarding the design of anti-aliasing filters, refer to Microchip Technology's AN699, "Anti-Aliasing, Analog Filters for Data Acquisition Systems" (DS00699).

The signal at the output of the filter is connected to the input of a 12-bit ADC, MCP3201. In this circuit, if noise is kept under control, it is possible to obtain 12-bit accuracy from the converter. Beyond the anti-aliasing filter, noise is kept under control by appropriate bypass capacitors, short traces, linear supplies and a solid ground plane. The entire system is manipulated on the same Serial Peripheral Interface (SPI[™]) bus of the PIC16C63 for the PGA, digital potentiometer and ADC with no digital feedthrough from the converter during

conversion. Any PICmicro[®] microcontroller can be used in this circuit. In Figure 1, the PIC16C623 was selected for its SPI ports and clock speed. In this circuit, the PGA is toggled between CH0 and CH1. In each state, the voltage at the output of the PGA is converted by the 12-bit ADC. It is important to keep CH0 and CH1 relatively static (within 12-bit accuracy) during this dual measurement. To derive the final voltage difference between CH0 and CH1, the data taken from CH0 and CH1 is subtracted and divided by the gain in the microcontroller to derive the voltage across the bridge.

Bus lines to the microcontroller can be eliminated by changing the digital potentiometer to a voltage divider or voltage reference, such as the MCP1525 (2.5V Precision Reference). Alternatively, the microcontroller's internal ADC can replace the MCP3201, if one is available. As an option, the PGA and digital potentiometer can be daisy-chained, eliminating the use of one I/O line. Refer to DS2117, "Single Ended, Rail-to-Rail I/O, Low Gain PGA", and DS11195, "Single/Dual Digital Potentiometer with SPI[™] Interface", for details.

DETAILS OF PGA CIRCUIT OPERATION

An instrumentation amplifier (INA) is typically used instead of the PGA used in this circuit. The PGA's strength in this application is its front-end multiplexer and gain adjustability, allowing an easy interface to a variety of sensors and/or channels in the same application circuit. With an INA, the gain and reference voltage to the INA are not easily adjusted from the microcontroller. The PGA is easily adjusted in this respect by offering gain selectability, channel selectability and easy voltage reference adjustment.

The conversion speed of this circuit was affected by the conversion time of the ADC and channel-to-channel switching time of the PGA. The conversion time of the ADC was 50 ksp/s, taking 20 μ secs to convert and store data. The PGA channel-switching time was 20 μ secs. The total time that was required to switch from channel-to-channel was 50 μ secs, including additional PICmicro code. In this manner, the interfering main's noise was rejected.

Discussion of the design of other PGA circuits that can be implemented with different sensors is found in Microchip Technology's AN865, "Sensing Light with a Programmable Gain Amplifier" (DS00865).

PGA Reference Voltage

The input range of the reference voltage pin is V_{SS} to V_{DD} of the PGA. In this case, V_{SS} = Ground and V_{DD} = 5V. The transfer function of the PGA is equal to:

EQUATION

$$V_{OUT} = GV_{IN} - (G - 1)V_{REF}$$

With this ideal formula, the actual restrictions on the output of the PGA should be taken into consideration. Generally speaking, the output swing of the PGA is less than 20 mV from the positive rail and 125 mV above ground, as specified in the MCP6S2X PGA data sheet (DS21117). However, to obtain good, linear performance, the output should be kept within 300 mV from both rails. This is specified in the conditions of the “DC gain error” and “DC output non-linearity”.

Consequently, beyond the absolute voltage limitations on the PGA voltage reference pin, the voltage output swing capability further limits the selection of the voltage at pin 8. This is illustrated in Figure 2 and Figure 3 below.

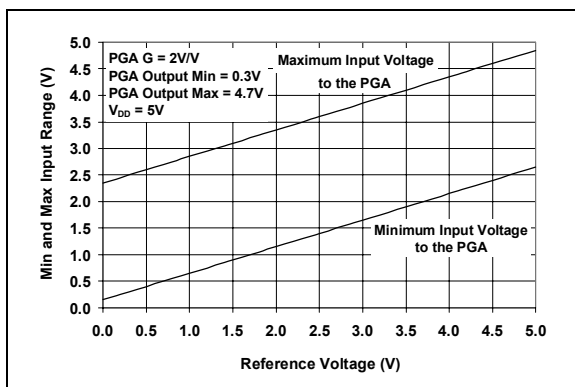


FIGURE 2: If the programmed gain to the PGA is 2, the voltage applied to V_{REF} (pin 8) is limited to approximated 1/2 of the range in a gain of 1 V/V.

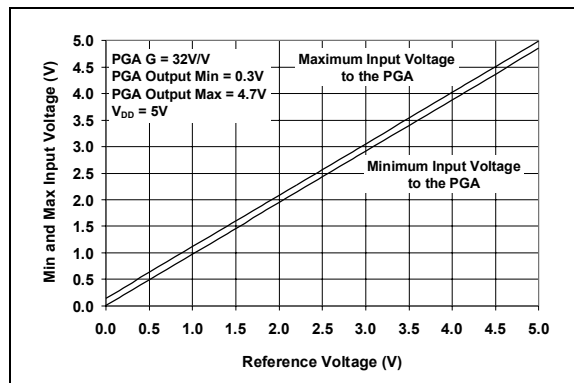


FIGURE 3: If the programmed gain to the PGA is 32, the voltage applied to V_{REF} (pin 8) is limited to approximated 1/32 of the range in a gain of 1 V/V.

As shown in Figure 2 and Figure 3, the reference voltage of the PGA should be programmed between the expected input voltage range of the PGA. For instance, in a gain of 2 V/V (Figure 2) with an input range of 1.0V to 3.2V, the voltage reference at pin 8 of the MCP6S26 should be equal to 1.7V for optimum performance.

The formulas that are to be used to calculate the appropriate gain setting (G) for the PGA and the optimum V_{REF} value are:

EQUATION

$$V_{IN}(min) \geq (V_{OUT}(min) + (G - 1)V_{REF})/G$$

$$V_{IN}(max) \geq (V_{OUT}(max) + (G - 1)V_{REF})/G$$

where:

V_{IN} = input voltage to the PGA.

$V_{OUT}(min)$ = minimum output voltage of PGA
= $V_{SS} + 0.3V$.

$V_{OUT}(max)$ = minimum output voltage of PGA
= $V_{DD} - 0.3V$.

G = gain of the PGA.

V_{REF} = Voltage reference applied to pin 8 of the PGA.

AN251

Performance Data

In the circuit of Figure 1, the power supply (V_{DD}) was 5V and the voltage applied to V_{SEN} was also 5V. The reference voltage to the PGA was generated by the MCP1525, a 2.5V precision voltage reference. The gain setting of the PGA is 32 V/V. The analog filter was built to have a 1 kHz cut-off frequency.

The pressure sensor, SCX30AN (a precision compensated pressure sensor) from SenSym ICT was used. The standard full-scale pressure range of this sensor is 30 PSI, with a full-scale output voltage of 90 mV (typ.). Pressure was generated using the PCL425-PUMP pressure pump from Omega™. The pressure from this pump was verified with HHP-102E Handheld Manometer also from Omega.

The data taken from this setup is given in a tabular form in Table 1 and is graphically illustrated in Figure 4.

TABLE 1: DATA TAKEN USING THE CIRCUIT IN FIGURE 1*

PSI	CH0 Code	CH1 Code
0	1569	2063
5.5	1505	2162
7.6	1475	2199
10.9	1421	2262
13.2	1386	2301
18.3	1315	2390
21.4	1286	2446
26.7	1188	2535
27.4	1180	2550
29.9	1140	2590

* This data indicates that the sensor is relatively linear across the PSI range of measurement

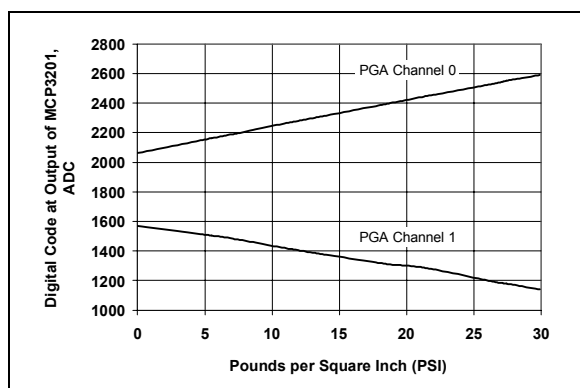


FIGURE 4: The tabular data from Table 1 is shown graphically in this figure.

This data was taken using one MCP6S26, MCP3201, MCP6022 and pressure sensor from SenSym ICT. The selected pressure sensor for this application note is not necessarily the appropriate sensor for all applications. The data is reported reliably, but does not represent a statistical sample of the performance of all devices in the products' families. During this test, a 120 Hz interference signal was recorded due to the mains supply. If data is converted from channel-to-channel before the signal changes more than 1/4 LSb (due to this interfering signal), the common mode error signal will not be superimposed on the resulting data. In this manner, the mains common mode signal is rejected.

CONCLUSION

This circuit provides an accurate conversion for Wheatstone bridge networks. With Microchip's line of PGAs, there are several issues that are also resolved before inserting the MCP6S26 in the circuit. Regardless of the gain, the circuit is stable. This is contrary to a stand-alone amplifier, where stability could compromise the circuit. This is particularly true if the gain of the op amp circuit is being changed on the fly. Additionally, the bandwidth with the PGA is kept fairly constant. It is true that the internal amplifier has a voltage feedback topology, but Microchip not only changes the gain, it also changes the compensation with every programmed gain change.

The MCP6S2X family of PGAs have one channel, two channel, six and eight-channel devices in the product offering. Changing from channel-to-channel would require one 16-bit communication to occur between the PGA on the SPI interface. A clock rate of 10 MHz on the SPI interface would require approximately ~1.6 μ s. Additionally, the PGA amplifier would need to settle. Refer to the MCP6S2X PGA data sheet (DS21117) for the settling time versus gain specification.

The PGA, a precision device from Microchip Technology Inc., not only offers excellent offset voltage performance, but also the configurations in this sensing circuit are easily designed without the headaches of stability that the stand-alone amplifier circuits present to the designer. Stability with these programmable gain amplifiers have been built-in by Microchip's engineers.

REFERENCES

- AN865, "Sensing Light with a Programmable Gain Amplifier", Bonnie C. Baker; Microchip Technology Inc. (DS00865).
- AN699, "Anti-Aliasing, "Analog Filters for Data Acquisition Systems", Bonnie C. Baker; Microchip Technology Inc. (DS00699).

Note the following details of the code protection feature on Microchip devices:

- Microchip products meet the specification contained in their particular Microchip Data Sheet.
- Microchip believes that its family of products is one of the most secure families of its kind on the market today, when used in the intended manner and under normal conditions.
- There are dishonest and possibly illegal methods used to breach the code protection feature. All of these methods, to our knowledge, require using the Microchip products in a manner outside the operating specifications contained in Microchip's Data Sheets. Most likely, the person doing so is engaged in theft of intellectual property.
- Microchip is willing to work with the customer who is concerned about the integrity of their code.
- Neither Microchip nor any other semiconductor manufacturer can guarantee the security of their code. Code protection does not mean that we are guaranteeing the product as "unbreakable."

Code protection is constantly evolving. We at Microchip are committed to continuously improving the code protection features of our products. Attempts to break microchip's code protection feature may be a violation of the Digital Millennium Copyright Act. If such acts allow unauthorized access to your software or other copyrighted work, you may have a right to sue for relief under that Act.

Information contained in this publication regarding device applications and the like is intended through suggestion only and may be superseded by updates. It is your responsibility to ensure that your application meets with your specifications. No representation or warranty is given and no liability is assumed by Microchip Technology Incorporated with respect to the accuracy or use of such information, or infringement of patents or other intellectual property rights arising from such use or otherwise. Use of Microchip's products as critical components in life support systems is not authorized except with express written approval by Microchip. No licenses are conveyed, implicitly or otherwise, under any intellectual property rights.

Trademarks

The Microchip name and logo, the Microchip logo, KEELOQ, MPLAB, PIC, PICmicro, PICSTART, PRO MATE and PowerSmart are registered trademarks of Microchip Technology Incorporated in the U.S.A. and other countries.


FilterLab, microID, MXDEV, MXLAB, PICMASTER, SEEVAL and The Embedded Control Solutions Company are registered trademarks of Microchip Technology Incorporated in the U.S.A.


Accuron, Application Maestro, dsPIC, dsPICDEM, dsPICDEM.net, ECONOMONITOR, FanSense, FlexROM, fuzzyLAB, In-Circuit Serial Programming, ICSP, ICEPIC, microPort, Migratable Memory, MPASM, MPLIB, MPLINK, MPSIM, PICC, PICkit, PICDEM, PICDEM.net, PowerCal, PowerInfo, PowerMate, PowerTool, rLAB, rPIC, Select Mode, SmartSensor, SmartShunt, SmartTel and Total Endurance are trademarks of Microchip Technology Incorporated in the U.S.A. and other countries.

Serialized Quick Turn Programming (SQTP) is a service mark of Microchip Technology Incorporated in the U.S.A.

All other trademarks mentioned herein are property of their respective companies.

© 2003, Microchip Technology Incorporated, Printed in the U.S.A., All Rights Reserved.

 Printed on recycled paper.

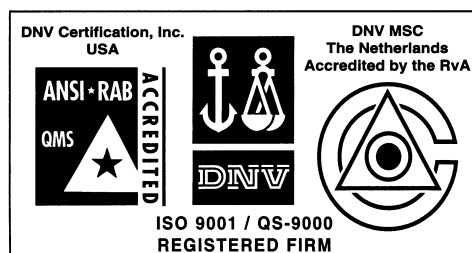

Microchip received QS-9000 quality system certification for its worldwide headquarters, design and wafer fabrication facilities in Chandler and Tempe, Arizona in July 1999 and Mountain View, California in March 2002. The Company's quality system processes and procedures are QS-9000 compliant for its PICmicro® 8-bit MCUs, KEELOQ® code hopping devices, Serial EEPROMs, microperipherals, non-volatile memory and analog products. In addition, Microchip's quality system for the design and manufacture of development systems is ISO 9001 certified.



WORLDWIDE SALES AND SERVICE

AMERICAS

Corporate Office

2355 West Chandler Blvd.
Chandler, AZ 85224-6199
Tel: 480-792-7200 Fax: 480-792-7277
Technical Support: 480-792-7627
Web Address: <http://www.microchip.com>

Atlanta

3780 Mansell Road, Suite 130
Alpharetta, GA 30022
Tel: 770-640-0034 Fax: 770-640-0307

Boston

2 Lan Drive, Suite 120
Westford, MA 01886
Tel: 978-692-3848 Fax: 978-692-3821

Chicago

333 Pierce Road, Suite 180
Itasca, IL 60143
Tel: 630-285-0071 Fax: 630-285-0075

Dallas

4570 Westgrove Drive, Suite 160
Addison, TX 75001
Tel: 972-818-7423 Fax: 972-818-2924

Detroit

Tri-Atria Office Building
32255 Northwestern Highway, Suite 190
Farmington Hills, MI 48334
Tel: 248-538-2250 Fax: 248-538-2260

Kokomo

2767 S. Albright Road
Kokomo, Indiana 46902
Tel: 765-864-8360 Fax: 765-864-8387

Los Angeles

18201 Von Karman, Suite 1090
Irvine, CA 92612
Tel: 949-263-1888 Fax: 949-263-1338

Phoenix

2355 West Chandler Blvd.
Chandler, AZ 85224-6199
Tel: 480-792-7966 Fax: 480-792-4338

San Jose

Microchip Technology Inc.
2107 North First Street, Suite 590
San Jose, CA 95131
Tel: 408-436-7950 Fax: 408-436-7955

Toronto

6285 Northam Drive, Suite 108
Mississauga, Ontario L4V 1X5, Canada
Tel: 905-673-0699 Fax: 905-673-6509

ASIA/PACIFIC

Australia

Microchip Technology Australia Pty Ltd
Marketing Support Division
Suite 22, 41 Rawson Street
Epping 2121, NSW
Australia
Tel: 61-2-9868-6733 Fax: 61-2-9868-6755

China - Beijing

Microchip Technology Consulting (Shanghai)
Co., Ltd., Beijing Liaison Office
Unit 915
Bei Hai Wan Tai Bldg.
No. 6 Chaoyangmen Beidajie
Beijing, 100027, No. China
Tel: 86-10-85282100 Fax: 86-10-85282104

China - Chengdu

Microchip Technology Consulting (Shanghai)
Co., Ltd., Chengdu Liaison Office
Rm. 2401-2402, 24th Floor,
Ming Xing Financial Tower
No. 88 TIDU Street
Chengdu 610016, China
Tel: 86-28-86766200 Fax: 86-28-86766599

China - Fuzhou

Microchip Technology Consulting (Shanghai)
Co., Ltd., Fuzhou Liaison Office
Unit 28F, World Trade Plaza
No. 71 Wusi Road
Fuzhou 350001, China
Tel: 86-591-7503506 Fax: 86-591-7503521

China - Hong Kong SAR

Microchip Technology Hongkong Ltd.
Unit 901-6, Tower 2, Metroplaza
223 Hing Fong Road
Kwai Fong, N.T., Hong Kong
Tel: 852-2401-1200 Fax: 852-2401-3431

China - Shanghai

Microchip Technology Consulting (Shanghai)
Co., Ltd.
Room 701, Bldg. B
Far East International Plaza
No. 317 Xian Xia Road
Shanghai, 200051
Tel: 86-21-6275-5700 Fax: 86-21-6275-5060

China - Shenzhen

Microchip Technology Consulting (Shanghai)
Co., Ltd., Shenzhen Liaison Office
Rm. 1812, 18/F, Building A, United Plaza
No. 5022 Binhe Road, Futian District
Shenzhen 518033, China
Tel: 86-755-82901380 Fax: 86-755-82966626

China - Qingdao

Rm. B505A, Fullhope Plaza,
No. 12 Hong Kong Central Rd.
Qingdao 266071, China
Tel: 86-532-5027355 Fax: 86-532-5027205

India

Microchip Technology Inc.
India Liaison Office
Marketing Support Division
Divyasree Chambers
1 Floor, Wing A (A3/A4)
No. 11, O'Shaughnessy Road
Bangalore, 560 025, India
Tel: 91-80-2290061 Fax: 91-80-2290062

Japan

Microchip Technology Japan K.K.
Benex S-1 6F
3-18-20, Shinyokohama
Kohoku-Ku, Yokohama-shi
Kanagawa, 222-0033, Japan
Tel: 81-45-471-6166 Fax: 81-45-471-6122

Korea

Microchip Technology Korea
168-1, Youngbo Bldg. 3 Floor
Samsung-Dong, Kangnam-Ku
Seoul, Korea 135-882
Tel: 82-2-554-7200 Fax: 82-2-558-5934

Singapore

Microchip Technology Singapore Pte Ltd.
200 Middle Road
#07-02 Prime Centre
Singapore, 188980
Tel: 65-6334-8870 Fax: 65-6334-8850

Taiwan

Microchip Technology (Barbados) Inc.,
Taiwan Branch
11F-3, No. 207
Tung Hua North Road
Taipei, 105, Taiwan
Tel: 886-2-2717-7175 Fax: 886-2-2545-0139

EUROPE

Austria

Microchip Technology Austria GmbH
Durisolstrasse 2
A-4600 Wels
Austria
Tel: 43-7242-2244-399
Fax: 43-7242-2244-393

Denmark

Microchip Technology Nordic ApS
Regus Business Centre
Lautrup høj 1-3
Ballerup DK-2750 Denmark
Tel: 45 4420 9895 Fax: 45 4420 9910

France

Microchip Technology SARL
Parc d'Activite du Moulin de Massy
43 Rue du Saule Trapu
Batiment A - 1er Etage
91300 Massy, France
Tel: 33-1-69-53-63-20 Fax: 33-1-69-30-90-79

Germany

Microchip Technology GmbH
Steinheilstrasse 10
D-85737 Ismaning, Germany
Tel: 49-89-627-144-0
Fax: 49-89-627-144-44

Italy

Microchip Technology SRL
Via Quasimodo, 12
20025 Legnano (MI)
Milan, Italy
Tel: 39-0331-742611 Fax: 39-0331-466781

United Kingdom

Microchip Ltd.
505 Eskdale Road
Winnersh Triangle
Wokingham
Berkshire, England RG41 5TU
Tel: 44 118 921 5869 Fax: 44-118 921-5820

03/25/03