

## Power-up Considerations

Author: *Sumit Mitra*  
Microchip Technology Inc.

### INTRODUCTION

When powering up any microcontroller it is necessary for the power supply voltage to traverse voltage ranges, where the device is not guaranteed to operate, before the power supply voltage reaches its final state. Since some circuits on the device (logic) will start operating at voltage levels lower than other circuits on the chip (memory), the device may power-up in an unknown state. To guarantee that the device starts up in a known state, it must contain a power-up reset circuit. PIC16C5X microcontrollers are equipped with on-chip Power-on Reset circuitry, which eliminates the need for external reset logic. This circuit will function in most power-up situations where  $V_{DD}$  rise time is fast enough (50 ms or less). This application note describes the typical power-up sequence for PIC16C5X microcontrollers. Methods of assuring reset on power-up and after a brown-out are discussed and simple, low-cost external solutions are discussed for power-up situations where the PIC16C5X's internal circuitry cannot provide the reset.

### POWER-UP SEQUENCE


The PIC16C5X incorporates complex Power-on Reset (POR) circuitry on-chip which provides a solid, reliable internal chip reset for most power-up situations. To use this feature, the user merely needs to tie the  $\overline{MCLR}$  pin to the  $V_{DD}$  pin. A simplified block diagram of the on-chip

reset circuitry is shown in Figure 1. On power-up, the reset latch and the start-up timer are reset to appropriate states by the Power-on Reset (POR). The start-up timer will begin counting once it detects  $\overline{MCLR}$  to be high (i.e., external chip reset goes inactive). After the time-out period, which is typically 18 ms long, the timer will reset the reset latch and thus end the on-chip reset signal.


Figure 3 and Figure 4 are two power-up situations with relative fast rise time on  $V_{DD}$ . In Figure 2,  $V_{DD}$  is stable when  $\overline{MCLR}$  is brought high (i.e., reset pulse is being provided by external source). The chip actually comes out of reset about  $T_{OST}$  ms after that, where  $T_{OST}$  = Time of the Oscillator Start-up Timer. (The timer is called Oscillator Start-up Timer because the time-out was incorporated primarily to allow the crystal oscillator to stabilize on power-up). In Figure 3, the  $\overline{MCLR}$  and  $V_{DD}$  are tied together and clearly the on-chip reset mechanism is being used.  $V_{DD}$  is stable before the start-up timer expires and there is no problem with proper reset.

In Figure 4, where the  $V_{DD}$  rise time is much greater than  $T_{OST}$  (typically 18 ms) this is clearly a potentially problematic situation. The POR pulse comes when  $V_{DD}$  is about 1.5V. Most CMOS logic, including the start-up timer, starts functioning between 1.5V to 2.0V. When the start-up timer times out, the chip reset is ended and the chip attempts to execute. If by this time  $V_{DD}$  has reached the  $V_{DD\ min.}$  value, then all circuits are guaranteed to function correctly and power-up reset is successful. If, however, the  $V_{DD}$  slope was too slow and had not reached  $V_{DD\ min.}$ , then the chip is not guaranteed to function properly.


**FIGURE 1: PIC16C5X INTERNAL RESET CIRCUIT**

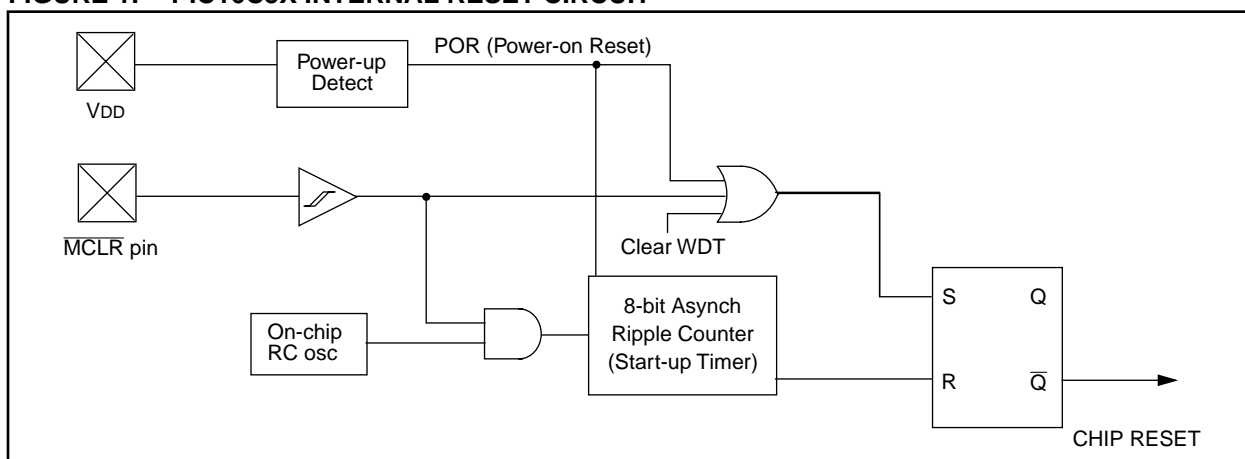


**FIGURE 2: EXTERNAL RESET PULSE**

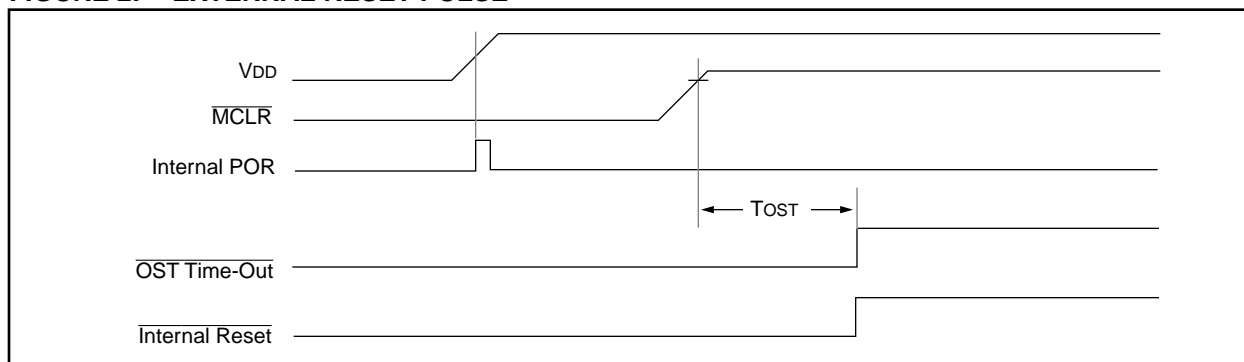

**FIGURE 3: INTERNAL RESET (VDD AND MCLR TIED TOGETHER)**

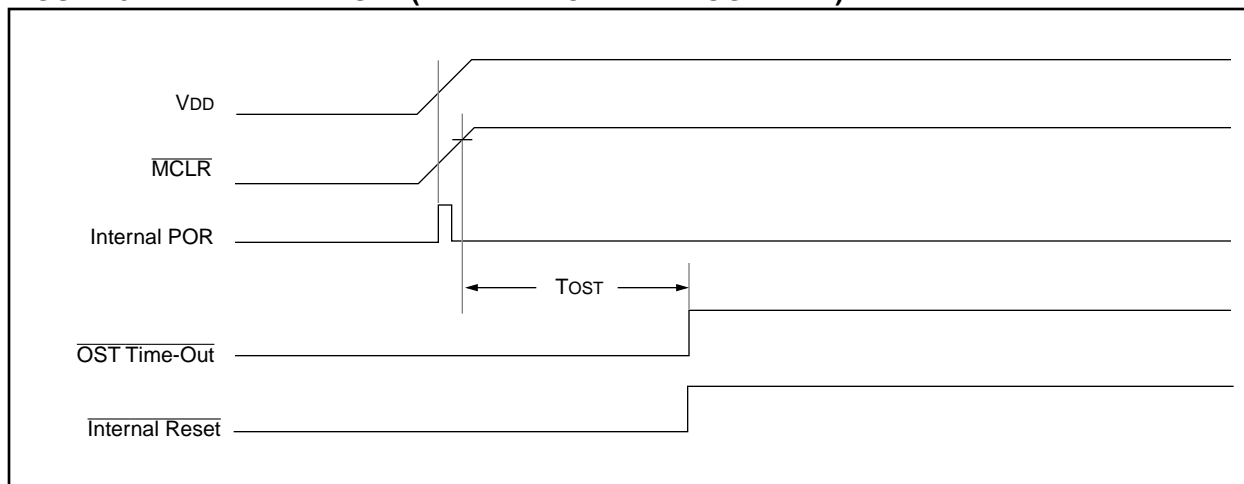


**FIGURE 4: INTERNAL RESET (VDD AND MCLR TIED TOGETHER): SLOW VDD RISE TIME**

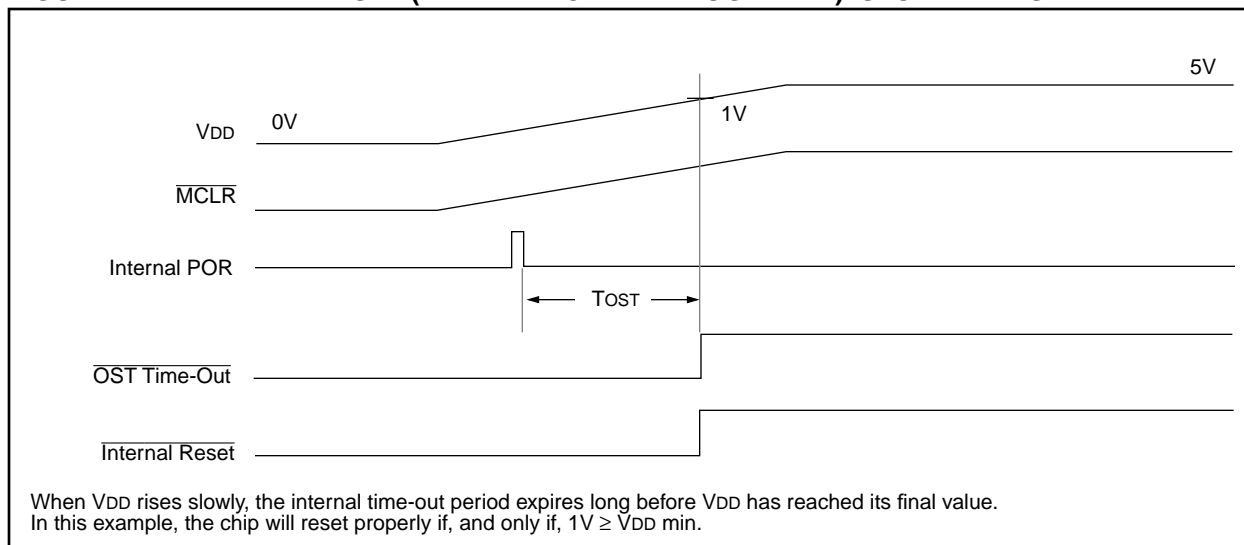

## EXTERNAL POWER-ON RESET CIRCUIT

To use power supplies with slow rise times it is necessary to use an external power-on reset circuit such as the one shown in Figure 5. This circuit uses an external RC to generate the reset pulse. The time constant of the RC should be long enough to guarantee that the reset pulse is still present until VDD has reached VDD min. R should be 40k or less to guarantee that MCLR will pull to within 0.2 volts of VDD (since the leakage spec on MCLR is  $\pm 5 \mu\text{A}$ , a resistor larger than 40k may cause input high voltage on this pin to be less than VDD – 0.2V, the required spec). The diode (D) is used to rapidly discharge the capacitor on power-down. This is very important as a power-up reset pulse is needed after a short power-down (less than the time constant of RC) or after a power spike. The resistor (R1) protects against a high current flowing into the MCLR pin from fully charged capacitor (C), in the event the MCLR pin breakdown is induced via ESD (electrostatic discharge) or EOS (electrical overstress). The circuit, however, does not protect against brown-out situations where power does not drop to zero, but merely dips below VDD min. In such a situation, voltage at the MCLR pin will not go low enough (i.e., below VIL) to guarantee a reset pulse. The following section presents an example circuit to protect against such brown-outs.

**FIGURE 5: EXTERNAL POWER-ON RESET CIRCUIT**

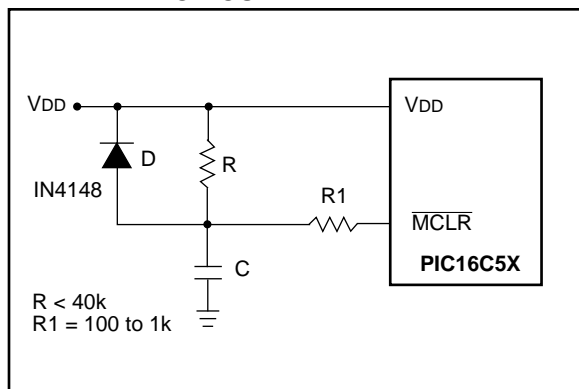


## BROWN-OUT PROTECTION

In many applications it is necessary to guarantee a reset pulse whenever VDD is less than VDD min. This can be accomplished using a brown-out protection circuit such as the one shown in Figure 6. This is a simple circuit that causes a reset pulse whenever VDD drops below the zener diode voltage plus the VBE

$$V_{BE} = V_{DD} \cdot R1 / (R1 + R2)$$


of Q1. A 3.3V zener will produce a reset pulse whenever VDD drops below about 4V. This circuit has a typical accuracy of about  $\pm 100 \text{ mV}$ .

**FIGURE 6: EXTERNAL BROWN-OUT PROTECTION CIRCUIT**

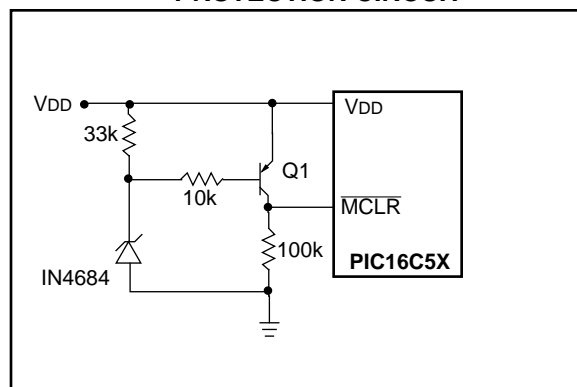

A less expensive, albeit less precise, brownout circuit is shown in Figure 7. Transistor Q1 turns off when VBE falls below 0.7V allowing R3 to pull down the MCLR input.

**FIGURE 7: EXTERNAL BROWN-OUT PROTECTION CIRCUIT**

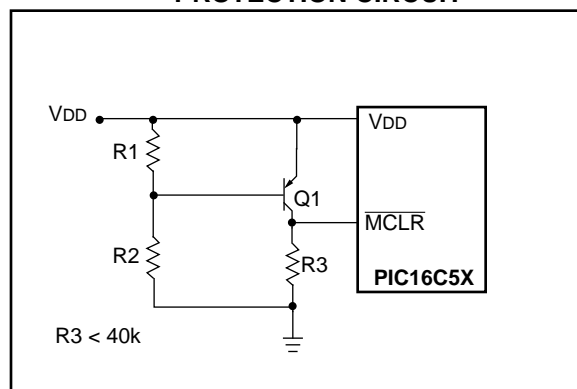

---

**Note the following details of the code protection feature on PICmicro® MCUs.**

- The PICmicro family meets the specifications contained in the Microchip Data Sheet.
- Microchip believes that its family of PICmicro microcontrollers is one of the most secure products of its kind on the market today, when used in the intended manner and under normal conditions.
- There are dishonest and possibly illegal methods used to breach the code protection feature. All of these methods, to our knowledge, require using the PICmicro microcontroller in a manner outside the operating specifications contained in the data sheet. The person doing so may be engaged in theft of intellectual property.
- Microchip is willing to work with the customer who is concerned about the integrity of their code.
- Neither Microchip nor any other semiconductor manufacturer can guarantee the security of their code. Code protection does not mean that we are guaranteeing the product as “unbreakable”.
- Code protection is constantly evolving. We at Microchip are committed to continuously improving the code protection features of our product.

If you have any further questions about this matter, please contact the local sales office nearest to you.

---

Information contained in this publication regarding device applications and the like is intended through suggestion only and may be superseded by updates. It is your responsibility to ensure that your application meets with your specifications. No representation or warranty is given and no liability is assumed by Microchip Technology Incorporated with respect to the accuracy or use of such information, or infringement of patents or other intellectual property rights arising from such use or otherwise. Use of Microchip's products as critical components in life support systems is not authorized except with express written approval by Microchip. No licenses are conveyed, implicitly or otherwise, under any intellectual property rights.

#### **Trademarks**


The Microchip name and logo, the Microchip logo, FilterLab, KEELOQ, microID, MPLAB, PIC, PICmicro, PICMASTER, PICSTART, PRO MATE, SEEVAL and The Embedded Control Solutions Company are registered trademarks of Microchip Technology Incorporated in the U.S.A. and other countries.


dsPIC, ECONOMONITOR, FanSense, FlexROM, fuzzyLAB, In-Circuit Serial Programming, ICSP, ICEPIC, microPort, Migratable Memory, MPASM, MPLIB, MPLINK, MPSIM, MXDEV, PICC, PICDEM, PICDEM.net, rPIC, Select Mode and Total Endurance are trademarks of Microchip Technology Incorporated in the U.S.A.

Serialized Quick Turn Programming (SQTP) is a service mark of Microchip Technology Incorporated in the U.S.A.

All other trademarks mentioned herein are property of their respective companies.

© 2002, Microchip Technology Incorporated, Printed in the U.S.A., All Rights Reserved.

 Printed on recycled paper.

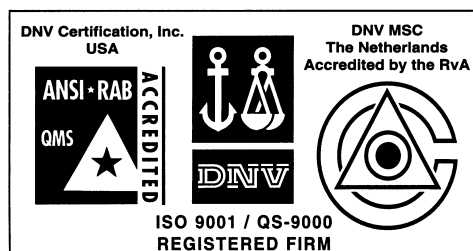

*Microchip received QS-9000 quality system certification for its worldwide headquarters, design and wafer fabrication facilities in Chandler and Tempe, Arizona in July 1999. The Company's quality system processes and procedures are QS-9000 compliant for its PICmicro® 8-bit MCUs, KEELOQ® code hopping devices, Serial EEPROMs and microperipheral products. In addition, Microchip's quality system for the design and manufacture of development systems is ISO 9001 certified.*



## WORLDWIDE SALES AND SERVICE

### AMERICAS

#### Corporate Office

2355 West Chandler Blvd.  
Chandler, AZ 85224-6199  
Tel: 480-792-7200 Fax: 480-792-7277  
Technical Support: 480-792-7627  
Web Address: <http://www.microchip.com>

#### Rocky Mountain

2355 West Chandler Blvd.  
Chandler, AZ 85224-6199  
Tel: 480-792-7966 Fax: 480-792-7456

#### Atlanta

500 Sugar Mill Road, Suite 200B  
Atlanta, GA 30350  
Tel: 770-640-0034 Fax: 770-640-0307

#### Boston

2 Lan Drive, Suite 120  
Westford, MA 01886  
Tel: 978-692-3848 Fax: 978-692-3821

#### Chicago

333 Pierce Road, Suite 180  
Itasca, IL 60143  
Tel: 630-285-0071 Fax: 630-285-0075

#### Dallas

4570 Westgrove Drive, Suite 160  
Addison, TX 75001  
Tel: 972-818-7423 Fax: 972-818-2924

#### Detroit

Tri-Atria Office Building  
32255 Northwestern Highway, Suite 190  
Farmington Hills, MI 48334  
Tel: 248-538-2250 Fax: 248-538-2260

#### Kokomo

2767 S. Albright Road  
Kokomo, Indiana 46902  
Tel: 765-864-8360 Fax: 765-864-8387

#### Los Angeles

18201 Von Karman, Suite 1090  
Irvine, CA 92612  
Tel: 949-263-1888 Fax: 949-263-1338

#### New York

150 Motor Parkway, Suite 202  
Hauppauge, NY 11788  
Tel: 631-273-5305 Fax: 631-273-5335

#### San Jose

Microchip Technology Inc.  
2107 North First Street, Suite 590  
San Jose, CA 95131  
Tel: 408-436-7950 Fax: 408-436-7955

#### Toronto

6285 Northam Drive, Suite 108  
Mississauga, Ontario L4V 1X5, Canada  
Tel: 905-673-0699 Fax: 905-673-6509

### ASIA/PACIFIC

#### Australia

Microchip Technology Australia Pty Ltd  
Suite 22, 41 Rawson Street  
Epping 2121, NSW  
Australia  
Tel: 61-2-9868-6733 Fax: 61-2-9868-6755

#### China - Beijing

Microchip Technology Consulting (Shanghai)  
Co., Ltd., Beijing Liaison Office  
Unit 915  
Bei Hai Wan Tai Bldg.  
No. 6 Chaoyangmen Beidajie  
Beijing, 100027, No. China  
Tel: 86-10-85282100 Fax: 86-10-85282104

#### China - Chengdu

Microchip Technology Consulting (Shanghai)  
Co., Ltd., Chengdu Liaison Office  
Rm. 2401, 24th Floor,  
Ming Xing Financial Tower  
No. 88 TIDU Street  
Chengdu 610016, China  
Tel: 86-28-6766200 Fax: 86-28-6766599

#### China - Fuzhou

Microchip Technology Consulting (Shanghai)  
Co., Ltd., Fuzhou Liaison Office  
Unit 28F, World Trade Plaza  
No. 71 Wusi Road  
Fuzhou 350001, China  
Tel: 86-591-7503506 Fax: 86-591-7503521

#### China - Shanghai

Microchip Technology Consulting (Shanghai)  
Co., Ltd.  
Room 701, Bldg. B  
Far East International Plaza  
No. 317 Xian Xia Road  
Shanghai, 200051  
Tel: 86-21-6275-5700 Fax: 86-21-6275-5060

#### China - Shenzhen

Microchip Technology Consulting (Shanghai)  
Co., Ltd., Shenzhen Liaison Office  
Rm. 1315, 13/F, Shenzhen Kerry Centre,  
Renminnan Lu  
Shenzhen 518001, China  
Tel: 86-755-2350361 Fax: 86-755-2366086

#### Hong Kong

Microchip Technology Hongkong Ltd.  
Unit 901-6, Tower 2, Metroplaza  
223 Hing Fong Road  
Kwai Fong, N.T., Hong Kong  
Tel: 852-2401-1200 Fax: 852-2401-3431

#### India

Microchip Technology Inc.  
India Liaison Office  
Divyasree Chambers  
1 Floor, Wing A (A3/A4)  
No. 11, O'Shaugnessey Road  
Bangalore, 560 025, India  
Tel: 91-80-2290061 Fax: 91-80-2290062

### Japan

Microchip Technology Japan K.K.  
Benex S-1 6F  
3-18-20, Shinyokohama  
Kohoku-Ku, Yokohama-shi  
Kanagawa, 222-0033, Japan  
Tel: 81-45-471- 6166 Fax: 81-45-471-6122

### Korea

Microchip Technology Korea  
168-1, Youngbo Bldg. 3 Floor  
Samsung-Dong, Kangnam-Ku  
Seoul, Korea 135-882  
Tel: 82-2-554-7200 Fax: 82-2-558-5934

### Singapore

Microchip Technology Singapore Pte Ltd.  
200 Middle Road  
#07-02 Prime Centre  
Singapore, 188980  
Tel: 65-6334-8870 Fax: 65-6334-8850

### Taiwan

Microchip Technology Taiwan  
11F-3, No. 207  
Tung Hua North Road  
Taipei, 105, Taiwan  
Tel: 886-2-2717-7175 Fax: 886-2-2545-0139

### EUROPE

#### Denmark

Microchip Technology Nordic ApS  
Regus Business Centre  
Lautrup høj 1-3  
Ballerup DK-2750 Denmark  
Tel: 45 4420 9895 Fax: 45 4420 9910

#### France

Microchip Technology SARL  
Parc d'Activite du Moulin de Massy  
43 Rue du Saule Trapu  
Batiment A - 1er Etage  
91300 Massy, France  
Tel: 33-1-69-53-63-20 Fax: 33-1-69-30-90-79

#### Germany

Microchip Technology GmbH  
Gustav-Heinemann Ring 125  
D-81739 Munich, Germany  
Tel: 49-89-627-144 0 Fax: 49-89-627-144-44

#### Italy

Microchip Technology SRL  
Centro Direzionale Colleoni  
Palazzo Taurus 1 V. Le Colleoni 1  
20041 Agrate Brianza  
Milan, Italy  
Tel: 39-039-65791-1 Fax: 39-039-6899883

#### United Kingdom

Arizona Microchip Technology Ltd.  
505 Eskdale Road  
Winnersh Triangle  
Wokingham  
Berkshire, England RG41 5TU  
Tel: 44 118 921 5869 Fax: 44-118 921-5820

03/01/02