

## DC Performance Comparisons of CMOS vs. Bipolar LDOs when Operating in "Dropout" ( $V_{IN} = \text{Nominal } V_{OUT}$ ) Mode

Author: Patrick Maresca,  
Microchip Technology, Inc.

### INTRODUCTION

More and more, battery operated systems are requiring lower terminal voltages to power internal circuits. Multi-cell designs are rapidly migrating to single-cell architectures to reduce system cost. A prime example of this system type is digital cameras, which often use a single-cell 3.6V Li-Ion battery for their power source. Digital cameras contain high-speed memory ICs, which require tight voltage regulation at moderate loads to meet the required timing parameters of the system. Precision low dropout (LDO) regulator devices can be used to meet these requirements but in doing so, the LDO regulators must be able to successfully operate in the 'dropout' mode as the battery discharges. Dropout mode is entered when the input voltage (from the battery source) is equal to the "nominal output voltage" of the LDO; for example a 3.3V LDO enters dropout mode when its input voltage at the  $V_{IN}$  pin is equal to 3.3V. Minimal output voltage droop and minimal LDO power dissipation are critical to meeting various system performance parameters and extending the life of the battery.

This application note compares the performance of Microchip Technology's TC1015 CMOS family of LDOs to two of its bipolar counterparts, the National Semiconductor LP2981 and the Micrel MIC5205. Dropout measurements were taken on three different popular output voltage options (5.0V, 3.3V, and 3.0V) under varying load conditions ranging from 10mA to 150mA. All measurements were made at ambient temperature ( $T_A = +25^\circ\text{C}$ ).

### BACKGROUND INFORMATION: CMOS vs. BIPOLAR ARCHITECTURE

Figures 1A and 1B compare the block diagram for a common bipolar regulator with that of an equivalent regulator fabricated in CMOS. The supply current to the bipolar device is composed of the bias current, plus a "ground current" ( $I_{GND}$ ) component shown in Figure 1A, which is a fraction of the output current (determined by the  $h_{FE}$  of the pass transistor) sunk through the output stage of the error amplifier. The "ground current" component of the CMOS regulator shown in Figure 1B is virtually zero, due to the extremely large drain-to-gate impedance of the CMOS pass transistor.

### TEST CIRCUIT

The circuit shown in Figure 2 was used to measure output voltage droop and device ground current with loads ranging from 10mA to 100mA (in 10mA increments), 125mA, and 150mA. Both the TC1015 and the MIC5205 have optional reference bypass capacitor connections from pin four to ground. Measurements were made with and without a 470pF bypass capacitor on both of these devices but the output voltage droop and ground current did not vary much with the bypass capacitor connected (only the data taken without a bypass capacitor is shown in this application note).

### TEST RESULTS

Tables I, II, and III show the performance of the TC1015, LP2981, and MIC5205 for dropout mode operation. Table I contains the data taken for 5.0V LDOs, Table II contains the data taken for 3.3V LDOs, and Table III contains the data taken for 3V LDOs. Notice that in each case, the ground current and power dissipation for the

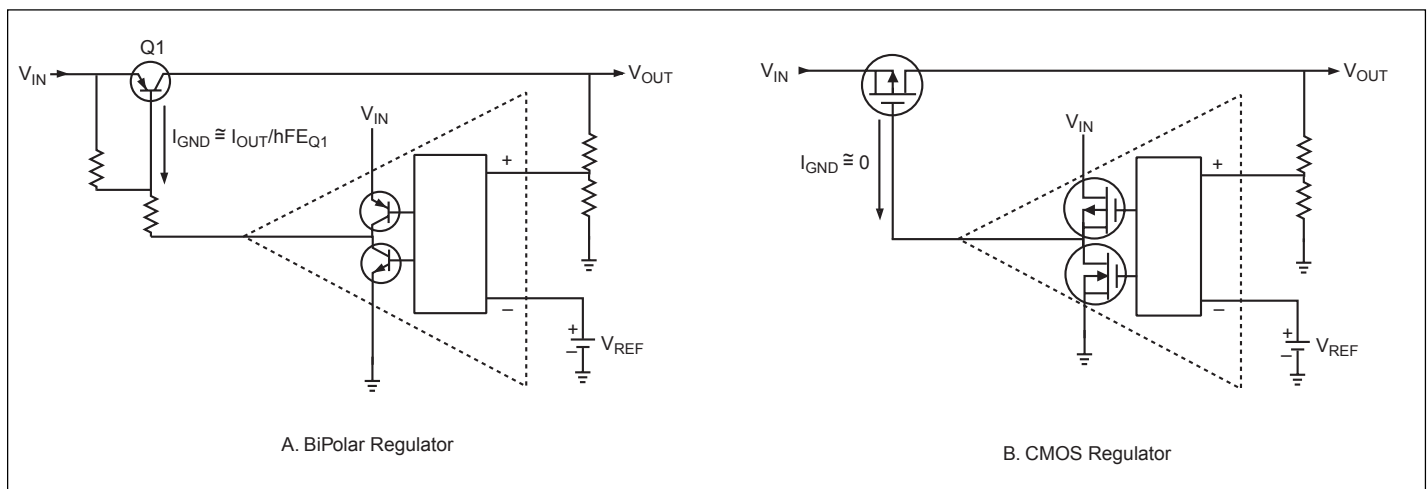


FIGURE 1: Bipolar vs. CMOS LDO regulator schematics.

# AN776

TC1015 CMOS devices is several orders of magnitude better than the bipolar LP2981/MIC5205 devices. The TC1015 has a slightly better output voltage droop in dropout mode than the LP2981 for all load currents and has slightly better droop performance than the MIC5205 for load currents up to 60mA. The TC1015 has similar droop performance compared to the MIC5205 for load currents between 70mA and 100mA and slightly poorer droop performance for load currents greater than 100mA. However, the extremely high power dissipation of the MIC5205 makes it a hazardous liability in systems where extending battery life is critical. The CMOS architecture of the TC1015 family tends to be the best fit for these types of battery powered applications requiring regulators to operate in the dropout mode.

## SUMMARY

In battery powered systems requiring lower terminal voltages (such as digital cameras), LDO regulators must often operate in the 'dropout' mode to enhance battery life. The TC1015 series of CMOS LDOs provide superior performance to bipolar LDOs in minimizing device power dissipation (through lower ground currents) when operating in the dropout mode. The TC1015 series has equivalent if not superior performance to bipolar LDOs in minimizing output voltage droop (under most load conditions) when operating in dropout.

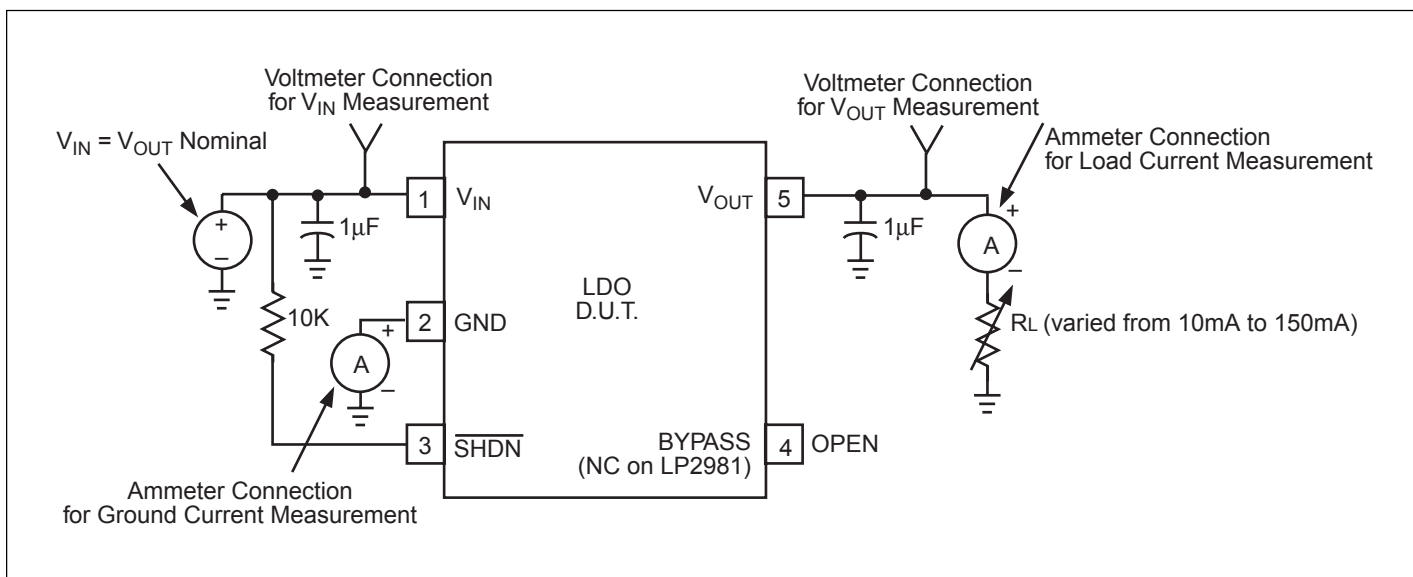


FIGURE 2: Dropout mode test circuit.

Test Conditions				Microchip TC1015-5.0VCT				NSCLP2981AIM5-5.0				Micrel MIC5205-5.0BM5			
V <sub>IN</sub> (V)	C <sub>IN</sub> (μF)	C <sub>OUT</sub> (μF)	Load Current (mA)	V <sub>OUT</sub> (V)	V <sub>OUT</sub> Droop (mV)	Ground Current (μA)	*Device Power Dissipation (mW)	V <sub>OUT</sub> (V)	V <sub>OUT</sub> Droop (mV)	Ground Current (μA)	*Device Power Dissipation (mW)	V <sub>OUT</sub> (V)	V <sub>OUT</sub> Droop (mV)	Ground Current (μA)	*Device Power Dissipation (mW)
5.0	1.0	1.0	10	4.98	20	57.4	0.287	4.96	40	439	2.20	4.96	40	790	3.95
5.0	1.0	1.0	20	4.96	40	58.3	0.292	4.94	60	569	2.85	4.93	70	878	4.39
5.0	1.0	1.0	30	4.94	60	59.1	0.296	4.92	80	687	3.44	4.92	80	966	4.83
5.0	1.0	1.0	40	4.93	70	59.9	0.299	4.90	100	808	4.04	4.91	90	1082	5.41
5.0	1.0	1.0	50	4.91	90	60.6	0.303	4.88	120	933	4.66	4.89	110	1213	6.07
5.0	1.0	1.0	60	4.89	110	61.4	0.307	4.87	130	1054	5.27	4.88	120	1358	6.79
5.0	1.0	1.0	70	4.88	120	62.1	0.310	4.85	150	1188	5.94	4.87	130	1517	7.59
5.0	1.0	1.0	80	4.86	140	62.8	0.314	4.83	170	1318	6.59	4.87	130	1695	8.47
5.0	1.0	1.0	90	4.85	150	63.3	0.317	4.81	190	1455	7.27	4.86	140	1874	9.37
5.0	1.0	1.0	100	4.83	170	64.0	0.320	4.79	210	1598	7.99	4.85	150	2058	10.29
5.0	1.0	1.0	125	4.78	220	65.3	0.327	4.75	250	1961	9.80	4.83	170	2546	12.73
5.0	1.0	1.0	150	4.73	270	66.6	0.333	4.70	300	2298	11.49	4.81	190	3087	15.43

Notes: \* Does not include power dissipated in pass element.  
No reference bypass capacitors were used when measuring TC1015 and MIC5205.

**TABLE 1:** 5.0V LDO data in device dropout mode ( $V_{IN}$  = nominal  $V_{OUT}$ ).

Test Conditions				Microchip TC1015-3.3VCT				NSCLP2981AIM5-3.3				Micrel MIC5205-3.3BM5			
V <sub>IN</sub> (V)	C <sub>IN</sub> (μF)	C <sub>OUT</sub> (μF)	Load Current (mA)	V <sub>OUT</sub> (V)	V <sub>OUT</sub> Droop (mV)	Ground Current (μA)	*Device Power Dissipation (mW)	V <sub>OUT</sub> (V)	V <sub>OUT</sub> Droop (mV)	Ground Current (μA)	*Device Power Dissipation (mW)	V <sub>OUT</sub> (V)	V <sub>OUT</sub> Droop (mV)	Ground Current (μA)	*Device Power Dissipation (mW)
3.3	1.0	1.0	10	3.28	20	58.5	0.193	3.27	30	467	1.54	3.27	30	1166	3.85
3.3	1.0	1.0	20	3.27	30	59.6	0.197	3.24	60	582	1.92	3.25	50	1264	4.17
3.3	1.0	1.0	30	3.25	50	60.4	0.199	3.22	80	693	2.29	3.23	70	1376	4.54
3.3	1.0	1.0	40	3.24	60	61.2	0.202	3.21	90	799	2.63	3.22	80	1497	4.94
3.3	1.0	1.0	50	3.22	80	61.8	0.204	3.19	110	917	3.03	3.21	90	1621	5.35
3.3	1.0	1.0	60	3.21	90	62.3	0.206	3.17	130	1050	3.47	3.20	100	1770	5.84
3.3	1.0	1.0	70	3.19	110	62.9	0.208	3.15	150	1173	3.87	3.19	110	1932	6.38
3.3	1.0	1.0	80	3.17	130	63.4	0.209	3.13	170	1304	4.30	3.18	120	2085	6.88
3.3	1.0	1.0	90	3.16	140	64.7	0.213	3.12	180	1452	4.79	3.18	120	2247	7.41
3.3	1.0	1.0	100	3.14	160	65.0	0.215	3.10	200	1597	5.27	3.17	130	2411	7.96
3.3	1.0	1.0	125	3.09	210	65.5	0.216	3.05	250	1955	6.45	3.15	150	2856	9.42
3.3	1.0	1.0	150	3.04	260	66.2	0.219	3.00	300	2293	7.57	3.13	170	3337	11.01

Notes: \* Does not include power dissipated in pass element.  
No reference bypass capacitors were used when measuring TC1015 and MIC5205.

**TABLE 2:** 3.3V LDO data in device dropout mode ( $V_{IN}$  = nominal  $V_{OUT}$ ).

# AN776

Test Conditions				Microchip TC1015-3.0VCT				NSCLP2981AIM5-3.0				Micrel MIC5205-3.0BM5			
V <sub>IN</sub> (V)	C <sub>IN</sub> (μF)	C <sub>OUT</sub> (μF)	Load Current (mA)	V <sub>OUT</sub> (V)	V <sub>OUT</sub> Droop (mV)	Ground Current (μA)	*Device Power Dissipation (mW)	V <sub>OUT</sub> (V)	V <sub>OUT</sub> Droop (mV)	Ground Current (μA)	*Device Power Dissipation (mW)	V <sub>OUT</sub> (V)	V <sub>OUT</sub> Droop (mV)	Ground Current (μA)	*Device Power Dissipation (mW)
3.0	1.0	1.0	10	2.98	20	60.7	0.182	2.97	30	572	1.72	2.94	60	536	1.61
3.0	1.0	1.0	20	2.97	30	61.5	0.185	2.95	50	685	2.06	2.92	80	619	1.86
3.0	1.0	1.0	30	2.95	50	62.2	0.187	2.93	70	793	2.38	2.90	100	724	2.17
3.0	1.0	1.0	40	2.94	60	62.8	0.189	2.91	90	903	2.71	2.89	110	845	2.53
3.0	1.0	1.0	50	2.92	80	63.4	0.190	2.90	100	1015	3.05	2.88	120	977	2.93
3.0	1.0	1.0	60	2.91	90	63.9	0.192	2.88	120	1137	3.41	2.87	130	1126	3.38
3.0	1.0	1.0	70	2.89	110	65.2	0.196	2.86	140	1253	3.76	2.86	140	1282	3.85
3.0	1.0	1.0	80	2.87	130	65.4	0.196	2.85	150	1379	4.14	2.85	150	1446	4.34
3.0	1.0	1.0	90	2.86	140	65.5	0.196	2.83	170	1504	4.51	2.84	160	1638	4.91
3.0	1.0	1.0	100	2.84	160	65.5	0.197	2.81	190	1639	4.92	2.83	170	1818	5.45
3.0	1.0	1.0	125	2.80	200	65.7	0.197	2.77	230	1969	5.91	2.81	190	2323	6.97
3.0	1.0	1.0	150	2.75	250	66.2	0.198	2.73	270	2251	6.75	2.79	210	2884	8.65

Notes: \* Does not include power dissipated in pass element.

No reference bypass capacitors were used when measuring TC1015 and MIC5205.

**TABLE 3:** 3.0V LDO data in device dropout mode ( $V_{IN}$  = nominal  $V_{OUT}$ ).

---

Information contained in this publication regarding device applications and the like is intended through suggestion only and may be superseded by updates. It is your responsibility to ensure that your application meets with your specifications. No representation or warranty is given and no liability is assumed by Microchip Technology Incorporated with respect to the accuracy or use of such information, or infringement of patents or other intellectual property rights arising from such use or otherwise. Use of Microchip's products as critical components in life support systems is not authorized except with express written approval by Microchip. No licenses are conveyed, implicitly or otherwise, under any intellectual property rights.

#### Trademarks


The Microchip name and logo, the Microchip logo, FilterLab, KEELOQ, microID, MPLAB, PIC, PICmicro, PICMASTER, PICSTART, PRO MATE, SEEVAL and The Embedded Control Solutions Company are registered trademarks of Microchip Technology Incorporated in the U.S.A. and other countries.


dsPIC, ECONOMONITOR, FanSense, FlexROM, fuzzyLAB, In-Circuit Serial Programming, ICSP, ICEPIC, microPort, Migratable Memory, MPASM, MPLIB, MPLINK, MPSIM, MXDEV, PICC, PICDEM, PICDEM.net, rfPIC, Select Mode and Total Endurance are trademarks of Microchip Technology Incorporated in the U.S.A.

Serialized Quick Turn Programming (SQTP) is a service mark of Microchip Technology Incorporated in the U.S.A.

All other trademarks mentioned herein are property of their respective companies.

© 2002, Microchip Technology Incorporated, Printed in the U.S.A., All Rights Reserved.

 Printed on recycled paper.

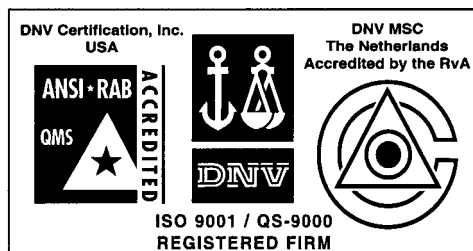

*Microchip received QS-9000 quality system certification for its worldwide headquarters, design and wafer fabrication facilities in Chandler and Tempe, Arizona in July 1999. The Company's quality system processes and procedures are QS-9000 compliant for its PICmicro® 8-bit MCUs, KEELOQ® code hopping devices, Serial EEPROMs and microperipheral products. In addition, Microchip's quality system for the design and manufacture of development systems is ISO 9001 certified.*



# MICROCHIP

## WORLDWIDE SALES AND SERVICE

### AMERICAS

#### Corporate Office

2355 West Chandler Blvd.  
Chandler, AZ 85224-6199  
Tel: 480-792-7200 Fax: 480-792-7277  
Technical Support: 480-792-7627  
Web Address: <http://www.microchip.com>

#### Rocky Mountain

2355 West Chandler Blvd.  
Chandler, AZ 85224-6199  
Tel: 480-692-7966 Fax: 480-792-7456

#### Atlanta

500 Sugar Mill Road, Suite 200B  
Atlanta, GA 30350  
Tel: 770-640-0034 Fax: 770-640-0307

#### Boston

2 Lan Drive, Suite 120  
Westford, MA 01886  
Tel: 978-692-3848 Fax: 978-692-3821

#### Chicago

333 Pierce Road, Suite 180  
Itasca, IL 60143  
Tel: 630-285-0071 Fax: 630-285-0075

#### Dallas

4570 Westgrove Drive, Suite 160  
Addison, TX 75001  
Tel: 972-818-7423 Fax: 972-818-2924

#### Detroit

Tri-Atria Office Building  
32255 Northwestern Highway, Suite 190  
Farmington Hills, MI 48334  
Tel: 248-538-2250 Fax: 248-538-2260

#### Kokomo

2767 S. Albright Road  
Kokomo, Indiana 46902  
Tel: 765-864-8360 Fax: 765-864-8387

#### Los Angeles

18201 Von Karman, Suite 1090  
Irvine, CA 92612  
Tel: 949-263-1888 Fax: 949-263-1338

#### New York

150 Motor Parkway, Suite 202  
Hauppauge, NY 11788  
Tel: 631-273-5305 Fax: 631-273-5335

#### San Jose

Microchip Technology Inc.  
2107 North First Street, Suite 590  
San Jose, CA 95131  
Tel: 408-436-7950 Fax: 408-436-7955

#### Toronto

6285 Northam Drive, Suite 108  
Mississauga, Ontario L4V 1X5, Canada  
Tel: 905-673-0699 Fax: 905-673-6509

### ASIA/PACIFIC

#### Australia

Microchip Technology Australia Pty Ltd  
Suite 22, 41 Rawson Street  
Epping 2121, NSW  
Australia  
Tel: 61-2-9868-6733 Fax: 61-2-9868-6755

#### China - Beijing

Microchip Technology Consulting (Shanghai)  
Co., Ltd., Beijing Liaison Office  
Unit 915  
Bei Hai Wan Tai Bldg.  
No. 6 Chaoyangmen Beidajie  
Beijing, 100027, No. China  
Tel: 86-10-85282100 Fax: 86-10-85282104

#### China - Chengdu

Microchip Technology Consulting (Shanghai)  
Co., Ltd., Chengdu Liaison Office  
Rm. 2401, 24th Floor,  
Ming Xing Financial Tower  
No. 88 TIDU Street  
Chengdu 610016, China  
Tel: 86-28-6766200 Fax: 86-28-6766599

#### China - Fuzhou

Microchip Technology Consulting (Shanghai)  
Co., Ltd., Fuzhou Liaison Office  
Unit 28F, World Trade Plaza  
No. 71 Wusi Road  
Fuzhou 350001, China  
Tel: 86-591-7503506 Fax: 86-591-7503521

#### China - Shanghai

Microchip Technology Consulting (Shanghai)  
Co., Ltd.  
Room 701, Bldg. B  
Far East International Plaza  
No. 317 Xian Xia Road  
Shanghai, 200051  
Tel: 86-21-6275-5700 Fax: 86-21-6275-5060

#### China - Shenzhen

Microchip Technology Consulting (Shanghai)  
Co., Ltd., Shenzhen Liaison Office  
Rm. 1315, 13/F, Shenzhen Kerry Centre,  
Renminnan Lu  
Shenzhen 518001, China  
Tel: 86-755-2350361 Fax: 86-755-2366086

#### Hong Kong

Microchip Technology Hongkong Ltd.  
Unit 901-6, Tower 2, Metroplaza  
223 Hing Fong Road  
Kwai Fong, N.T., Hong Kong  
Tel: 852-2401-1200 Fax: 852-2401-3431

#### India

Microchip Technology Inc.  
India Liaison Office  
Divyasree Chambers  
1 Floor, Wing A (A3/A4)  
No. 11, O'Shaughnessey Road  
Bangalore, 560 025, India  
Tel: 91-80-2290061 Fax: 91-80-2290062

### Japan

Microchip Technology Japan K.K.  
Benex S-1 6F  
3-18-20, Shinyokohama  
Kohoku-Ku, Yokohama-shi  
Kanagawa, 222-0033, Japan  
Tel: 81-45-471-6166 Fax: 81-45-471-6122

### Korea

Microchip Technology Korea  
168-1, Youngbo Bldg. 3 Floor  
Samsung-Dong, Kangnam-Ku  
Seoul, Korea 135-882  
Tel: 82-2-554-7200 Fax: 82-2-558-5934

### Singapore

Microchip Technology Singapore Pte Ltd.  
200 Middle Road  
#07-02 Prime Centre  
Singapore, 188980  
Tel: 65-6334-8870 Fax: 65-6334-8850

### Taiwan

Microchip Technology Taiwan  
11F-3, No. 207  
Tung Hua North Road  
Taipei, 105, Taiwan  
Tel: 886-2-2717-7175 Fax: 886-2-2545-0139

### EUROPE

#### Denmark

Microchip Technology Nordic ApS  
Regus Business Centre  
Lautrup høj 1-3  
Ballerup DK-2750 Denmark  
Tel: 45 4420 9895 Fax: 45 4420 9910

#### France

Microchip Technology SARL  
Parc d'Activite du Moulin de Massy  
43 Rue du Saule Trapu  
Batiment A - 1er Etage  
91300 Massy, France  
Tel: 33-1-69-53-63-20 Fax: 33-1-69-30-90-79

#### Germany

Microchip Technology GmbH  
Gustav-Heinemann Ring 125  
D-81739 Munich, Germany  
Tel: 49-89-627-144 0 Fax: 49-89-627-144-44

#### Italy

Microchip Technology SRL  
Centro Direzionale Colleoni  
Palazzo Taurus 1 V. Le Colleoni 1  
20041 Agrate Brianza  
Milan, Italy  
Tel: 39-039-65791-1 Fax: 39-039-6899883

#### United Kingdom

Arizona Microchip Technology Ltd.  
505 Eskdale Road  
Winnersh Triangle  
Wokingham  
Berkshire, England RG41 5TU  
Tel: 44 118 921 5869 Fax: 44-118 921-5820

03/01/02

