

Numerical-Integration Techniques Speed Dual-Slope A/D Conversion

Author: Gary Grandbois and Wes Freeman,
Microchip Technology, Inc.

INTRODUCTION

By using low-cost microprocessors and a program-controlled numerical-integration technique, you can achieve good noise rejection and take full advantage of the higher speeds offered by recently developed dual-slope A/D converters such as the TC7109.

This and similar converters overcome the speed limitations imposed by logic-gate and analog comparator delays in earlier dual-slope devices, and the modern units can operate at rates as high as 30 to 100 samples/sec. Nevertheless, operating them at their maximum conversion rates often makes it difficult or impossible to achieve the high normal-mode line-frequency rejection that dual-slope A/D converters inherently offer at slower conversion rates. Thus, noise considerations have often precluded use of these converters at their rated speeds — especially in industrial environments, where line-frequency and other low-frequency noise components can be a particular problem.

NORMAL-MODE LINE-FREQUENCY REJECTION

To understand normal-mode line-frequency rejection in dual-slope A/D converters, consider a typical 12-bit converter (Figure 1a) and its timing diagram (Figure 1b) for one conversion cycle. Note that the conversion depends on charging the integrating capacitor during a fixed time interval; the number of counts necessary to discharge the capacitor to zero is proportional to the input voltage.

The integrating A/D converter integrates the signal only in a certain time window, as Figure 1b shows. This limited integration period results in normal-mode noise rejection only when the integration period is equal to one or more periods of the noise signal (Figure 2a). The time integral of this noise over integer multiples of the noise period is, of course, zero.

Normal-mode noise-rejection performance can thus be represented as a function (Figure 2b) that reaches peaks at the fundamental and harmonic frequencies of the period defined by the signal-integrate time T . The minimum period T , which must equal the noise period, has been the limiting factor for conversion speed. At 60Hz, for example, the minimum signal-integrate time is 16.7msec; at 50Hz, it's 20msec.

Because the signal-integrate time is only a portion of the total conversion time, conversion rates are significantly less than $1/T$. A standard, high-performance, dual-slope A/D converter includes a reference deintegrate phase, typically $2T$ long, and an autozero period equal to the signal-integrate period T . The total conversion time is thus $4T$, which, for 60Hz rejection, yields a maximum conversion rate of 15 samples/sec; for 50Hz, it yields 12.5 samples/sec.

The most serious constraint arises when you want to offer an instrument for international use that can reject both 60 and 50Hz. This feature is attainable only when the signal-integrate period T can contain six cycles of 60Hz noise and five cycles of 50Hz noise. The resulting 100msec signal-integrate period dictates a 2.5 conversion/sec rate.

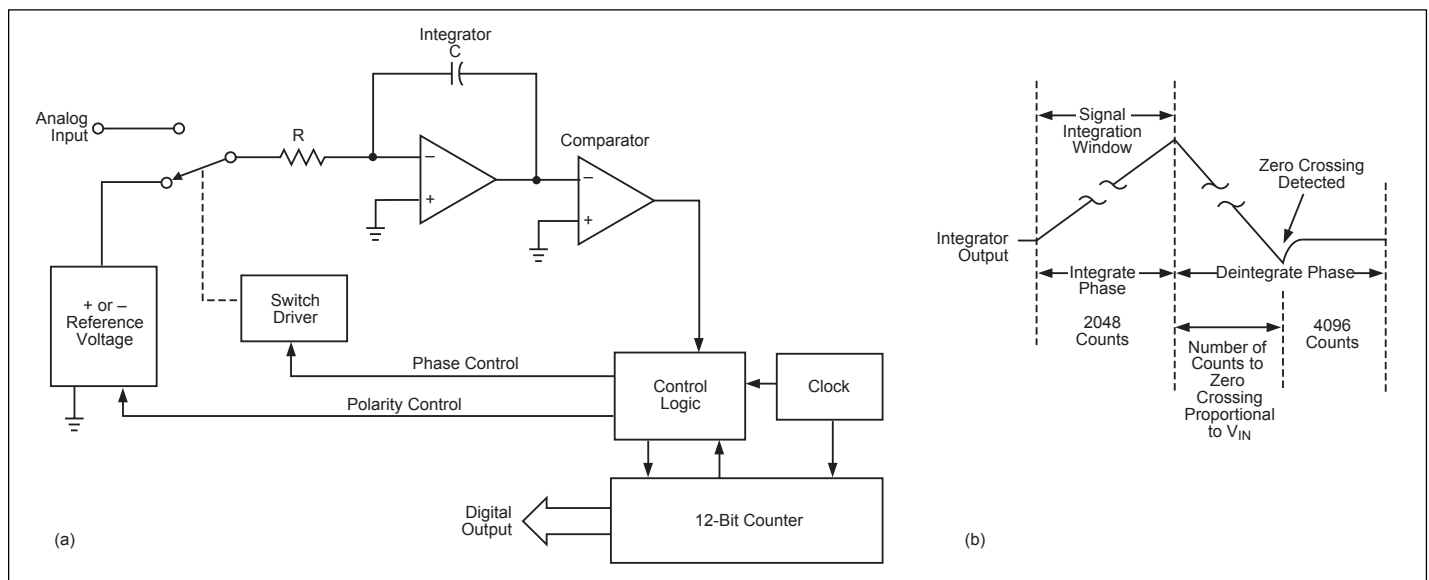


FIGURE 1: A dual-slope A/D converter operates by charging a capacitor from the input voltage during a fixed time, then discharging it to zero. The number of clock periods in the discharge time corresponds to the analog input voltage. The size of the integrating time window determines which normal-mode noise signals are rejected.

AN788

You can, however, overcome the inherent conversion-speed limitation of integrating A/D converters. A microprocessor with program-controlled numerical integration that complements the A/D converter's analog integration will speed dual-slope conversion considerably.

You can achieve high normal-mode rejection for specific frequencies with this method if three conditions are met. First, the signal-integrate period must be defined such that noise integration takes place on a segmented basis. In Figure 3a, for example, the integrate window opens on a noise-wave-form segment that's one-third of a period long.

Next, the second signal-integrate period must be at a point corresponding exactly to the point at which the first one ended, and the third's beginning must correspond to the point at which the second ended. This condition can be met only if the A/D converter has a fixed conversion time, irrespective of the signal input. Finally, the microprocessor must sum all three conversions to achieve the total integration of a cycle of noise. A consideration of all these constraints for the TC7109 A/D converter, for example, leads to the relationship:

$$f_{\text{NOISE}} = \frac{1}{XT} = \frac{4C}{X}$$

where C is the conversion rate, f the noise frequency and X the number of conversion results added. X must be an odd number; Figure 3b shows why X cannot be an even number. A frequency that would require an even number of samples is one at which the integrate window is locked in phase with the signal (i.e., the converter and signal periods are synchronized). For $CV = (f_{\text{NOISE}})(X/4)$ and $X=2$ (as in Figure 3b), the result is two times the error of one conversion.

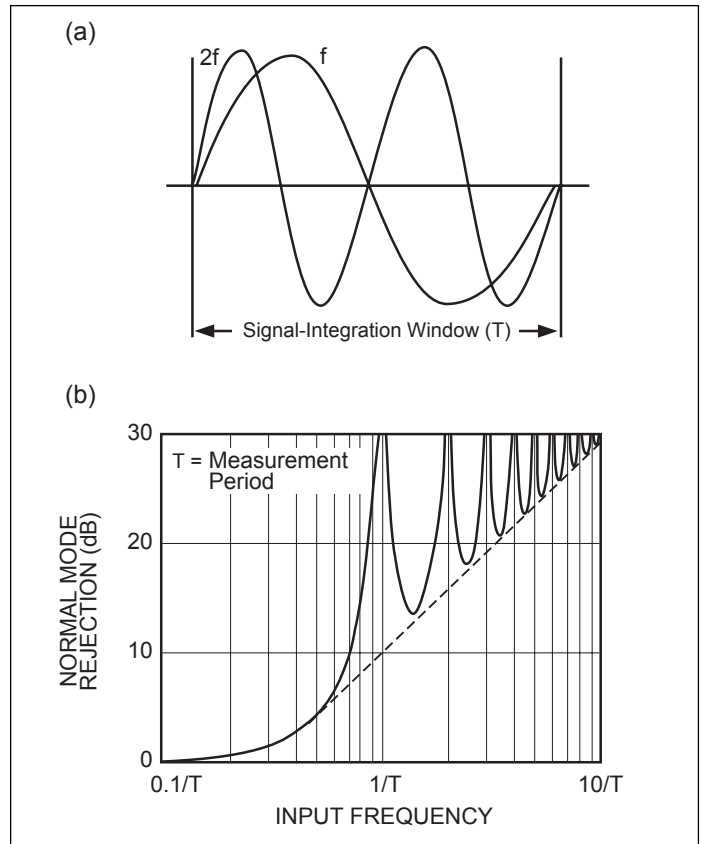


FIGURE 2: In a dual-slope A/D converter, high normal-mode noise rejection occurs when the integration period is a multiple of the noise signal's period.

 


FIGURE 3: Data-conversion systems employing a numerical-integration technique furnish noise rejection when an odd number of samples are summed (a). Adding the results of two conversions, though, can yield twice as much error as does one conversion (b) if the A/D converter and noise frequency are synchronized.

 


FIGURE 4: The normal-mode-rejection capability illustrated by the upper curve here demonstrates the effectiveness of taking nine conversion samples; the system that the curve represents rejects noise at all multiples of 10Hz. The lower curve shows the result of acquiring only one sample and employing an 11.11msec signal-integration period.

To achieve the desired normal-mode rejection, you must, therefore, sum an odd number of A/D converter results. You can accomplish this summation with firmware or with user-interaction software. Consider an example using a TC7109 A/D converter operating at 22.5 samples/sec. The equation yields the results in Table 1.

As Table 1 indicates, an A/D converter operating at 22.5 samples/sec can reject harmonics of 10Hz if you maintain a rolling average of nine samples. This technique rejects 50 and 60Hz; it's equivalent to one sample taken at the rate of 2.5 samples/sec. The curves in Figure 4 show the normal-mode rejection resulting from 1- and 9-sample averages at the rate of 22.5 conversions/sec (or one sample at 2.5 conversions/sec).

f_{NOISE} (Fundamental) In Hz	X Samples Summed
90	1
30	3
18	5
12.8	7
10	9

TABLE 1: TC67109 at 22.5 sample/sec.

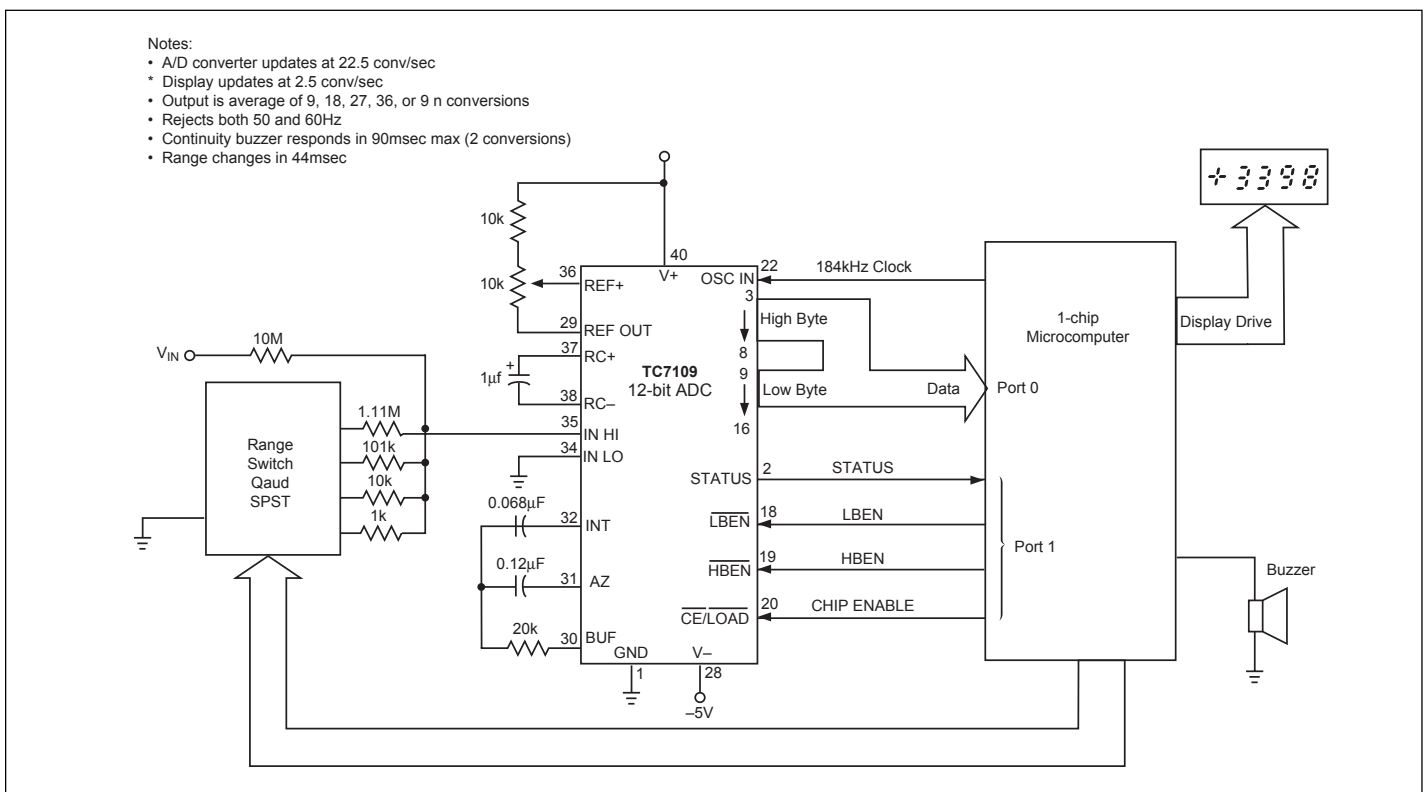


FIGURE 5: This 3 3/4-digit multimeter uses a numerical-integration technique to reject both 50 and 60Hz normal-mode noise. Although the DMM's display updates at 2.5 samples/sec, conversions take place at 22.5 samples/sec.

AN788

What's the point, you may ask, of sampling at the higher rate if you must wait for the result during a 9-period numerical integration? After the first 9-period wait, the system's pipeline is full and you may then obtain a new result for each cycle at the 22.5 samples/sec rate.

The numerical-integration technique has many practical applications. The Figure 5 circuit, for example, is a 3 3/4 digit DMM that uses a TC7109 13-bit A/D converter. The DMM updates the display at a 2.5 sample/sec rate for easy readability, yet it converts at a 22.5 samples/sec rate for fast response during autoranging and continuity checking.

Because the circuit averages nine samples, it rejects both 50 and 60Hz noise. Because it can carry a rolling average, the μP is capable of changing the number of conversions summed; it can therefore accommodate specific, user-programmable rejection frequencies.

Figure 6 shows connections for a system using the TC7109 in conjunction with a 6502 processor and 6522 peripheral interface adapter. The adapter's programmable timer provides the A/D converter's clock, thereby simplifying testing of noise rejection with different clock frequencies. This circuit allows you to evaluate numerical-integration-based designs using either a general-purpose μP -development system or a prototyping board. Figure 7 shows the assembly-language listing for the system; the flowchart appears in Figure 8.

X	Channels Scanned
3	13
5	16
7	15
9	10

TABLE 2: 16-channel multiplexer.

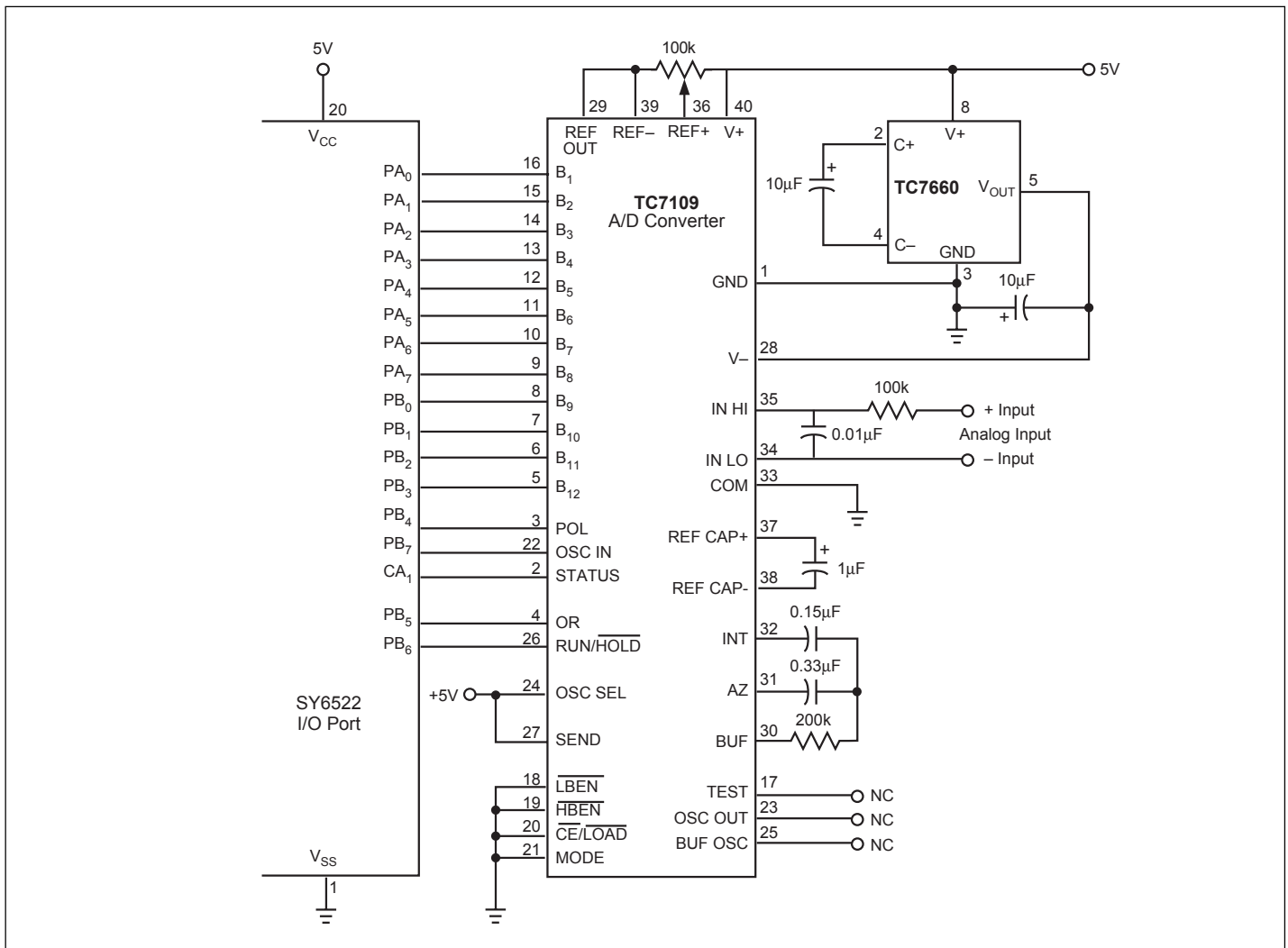


FIGURE 6: You can evaluate numerical integration with the circuit detailed in this schematic. The 6522 peripheral-interface adapter provides clocking and the μP interface for the dual-slope A/D converter.

```

094D.ASM
-----
000D      ;
000D      ; SOFTWARE TO DEMONSTRATE NUMERICAL INTEGRATION
000D      ; USING THE TC7109 INTERFACED TO A 6502
000D      ; MICROPROCESSOR VIA A 6522 I/O PORT
000D      ; RESULTS STORED AT 'RESLT' IN ZERO-PAGE MEMORY
000D      ; USER MUST PROVIDE INTERRUPT VECTOR FROM THE
000D      ; 6522'S CA1 INTERRUPT TO SVC ROUTINE AT *INTSVC*
000D      ;-----
000D      ;SYSTEM EQUATES
A800      10PT EQU A800H ;ADDRESS OF 6522 I/O PORT
0080      ORG 80H      ;RESERVE ZERO-PAGE MEMORY
0080      RESLT DS 3    ;16-BIT ACCUMULATOR FOR RESULTS, 1 BYTE FOR SIGN
0083      STORX DS 1    ;STORAGE FOR LOOP COUNTER
0084      STORHI DS 1   ;SAVE HIGH BYTE
0280      ORG 0280H    ;SET UP I/O PORT TO CONTROL TC7109
0280 A9C0  CLOCK LDA #0C0H ;PB6 & PB7 ARE OUTPUTS,
0282 8D00A8 STA IOPT ; PB7 IS THE TIMER 1 OUTPUT
0285 8D02A8 STA IOPT+2 ; (FOR 7109 CLOCK)
0288 8D0BA8 STA IOPT+0BH ;SQUARE WAVE OUTPUT ON PB-7
028B A912  LDA #12H    ;LOAD THE CONSTANT FOR
028D 8D04A8 STA IOPT+4 ; CLOCK TIMER
0290 20FA02 JSR SETREG ;INITIALIZE MEMORY REGISTERS
0293 8D05A8 STA IOPT+5 ; START THE 7109 CLOCK
0296 A982  LDA #82H    ;ENABLE INTERRUPT FROM
0298 8D0EA8 STA IOPT+0EM ; 6522 CA1 INPUT
029B 4C2303 JMP MAINPRG ;I/O PORT SETUP COMPLETE, SO
029E      ; JUMP TO O.S. OR TO MAIN PROGRAM
029E      ;INTERRUPT SERVICE ROUTINE
02B0      ORG 0280H
02B0 AD00A8 INTSVC LDA IOPT ;GET HIGH BYTE
02B3 AA    TAX        ;SAVE IT
02B4 290F  AND #0FH    ;ZERO MSBs FOR ARITHMATIC
02B6 8584  STA STORHI ;SAVE IT
02B8 8A    TXA        ;GET SIGN BIT BACK
02B9 2910  AND #10H   ;ANALOG INPUT NEGATIVE?
02BB F017  BEQ SUBTR  ; YES, SO SUBTRACT
02BD 18    CLC        ;RESULT POSITIVE SO ADD
02BE A580  LDA RESLT  ;GET LS BYTE OF THIS CONVERSION
02C0 6D01A8 ADC IOPT+1 ; ADD TO PREVIOUS READINGS
02C3 8580  STA RESLT  ; SAVE LS BYTE
02C5 A581  LDA RESLT+1 ;GET MS BYTE OF CONVERSION
02C7 6584  ADC STORHI ; ADD TO SUM
02C9 8581  STA RESLT+1 ; SAVE MS BYTE
02CB A582  LDA RESLT+2 ;GET SIGN
02CD 6900  ADC #00    ; ADD CARRY BIT, IF ANY
02CF 8582  STA RESLT+ ; AND SAVE
02D1 4CE802 JMP LOOPCNT ;JUMP TO TEST FOR 9 CONVERSIONS
02D4 38    SEC        ;SET CARRY FOR SUBTRACTION
02D5 A580  LDA RESLT  ; POLARITY OF THIS CONVERSION
02D7 ED01A8 SBC IOPT+1 ; IS NEGATIVE, SO DO A
02DA 8580  STA RESLT  ; DOUBLE-PRECISION
02DC A581  LDA RESLT+1 ; SUBTRACTION
02DE E584  SBC STORHI ;
02E0 8581  STA RESLT+1 ;
02E2 A582  LDA RESLT+2 ;
02E4 E900  SBC #00    ;
02E6 8582  STA RESLT+2 ;
02E8 C683  LOOPCNT DEC STORX ;HAVE WE DONE 9 CONVERSIONS?
02EA F001  BEQ DIVID  ; YES, SO NOW DIVIDE BY 9
02EC 40    RTI        ; NO, SO RETURN
02ED      PAGE

```

FIGURE 7: This assembly-language listing for the μ P A/D converter system in Figure 6 provides for 9-sample numerical integration, thereby eliminating normal-mode noise at frequencies that are multiples of 10Hz.

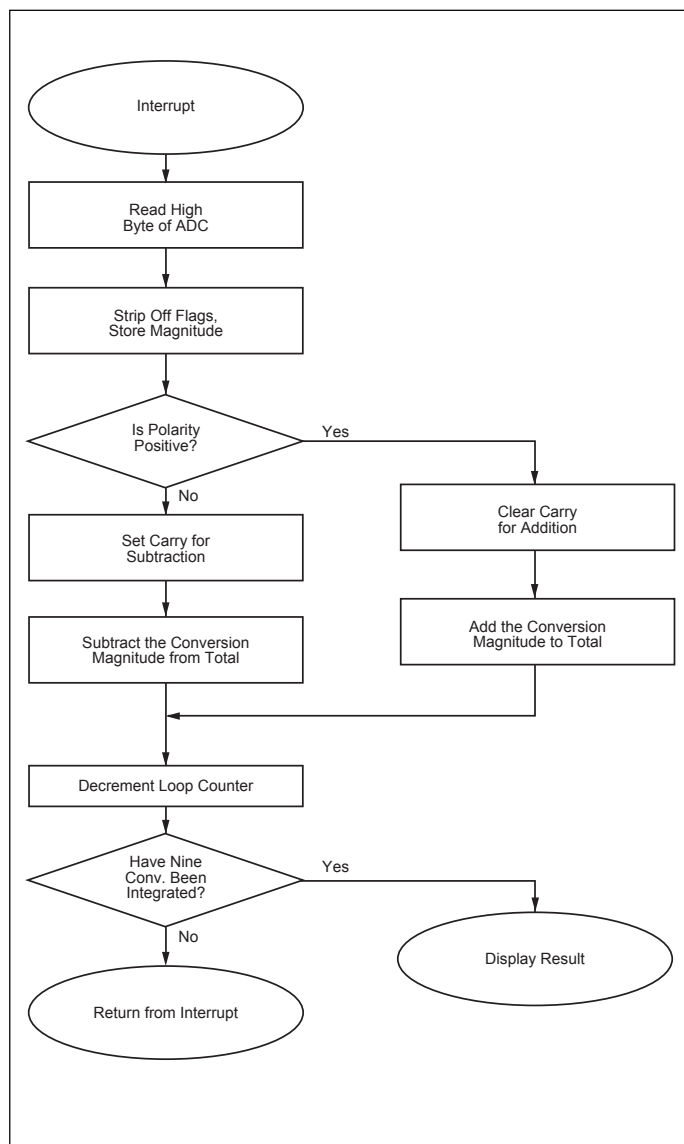


FIGURE 8: This flowchart for Figure 7's assembly-language routine summarizes the code necessary to control the Figure 6 evaluation circuit.

AN788

Adding Channels

By using analog multiplexers, you can take advantage of these speed-improvement techniques in multichannel systems. Solving the equation given earlier for X and using X to determine the scan length (or number of channels), you keep the noise-segment alignment in proper phase. This segmented approach (for a 16-channel system that requires the summation of three conversion) is shown in Figure 9. The scan length is found by dividing the number of available channels by X , taking the integer value, and then multiplying it by X and adding 1. Table 2 shows the relationship between the number of samples summed and the number of channels scanned for a 16-channel multiplexer.

A data-acquisition system using a 16-channel multiplexer could use a TC7109 running at 25 conversions/sec to reject all harmonics of 20Hz (including, of course, 60Hz), with a 5-sample average taken in the microprocessor. The system would still respond to large signal deviations in a single conversion.

The change from analog signal integration of noise to hybrid analog/numerical integration entails some trade-offs. The quantization error, for example, is always present; it can lead to a significant reduction in normal-mode rejection if the noise period is carved into too many segments. In addition, timing instability can create other error sources. For maximum stability, you must control the A/D converter's timing with a crystal oscillator.

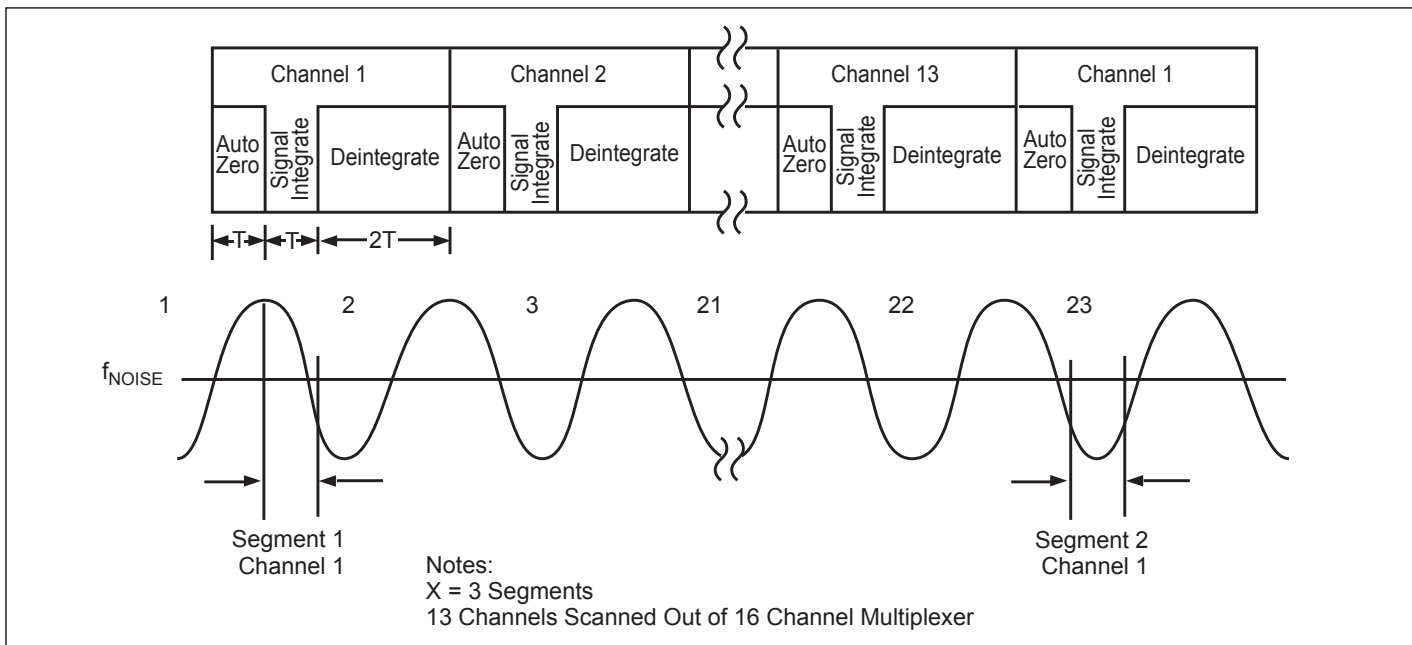


FIGURE 9: You can add multichannel capability to the enhanced-speed A/D-converter designs employing μ P-based numerical integration.

Information contained in this publication regarding device applications and the like is intended through suggestion only and may be superseded by updates. It is your responsibility to ensure that your application meets with your specifications. No representation or warranty is given and no liability is assumed by Microchip Technology Incorporated with respect to the accuracy or use of such information, or infringement of patents or other intellectual property rights arising from such use or otherwise. Use of Microchip's products as critical components in life support systems is not authorized except with express written approval by Microchip. No licenses are conveyed, implicitly or otherwise, under any intellectual property rights.

Trademarks

The Microchip name and logo, the Microchip logo, FilterLab, KEELOQ, microID, MPLAB, PIC, PICmicro, PICMASTER, PICSTART, PRO MATE, SEEVAL and The Embedded Control Solutions Company are registered trademarks of Microchip Technology Incorporated in the U.S.A. and other countries.


dsPIC, ECONOMONITOR, FanSense, FlexROM, fuzzyLAB, In-Circuit Serial Programming, ICSP, ICEPIC, microPort, Migratable Memory, MPASM, MPLIB, MPLINK, MPSIM, MXDEV, PICC, PICDEM, PICDEM.net, rfPIC, Select Mode and Total Endurance are trademarks of Microchip Technology Incorporated in the U.S.A.

Serialized Quick Turn Programming (SQTP) is a service mark of Microchip Technology Incorporated in the U.S.A.

All other trademarks mentioned herein are property of their respective companies.

© 2002, Microchip Technology Incorporated, Printed in the U.S.A., All Rights Reserved.

 Printed on recycled paper.

 

Microchip received QS-9000 quality system certification for its worldwide headquarters, design and wafer fabrication facilities in Chandler and Tempe, Arizona in July 1999. The Company's quality system processes and procedures are QS-9000 compliant for its PICmicro® 8-bit MCUs, KEELOQ® code hopping devices, Serial EEPROMs and microperipheral products. In addition, Microchip's quality system for the design and manufacture of development systems is ISO 9001 certified.



MICROCHIP

WORLDWIDE SALES AND SERVICE

AMERICAS

Corporate Office

2355 West Chandler Blvd.
Chandler, AZ 85224-6199
Tel: 480-792-7200 Fax: 480-792-7277
Technical Support: 480-792-7627
Web Address: <http://www.microchip.com>

Rocky Mountain

2355 West Chandler Blvd.
Chandler, AZ 85224-6199
Tel: 480-692-7966 Fax: 480-792-7456

Atlanta

500 Sugar Mill Road, Suite 200B
Atlanta, GA 30350
Tel: 770-640-0034 Fax: 770-640-0307

Boston

2 Lan Drive, Suite 120
Westford, MA 01886
Tel: 978-692-3848 Fax: 978-692-3821

Chicago

333 Pierce Road, Suite 180
Itasca, IL 60143
Tel: 630-285-0071 Fax: 630-285-0075

Dallas

4570 Westgrove Drive, Suite 160
Addison, TX 75001
Tel: 972-818-7423 Fax: 972-818-2924

Detroit

Tri-Atria Office Building
32255 Northwestern Highway, Suite 190
Farmington Hills, MI 48334
Tel: 248-538-2250 Fax: 248-538-2260

Kokomo

2767 S. Albright Road
Kokomo, Indiana 46902
Tel: 765-864-8360 Fax: 765-864-8387

Los Angeles

18201 Von Karman, Suite 1090
Irvine, CA 92612
Tel: 949-263-1888 Fax: 949-263-1338

New York

150 Motor Parkway, Suite 202
Hauppauge, NY 11788
Tel: 631-273-5305 Fax: 631-273-5335

San Jose

Microchip Technology Inc.
2107 North First Street, Suite 590
San Jose, CA 95131
Tel: 408-436-7950 Fax: 408-436-7955

Toronto

6285 Northam Drive, Suite 108
Mississauga, Ontario L4V 1X5, Canada
Tel: 905-673-0699 Fax: 905-673-6509

ASIA/PACIFIC

Australia

Microchip Technology Australia Pty Ltd
Suite 22, 41 Rawson Street
Epping 2121, NSW
Australia
Tel: 61-2-9868-6733 Fax: 61-2-9868-6755

China - Beijing

Microchip Technology Consulting (Shanghai)
Co., Ltd., Beijing Liaison Office
Unit 915
Bei Hai Wan Tai Bldg.
No. 6 Chaoyangmen Beidajie
Beijing, 100027, No. China
Tel: 86-10-85282100 Fax: 86-10-85282104

China - Chengdu

Microchip Technology Consulting (Shanghai)
Co., Ltd., Chengdu Liaison Office
Rm. 2401, 24th Floor,
Ming Xing Financial Tower
No. 88 TIDU Street
Chengdu 610016, China
Tel: 86-28-6766200 Fax: 86-28-6766599

China - Fuzhou

Microchip Technology Consulting (Shanghai)
Co., Ltd., Fuzhou Liaison Office
Unit 28F, World Trade Plaza
No. 71 Wusi Road
Fuzhou 350001, China
Tel: 86-591-7503506 Fax: 86-591-7503521

China - Shanghai

Microchip Technology Consulting (Shanghai)
Co., Ltd.
Room 701, Bldg. B
Far East International Plaza
No. 317 Xian Xia Road
Shanghai, 200051
Tel: 86-21-6275-5700 Fax: 86-21-6275-5060

China - Shenzhen

Microchip Technology Consulting (Shanghai)
Co., Ltd., Shenzhen Liaison Office
Rm. 1315, 13/F, Shenzhen Kerry Centre,
Renminnan Lu
Shenzhen 518001, China
Tel: 86-755-2350361 Fax: 86-755-2366086

Hong Kong

Microchip Technology Hongkong Ltd.
Unit 901-6, Tower 2, Metroplaza
223 Hing Fong Road
Kwai Fong, N.T., Hong Kong
Tel: 852-2401-1200 Fax: 852-2401-3431

India

Microchip Technology Inc.
India Liaison Office
Divyasree Chambers
1 Floor, Wing A (A3/A4)
No. 11, O'Shaughnessey Road
Bangalore, 560 025, India
Tel: 91-80-2290061 Fax: 91-80-2290062

Japan

Microchip Technology Japan K.K.
Benex S-1 6F
3-18-20, Shinyokohama
Kohoku-Ku, Yokohama-shi
Kanagawa, 222-0033, Japan
Tel: 81-45-471-6166 Fax: 81-45-471-6122

Korea

Microchip Technology Korea
168-1, Youngbo Bldg. 3 Floor
Samsung-Dong, Kangnam-Ku
Seoul, Korea 135-882
Tel: 82-2-554-7200 Fax: 82-2-558-5934

Singapore

Microchip Technology Singapore Pte Ltd.
200 Middle Road
#07-02 Prime Centre
Singapore, 188980
Tel: 65-6334-8870 Fax: 65-6334-8850

Taiwan

Microchip Technology Taiwan
11F-3, No. 207
Tung Hua North Road
Taipei, 105, Taiwan
Tel: 886-2-2717-7175 Fax: 886-2-2545-0139

EUROPE

Denmark

Microchip Technology Nordic ApS
Regus Business Centre
Lautrup høj 1-3
Ballerup DK-2750 Denmark
Tel: 45 4420 9895 Fax: 45 4420 9910

France

Microchip Technology SARL
Parc d'Activite du Moulin de Massy
43 Rue du Saule Trapu
Batiment A - 1er Etage
91300 Massy, France
Tel: 33-1-69-53-63-20 Fax: 33-1-69-30-90-79

Germany

Microchip Technology GmbH
Gustav-Heinemann Ring 125
D-81739 Munich, Germany
Tel: 49-89-627-144 0 Fax: 49-89-627-144-44

Italy

Microchip Technology SRL
Centro Direzionale Colleoni
Palazzo Taurus 1 V. Le Colleoni 1
20041 Agrate Brianza
Milan, Italy
Tel: 39-039-65791-1 Fax: 39-039-6899883

United Kingdom

Arizona Microchip Technology Ltd.
505 Eskdale Road
Winnersh Triangle
Wokingham
Berkshire, England RG41 5TU
Tel: 44 118 921 5869 Fax: 44-118 921-5820

03/01/02

