

Using the TC1142 for Biasing a GaAs Power Amplifier

Author: Patrick Maresca,
Microchip Technology, Inc.

INTRODUCTION

RF bandwidths for cellular systems such as AMPS, TACS, GSM, TDMA, and CDMA range from 800MHz to 1.0GHz. To provide RF transmissions over this range of frequencies, Gallium Arsenide (GaAs) has become the technology of choice and offers several advantages over silicon technology: a much higher cutoff frequency, higher breakdown voltage, lower noise figure, and higher power-added efficiency. This translates to lower power dissipation and longer talk time for cellular subscribers.

To properly bias a GaAs Power Amplifier (PA), a negative DC bias is required. There are many methods for providing this DC bias, but in a majority of applications, a regulated bias scheme is desirable over an unregulated inverting charge pump.

APPLICATION CIRCUIT

Figure 1 shows a typical application circuit for biasing a GaAs PA in a cellular subscriber unit's transmitter. Each key component of the circuit is described below.

Single Cell Li-Ion Battery and High-Side FET Switch

The main power source of this circuit is a single +3.6V Lithium Ion (Li-Ion) cell. Commercial packs using this battery chemistry can have a voltage as high as +4.2V or as low as +2.8V. This circuit will work under any condition within this range. Digital wireless standards such as TDMA and CDMA tend to operate the transmit section in "burst mode," switching the PA circuit off most of the time. Consequently, a digitally controlled power switch is included. The main requirements of this switch are: TTL/CMOS compatible control input, low "on" resistance, and high-side switching capability. "TX_ENABLE" signifies the power switch control signal, and is generated in the subscriber unit's modem controller.

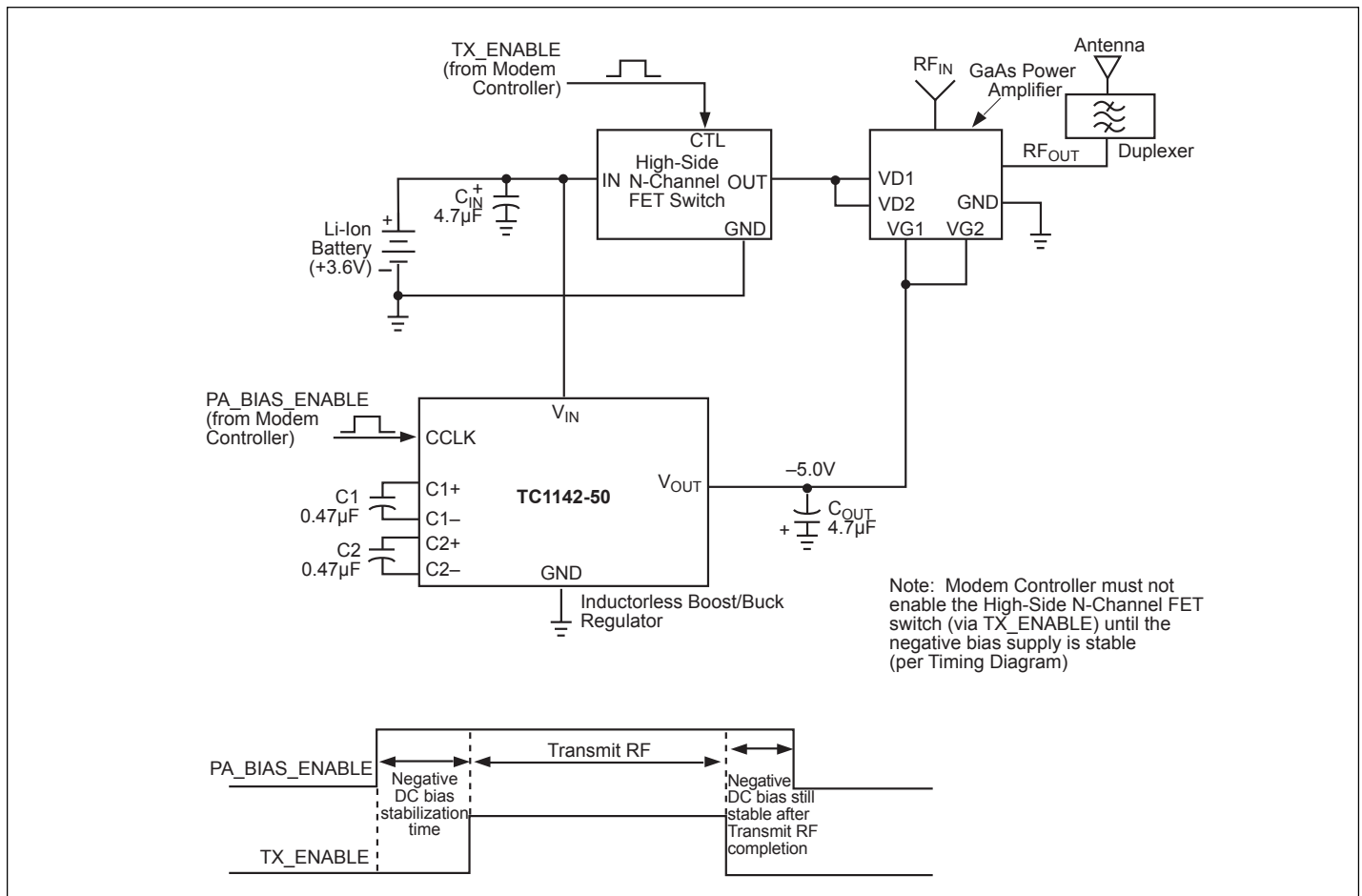


FIGURE 1: Application circuit for biasing a GaAs power amplifier in a cellular subscriber unit's transmitter.

AN808

Regulated Voltage Inverter

The inductorless voltage inverter is the core of the negative DC bias generator. It is a switched capacitor (charge pump) voltage converter, and the two 0.47 μ F flying capacitors (C1, C2) and the 4.7 μ F output capacitor (C_{OUT}) are the only external components required. The output current is a function of the C1, C2 flying capacitors, and the output ripple voltage magnitude is dependent on C1, C2, and C_{OUT}. The output ripple waveform is superimposed on the nominal -5.0VDC and has a fundamental frequency of 200KHz.

“PA_BIAS_ENABLE” is the power control signal for the regulated negative bias generator from the subscriber unit’s modem controller. Timing requirements for this signal versus “TX_ENABLE” are shown in Figure 1.

Previously, many designers have chosen a switching regulator for this circuit application, however the TC1142 has altered this approach. Since switching regulators require inductors, they increase the installed size, generated noise, and cost of providing this negative DC bias requirement. The TC1142 provides a “boost/buck” regulated conversion from either a single-cell Li-Ion, a multi-cell Nickel Cadmium (NiCd), or a multi-cell Nickel Metal Hydride (NiMH) battery pack. Figure 2 shows a simple block diagram of the TC1142 Inductorless Boost/Buck regulator architecture. The TC1142 can be ordered to provide output voltages from -3.0V to -5.0V in 1.0V increments.

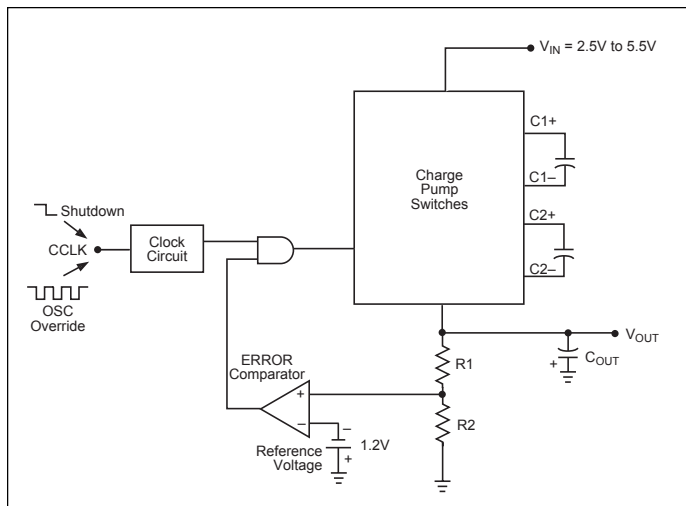


FIGURE 2: TC1142 architecture.

Circuit Description of Inductorless Boost/Buck Regulator

Ordinary charge pumps simply “convert” (not regulate) their input voltages. For example, a TC7660 charge pump generates a no-load output voltage of -5V when V_{IN} = +5V. However, its output voltage falls with a corresponding decrease in input voltage, an increase in output current, or both.

The TC1142 differs in that it uses pulse-frequency modulation (PFM) control to generate a regulated output voltage without the use of a post linear regulator. The TC1142 consists of an inverting/doubling charge pump and a feedback circuit (sampling resistors R1, R2, ERROR comparator, and associated voltage reference). When operating at full clock speed, the charge pump generates an unregulated output voltage equal to -2V_{IN}. The ERROR comparator inhibits operation of this charge pump (i.e. skips clock pulses) whenever the output voltage sampled by R1 and R2 is more negative than the reference voltage. The combination of the doubling pump and feedback regulation allows the absolute value of V_{OUT} to be regulated above or below that of V_{IN}. The TC1142 delivers an output voltage of -5V at a maximum of 20 mA over an input voltage range of +2.5V to +5.5V.

In order to maintain the lowest output resistance and output ripple voltage, it is recommended that low equivalent series resistance (ESR) capacitors be used. Additionally, larger values of the output capacitor and lower values of the flying capacitors will reduce the output voltage ripple.

Depending on the maximum voltage ripple allowed, the TC1142 will provide more-than-adequate regulation for most portable applications. Table 1 shows the relationship between output voltage ripple versus the two flying capacitors (C1 and C2) and the output capacitor (C_{OUT}). In each case, a 3.2V input is being converted to a -5V output.

Assuming the output is loaded to at least 20% of the maximum available current, the power efficiency of the inductorless boost/buck regulator can be estimated as the absolute value of the regulated voltage, divided by twice the input voltage. Thus, for a 3.6V battery input generating a -5V output, the efficiency of the inductorless boost/buck regulator will be approximately 70%.

C1, C2 (μF)	C _{OUT} (μF)	V _{IN} (V)	V _{OUT} (V)	V _{RIPPLE} (mV)
0.01	4.7	3.2	-5	14.6
0.22	4.7	3.2	-5	31.4
0.33	4.7	3.2	-5	46.1
0.47	4.7	3.2	-5	63.9
0.68	4.7	3.2	-5	88.7
1.0	4.7	3.2	-5	123.2
0.1	10	3.2	-5	7.0
0.22	10	3.2	-5	15.1
0.33	10	3.2	-5	22.4
0.47	10	3.2	-5	31.5
0.68	10	3.2	-5	44.7
1.0	10	3.2	-5	63.8

TABLE 1: Voltage ripple vs. C1/C2 flying capacitors and output capacitor C_{OUT}. ESR = 0.1Ω, I_{OUT} = 20mA.

GaAs PA, Duplexer, and Antenna

The GaAs PA radiates RF energy through a tuned bandpass filter (i.e. duplexer) to the subscriber unit's antenna port. Depending on the cellular standard and the power class of the subscriber unit, different power levels are required of GaAs PAs. For instance, a Class III AMPS subscriber unit must be able to radiate a minimum power level of +28dBm through the antenna. A CDMA Class III subscriber unit, in comparison, has a lower minimum power level requirement of +23dBm. Since the GaAs PA must be able to efficiently meet these industry standard power requirements, the RF losses in the duplexer must also be considered in the design of the PA.

SUMMARY

GaAs has become the technology of choice over silicon in cellular telephone power amplifier applications. With GaAs technology, lower noise figures, higher cutoff frequencies, and higher power-added efficiency allow the cellular user increased talk time as compared to silicon PAs.

GaAs PAs require a negative DC bias, and the TC1142 offers significant advantages over inductor-based switchers or unregulated charge pumps: lower generated noise; smaller installed size; lower installed cost; and excellent output regulation for subscriber units which operate in most existing worldwide cellular standards.

AN808

NOTES:

Information contained in this publication regarding device applications and the like is intended through suggestion only and may be superseded by updates. It is your responsibility to ensure that your application meets with your specifications. No representation or warranty is given and no liability is assumed by Microchip Technology Incorporated with respect to the accuracy or use of such information, or infringement of patents or other intellectual property rights arising from such use or otherwise. Use of Microchip's products as critical components in life support systems is not authorized except with express written approval by Microchip. No licenses are conveyed, implicitly or otherwise, under any intellectual property rights.

Trademarks


The Microchip name and logo, the Microchip logo, FilterLab, KEELOQ, microID, MPLAB, PIC, PICmicro, PICMASTER, PICSTART, PRO MATE, SEEVAL and The Embedded Control Solutions Company are registered trademarks of Microchip Technology Incorporated in the U.S.A. and other countries.


dsPIC, ECONOMONITOR, FanSense, FlexROM, fuzzyLAB, In-Circuit Serial Programming, ICSP, ICEPIC, microPort, Migratable Memory, MPASM, MPLIB, MPLINK, MPSIM, MXDEV, PICC, PICDEM, PICDEM.net, rfPIC, Select Mode and Total Endurance are trademarks of Microchip Technology Incorporated in the U.S.A.

Serialized Quick Turn Programming (SQTP) is a service mark of Microchip Technology Incorporated in the U.S.A.

All other trademarks mentioned herein are property of their respective companies.

© 2002, Microchip Technology Incorporated, Printed in the U.S.A., All Rights Reserved.

 Printed on recycled paper.

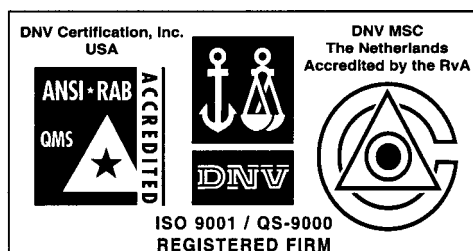

Microchip received QS-9000 quality system certification for its worldwide headquarters, design and wafer fabrication facilities in Chandler and Tempe, Arizona in July 1999. The Company's quality system processes and procedures are QS-9000 compliant for its PICmicro® 8-bit MCUs, KEELOQ® code hopping devices, Serial EEPROMs and microperipheral products. In addition, Microchip's quality system for the design and manufacture of development systems is ISO 9001 certified.



MICROCHIP

WORLDWIDE SALES AND SERVICE

AMERICAS

Corporate Office

2355 West Chandler Blvd.
Chandler, AZ 85224-6199
Tel: 480-792-7200 Fax: 480-792-7277
Technical Support: 480-792-7627
Web Address: <http://www.microchip.com>

Rocky Mountain

2355 West Chandler Blvd.
Chandler, AZ 85224-6199
Tel: 480-692-7966 Fax: 480-792-7456

Atlanta

500 Sugar Mill Road, Suite 200B
Atlanta, GA 30350
Tel: 770-640-0034 Fax: 770-640-0307

Boston

2 Lan Drive, Suite 120
Westford, MA 01886
Tel: 978-692-3848 Fax: 978-692-3821

Chicago

333 Pierce Road, Suite 180
Itasca, IL 60143
Tel: 630-285-0071 Fax: 630-285-0075

Dallas

4570 Westgrove Drive, Suite 160
Addison, TX 75001
Tel: 972-818-7423 Fax: 972-818-2924

Detroit

Tri-Atria Office Building
32255 Northwestern Highway, Suite 190
Farmington Hills, MI 48334
Tel: 248-538-2250 Fax: 248-538-2260

Kokomo

2767 S. Albright Road
Kokomo, Indiana 46902
Tel: 765-864-8360 Fax: 765-864-8387

Los Angeles

18201 Von Karman, Suite 1090
Irvine, CA 92612
Tel: 949-263-1888 Fax: 949-263-1338

New York

150 Motor Parkway, Suite 202
Hauppauge, NY 11788
Tel: 631-273-5305 Fax: 631-273-5335

San Jose

Microchip Technology Inc.
2107 North First Street, Suite 590
San Jose, CA 95131
Tel: 408-436-7950 Fax: 408-436-7955

Toronto

6285 Northam Drive, Suite 108
Mississauga, Ontario L4V 1X5, Canada
Tel: 905-673-0699 Fax: 905-673-6509

ASIA/PACIFIC

Australia

Microchip Technology Australia Pty Ltd
Suite 22, 41 Rawson Street
Epping 2121, NSW
Australia
Tel: 61-2-9868-6733 Fax: 61-2-9868-6755

China - Beijing

Microchip Technology Consulting (Shanghai)
Co., Ltd., Beijing Liaison Office
Unit 915
Bei Hai Wan Tai Bldg.
No. 6 Chaoyangmen Beidajie
Beijing, 100027, No. China
Tel: 86-10-85282100 Fax: 86-10-85282104

China - Chengdu

Microchip Technology Consulting (Shanghai)
Co., Ltd., Chengdu Liaison Office
Rm. 2401, 24th Floor,
Ming Xing Financial Tower
No. 88 TIDU Street
Chengdu 610016, China
Tel: 86-28-6766200 Fax: 86-28-6766599

China - Fuzhou

Microchip Technology Consulting (Shanghai)
Co., Ltd., Fuzhou Liaison Office
Unit 28F, World Trade Plaza
No. 71 Wusi Road
Fuzhou 350001, China
Tel: 86-591-7503506 Fax: 86-591-7503521

China - Shanghai

Microchip Technology Consulting (Shanghai)
Co., Ltd.
Room 701, Bldg. B
Far East International Plaza
No. 317 Xian Xia Road
Shanghai, 200051
Tel: 86-21-6275-5700 Fax: 86-21-6275-5060

China - Shenzhen

Microchip Technology Consulting (Shanghai)
Co., Ltd., Shenzhen Liaison Office
Rm. 1315, 13/F, Shenzhen Kerry Centre,
Renminnan Lu
Shenzhen 518001, China
Tel: 86-755-2350361 Fax: 86-755-2366086

Hong Kong

Microchip Technology Hongkong Ltd.
Unit 901-6, Tower 2, Metroplaza
223 Hing Fong Road
Kwai Fong, N.T., Hong Kong
Tel: 852-2401-1200 Fax: 852-2401-3431

India

Microchip Technology Inc.
India Liaison Office
Divyasree Chambers
1 Floor, Wing A (A3/A4)
No. 11, O'Shaughnessey Road
Bangalore, 560 025, India
Tel: 91-80-2290061 Fax: 91-80-2290062

Japan

Microchip Technology Japan K.K.
Benex S-1 6F
3-18-20, Shinyokohama
Kohoku-Ku, Yokohama-shi
Kanagawa, 222-0033, Japan
Tel: 81-45-471-6166 Fax: 81-45-471-6122

Korea

Microchip Technology Korea
168-1, Youngbo Bldg. 3 Floor
Samsung-Dong, Kangnam-Ku
Seoul, Korea 135-882
Tel: 82-2-554-7200 Fax: 82-2-558-5934

Singapore

Microchip Technology Singapore Pte Ltd.
200 Middle Road
#07-02 Prime Centre
Singapore, 188980
Tel: 65-6334-8870 Fax: 65-6334-8850

Taiwan

Microchip Technology Taiwan
11F-3, No. 207
Tung Hua North Road
Taipei, 105, Taiwan
Tel: 886-2-2717-7175 Fax: 886-2-2545-0139

EUROPE

Denmark

Microchip Technology Nordic ApS
Regus Business Centre
Lautrup høj 1-3
Ballerup DK-2750 Denmark
Tel: 45 4420 9895 Fax: 45 4420 9910

France

Microchip Technology SARL
Parc d'Activite du Moulin de Massy
43 Rue du Saule Trapu
Batiment A - 1er Etage
91300 Massy, France
Tel: 33-1-69-53-63-20 Fax: 33-1-69-30-90-79

Germany

Microchip Technology GmbH
Gustav-Heinemann Ring 125
D-81739 Munich, Germany
Tel: 49-89-627-144 0 Fax: 49-89-627-144-44

Italy

Microchip Technology SRL
Centro Direzionale Colleoni
Palazzo Taurus 1 V. Le Colleoni 1
20041 Agrate Brianza
Milan, Italy
Tel: 39-039-65791-1 Fax: 39-039-6899883

United Kingdom

Arizona Microchip Technology Ltd.
505 Eskdale Road
Winnersh Triangle
Wokingham
Berkshire, England RG41 5TU
Tel: 44 118 921 5869 Fax: 44-118 921-5820

03/01/02

