

Basic PLL Filters for the rfPIC™ /rfHCS

Author: Myron Loewen
Microchip Technology Inc.


INTRODUCTION

This application note will give designers a method to design their own Phase Lock Loop (PLL) filters for rfPIC transmitters, such as the rfPIC12C509 and the rfHCS362. First the circuit will be briefly described and then example components will be found with the included Microsoft® Excel® spreadsheet. The spreadsheet is called pllfiler.xls and can be downloaded from the same Microchip web page that hosts this application note.

A PLL circuit creates an output signal synchronized to the phase of the crystal reference signal as shown in Figure 1. The RF output frequency is from a voltage controlled oscillator (VCO). It is divided by 32 for comparison to the reference oscillator. A phase-frequency detector compares the phase of the output signal to the crystal oscillator reference signal. The loop filter closes the control loop by filtering the phase error signal to create the voltage that drives the VCO.

If the output signal drifts, then the phase-frequency detector tells the charge pump to push it back into phase. Thus, the accuracy and stability of a crystal oscillator can correct an otherwise poor RF oscillator.

FIGURE 1: BLOCK DIAGRAM

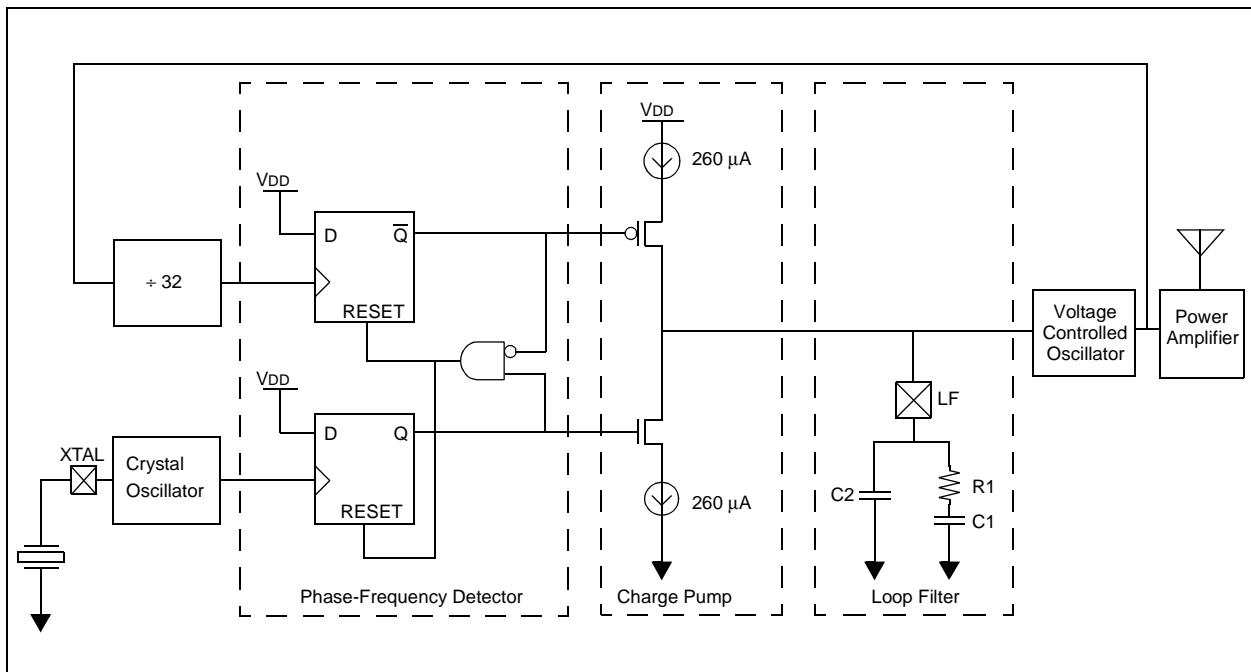

The loop filter we are trying to design is basically a capacitor holding the DC voltage that controls the VCO. The charge pump gives it a shot of current when the phase-frequency detector determines the output frequency is a little slow, or discharges the cap when the output is a little fast. Since the output error cannot be resolved faster than the reference frequency, the maximum frequency of current spikes hitting the loop filter is the reference frequency.

Every filter has a bandwidth and a phase response, this low pass PLL filter is no exception. The low pass bandwidth is easy to understand as the maximum frequency that the filter will pass. Low order filters roll off slowly, so we consider the frequency whose output is 3 dB down as the cutoff frequency. The phase response is a little more difficult to visualize, but just imagine that the filter is increasingly delaying the output signal as it exceeds the cutoff frequency. Our low pass filter will be able to delay the higher frequencies up to a quarter wavelength, or 90°. However, together with the 90° phase shift of the VCO we get dangerously close to 180° which would let the loop oscillate around the RF output frequency.

Oscillations would also require a minimum loop gain of 1, so for a low pass filter we only need to determine the phase shift of frequency where the filter is at unity gain.

Then subtract this calculated phase shift from the 180° limit to get our safety margin, which we call the phase margin. All higher frequencies with phase shift approaching 180° will be attenuated and will not pose an oscillation threat.


For those more familiar with control theory, phase margin (ϕ_m) is directly related to the damping factor (ζ) by this formula:

$$\tan \frac{(90^\circ - \phi_m)}{2} = \frac{1}{4 \cdot \zeta^2}$$

As the phase margin gets small, the loop filter will ring when the reference frequency starts up or is modulated. If the phase margin is large, then it takes much longer to lock on the reference frequency. The response time is actually a function of both the phase margin and the filter bandwidth. Filter capacitors larger than 10 nF, or resistive loading on the filter pin, will also affect response time by limiting the slew rate. The 260 μ A peak output current from the charge pump, reduced by maximum duty cycle to about 180 μ A, limits the slew rate according to this formula:

$$\text{rise time} = \Delta V \cdot C / I$$

FIGURE 2: LOOP BANDWIDTH VS. PHASE NOISE

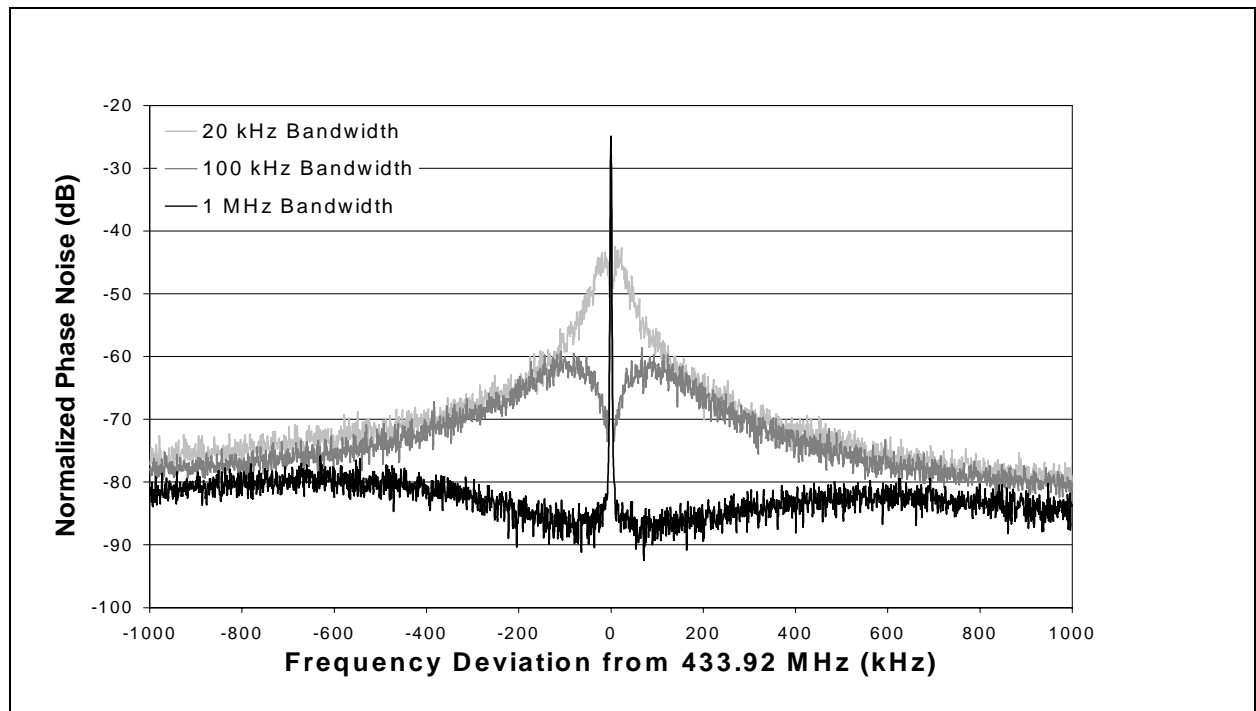

The VCO output frequency is not very stable by itself and this frequency jitter is called phase noise. A benefit of the closed control loop is that the phase noise can be controlled. Figure 2 shows the filter bandwidth effect on phase noise. There is more information on this in the Microwave & RF Radio Systems article, parts 4 and 5, which are referenced at the end of this application note.

Noise within the loop bandwidth is suppressed while noise outside the bandwidth may increase. Thus it is desirable to design a filter with the largest possible bandwidth.


As the filter bandwidth is increased, more of the phase-frequency detector noise gets through. This noise appears as spurs in the RF output spectrum at the carrier frequency plus and minus integer multiples of the reference frequency. Figure 3 shows the spur levels for a filter bandwidth of 1 MHz. This is an important bandwidth because here the noise spurs start to get significant with respect to the carrier phase noise. Increasing the bandwidth further will make the spurs dominate the transmitted noise. For a narrow band receiver it may be beneficial to increase the bandwidth to 2 MHz and eliminate more of the phase noise since the spurs are filtered off by the receiver bandwidth. If the carrier

frequency is adjacent to a restricted band then it is better to reduce the bandwidth to below 500 kHz which will reduce the spurs that reach into the restricted band.

Choosing a loop filter bandwidth is also limited by physical constraints. As the bandwidth gets very narrow the capacitors required become very large. Too wide a bandwidth will be difficult to manufacture because the capacitors become very small. To keep the design simple try and use capacitors that are at least 5 times bigger than the sum of the parasitic and LF pin capacitance. Assuming this is about 2 pF, the filter capacitors should be at least 10 pF. This will limit the bandwidth to a maximum of 1.2 MHz. Lower carrier frequencies can have a slightly higher loop bandwidth. The spreadsheet will let you enter a stray capacitance value to design for wider bandwidths but these designs are more susceptible to manufacturing variations.

The 2 pole filter design, shown in Figure 1, was chosen because it is the lowest order filter that gets the desired bandwidth and phase margin performance. This simple circuit is easy to analyze and uses only three passive components. More expensive active filters or more complex passive filters may improve particular characteristics, but they can also insert more noise into the control loop.

FIGURE 3: REFERENCE FREQUENCY SPURS

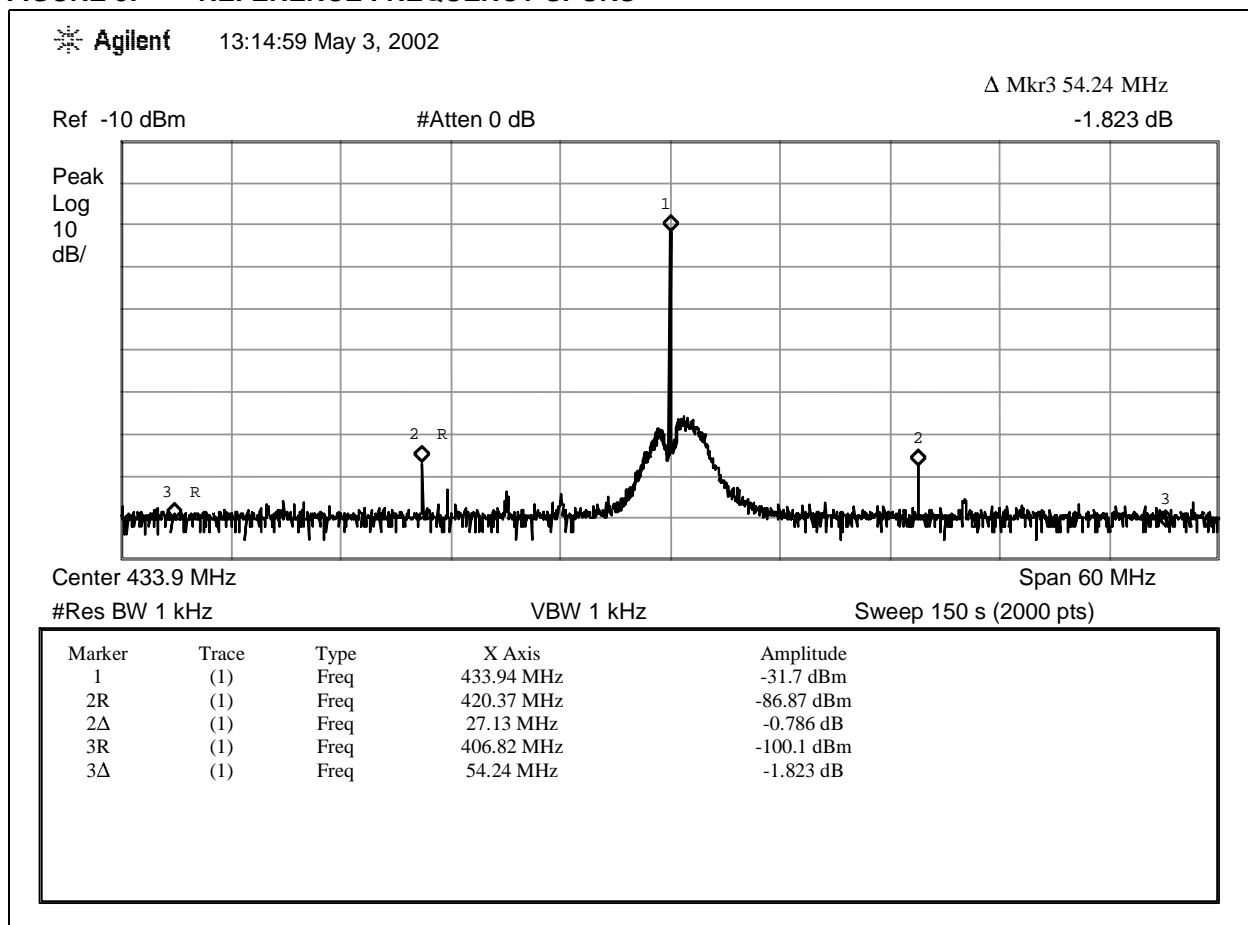

Initial Requirements

For most designs, the three loop filter components can be quickly found with the spreadsheet calculator. The only value the spreadsheet requires is the RF frequency. The application and the governing regulations in the market area will determine this frequency. The Microwave & RF Radio Systems article part 2, referenced at the end of this application note, provides more detail on frequency selection.

To optimize the design a little more, you may also modify any of the assumptions that the spreadsheet makes for loop bandwidth, phase margin, and stray capacitance.

The PLL filter basically holds the DC level that controls the VCO. However, the output frequency has an impact on the filter because the VCO is not linear. At some loop filter voltages the VCO frequency is more sensitive to loop filter variations. The typical response curve is shown in Figure 4. The spreadsheet interpolates a look-up table of typical measured values to determine the loop gain.

In amplitude shift keying (ASK) the signal amplitude is modulated to transmit data while the carrier frequency is held constant. Since the frequency does not change the filter can trade off slower response time for better spurious noise filtering. The response time must be fast enough to enable and stabilize the output frequency before the power amp begins transmitting. A faster PLL also reduces unwanted frequency modulation caused by power supply variations.

In frequency shift keying (FSK), the carrier frequency is modulated to transmit data while the signal amplitude is held constant. The frequency must change quickly and smoothly to the new frequency to achieve higher

baud rates and lower inter-symbol interference. Decreasing the phase margin a couple degrees and increasing the filter bandwidth will improve settling time on the start of each bit. Making the bandwidth too wide increases the size of the reference spurs. In most cases the default bandwidth of 1 MHz will work well since the data rate is already limited by how far the crystal can be pulled.

Calculating Component Values

The formulas to do these calculations are embedded in the Microsoft Excel spreadsheet, called pllfiter.xls that can be downloaded from the same Microchip web page that hosts this application note. The format of the spreadsheet is shown in Figure 5. This spreadsheet example was run at 433.92 MHz, since it is a typical frequency for many rPIC and rHCS applications.

The spreadsheet is laid out in the order you would typically solve the problem. First the highlighted user input frequency, then the fixed transmitter parameters, and most importantly, the three calculated filter component values. Step 1 calculates theoretical component values for the given filter parameters. Step 2 does the reverse, calculating filter parameters for the actual filter components. Step 3 checks if your circuit measurements match the original design target.

The values for the 2 capacitors and resistor will immediately be recalculated as the RF frequency is modified. This is your opportunity to see how the components vary as the other fields, like the filter bandwidth, are modified. Just use the Undo command to restore the original default parameters or download the file again. Some of the cells are hidden to reduce clutter. Most of the cells are locked without a password to prevent accidentally changing the fixed parameters.

FIGURE 4: TYPICAL LOOP FILTER VOLTAGE AND VCO GAIN CURVES

 


FIGURE 5: PLL FILTER DESIGN CALCULATOR

AN846 Filter Design Calculator

Rev 1

Step 1: Enter transmitter frequency

Desired System:
 Transmitter Frequency MHz

Notes:
 Determined by regulations

Design Parameters:
 Crystal Frequency 13.56 MHz
 Desired Phase Margin 50 degrees
 Desired Loop Bandwidth 1000 kHz

Device Parameters:
 Multiplication Factor (N) 32 times
 Phase Detector Gain (K ϕ) 0.26 mA
 VCO Gain (K v_{co}) 197.868 MHz/V
 LF pin stray capacitance 2 pF

Filter Calculations:

Natural Frequency	641155 Hz
Loop Bandwidth	6283185 rad/s
Calculated Pole	17262910 Hz
Calculated Zero	2286892 Hz
Lock Time	5 us
Calculated Ctotal	112 pF
Calculated C1	<input type="text" value="99"/> pF
Calculated C2	<input type="text" value="13"/> pF
Calculated R1	<input type="text" value="4414"/> ohms

Reduce loop bandwidth for smaller spurs
 Increase loop bandwidth for less phase noise

The diagram shows a circuit for the LF pin of an rfHCS362 rfPIC12C509 device. A resistor R1 is connected between the LF pin and a common ground point. Two capacitors, C1 and C2, are connected in parallel between this common ground point and the actual ground. The LF pin is also connected to the common ground point.

Step 2: Enter Actual Components and Tolerances

Actual Values Used:

Actual Value C1	<input type="text" value="100"/> pF
Actual Value C2	<input type="text" value="12"/> pF
Actual Value R1	<input type="text" value="4700"/> ohms

Tolerance:

	<input type="text" value="± 5.0%"/>
	<input type="text" value="± 5.0%"/>
	<input type="text" value="± 1.0%"/>

Filter Analysis:

	Min:	Typical:	Max:
Natural Frequency	622766	638145	654723 Hz
Actual Pole	16435003	17325228	18300705 Hz
Actual Zero	2006280	2127660	2262264 Hz
Actual Loop Bandwidth	1023146	1038389	1054269 Hz
Actual Phase Margin	47	49	51 degrees
Lock Time	5	5	5 us

Step 3: Enter Measured Voltage Peak and Bandwidth

Oscilloscope:

Voltage final	<input type="text" value="1.466"/> V
Voltage peak	<input type="text" value="1.648"/> V
Voltage valley	<input type="text" value="1.456"/> V
Time peak	<input type="text" value="370"/> us
Time valley	<input type="text" value="1880"/> us

Spectrum Analyser:

Shoulder-Shoulder	<input type="text" value="1800"/> kHz
-------------------	---------------------------------------

Phase Margin	33.0 degrees
Damping Factor	0.68
Natural Freq.	450.74 kHz
Bandwidth	900 kHz

Choosing Components

The filter calculations will yield ideal component values which may be considerably different than the standard or stocked values you have the freedom to choose from. For this reason Step 2 of the filter worksheet recalculates the filter performance for real world component values and tolerances.

Choose actual capacitor and resistor values from the pull-down lists or type in your own value. Do the same for the plus/minus tolerance and then press the Recalculate button. Choose different values or more accurate components if the resulting worst case phase margins are not between 40 and 60 degrees. A wide variation in the loop bandwidth means a wide variation in the reference clock spur levels. Be sure to test boards with the widest bandwidth to ensure the spur levels are acceptable.


The example in Figure 5 shows the closest standard values that matched this design. Pressing the Recalculate button shows that the typical results still match our design target. It also shows the component tolerances do not exceed the phase limits.

There is a lot of flexibility in the actual components you choose. For example, the footprint size, type of dielectric, voltage rating and tolerance. The loop filter circuit runs at the crystal frequency, so typically, ceramic capacitors are the best low cost choice. For dielectrics choose NP0 if possible. The larger value for C1 may require an X7R. In this example, C1 and C2 are both available in the 0603 package with an NP0 dielectric. Be sure to update the tolerance to 10% if you choose a X7R dielectric.

Using a metal film resistor can reduce the resistor's noise contribution, but a cheaper thick film resistor should work fine. In this example the resistor is a 1% thick film. This costs only a fraction of a cent more than a 5% tolerance part, but significantly reduces the phase margin variations in production for lower bandwidth filters.

The footprint size of the components is not critical and is usually determined by the production limitations. Ideally, smaller components are better to reduce the filter circuit area and the associated sensitivity to radiated noise. Surface mount components make RF design much easier with reduced lead inductance and they do not interfere with solid ground planes.

FIGURE 6: MEASURING FILTER BANDWIDTH ON SPECTRUM ANALYZER

 

Board Layout

The PLL loop filter may look like a DC voltage, but it is very sensitive to noise and leakage. Very small signals can be induced on top of the DC level and converted to frequency variations by the VCO. They will appear as noise spurs in the RF output spectrum. For example, Figure 6 shows two spurs about ± 100 kHz from the carrier which are caused by the internal rfHCS362 oscillator.

A dirty circuit board will let charge bleed off the capacitor and require extra current spikes from the phase detector to keep up the voltage. This extra ripple at the crystal reference frequency will appear on the output spectrum as spurs at the carrier frequency plus and minus multiples of the reference frequency. The leakage is not typically a problem until you get to filter capacitors below 20 pF where 100 k Ω of leakage can increase spurs by more than 10 dB.

Start your layout by keeping any other traces out of the filter area. Stay especially far away from high current traces like power and the antenna. Keep the filter traces as short as possible to pick up less noise. Provide a good solid ground plane on the back side of the board. Wrapping ground traces around the filter on the component side with several low impedance vias to the ground plane can also reduce radiated noise from being captured, but too close and the board will be more susceptible to leakage. One final tip that applies to any high frequency design is to eliminate or minimize the area of loops. Any traces and components in series that make a complete loop at RF frequencies create an antenna that is both susceptible to noise and transmits noise.


Testing

The min and max values calculated by the spreadsheet indicate variability, but do not guarantee your design will work. You should test the worst case boards over temperature and voltage ranges to verify your filter design is acceptable.

With an oscilloscope you can measure the phase margin from the transient response on the LF pin as the chip powers up, or when switching between frequencies in FSK operation. With a spectrum analyzer you can compare the spectrum of the transmitted carrier to the desired bandwidth and look for other sources of noise. Modify your circuit to test with a steady unmodulated RF signal. Your results may be clearer if you eliminate some resonances by detuning the antenna. Once the circuit is working and the transmit spectrum looks right, then turn on the modulation and test for filter response times and ringing on FSK designs.

A high logic level on RFENIN pin enables the reference crystal oscillator and the voltage controlled oscillator. The difference between the two oscillator frequencies causes the charge pump to quickly charge up the filter caps as shown in Figure 7. The PLL can lock onto the frequency faster than the starting up crystal oscillator can stabilize. When the LF pin reaches 0.8V the RF frequency is close to locked on the crystal frequency. This initiates an internal 150 microsecond delay to ensure that the PLL settles. After the delay the PS/DATAASK bias current and power amplifier are enabled to start transmitting.

FIGURE 7: TRANSMITTER START-UP WAVEFORM

 

To verify that the phase angle matches your design target, zoom in on the PLL filter voltage as the PLL locks on the crystal reference frequency. Measure the peak, valley, and settled voltages and times as shown in Figure 8. Plug them into Step 3 on the spreadsheet to get your measured phase margin and natural frequency. Even with a high impedance, low capacitance scope probe there can be significant measurement error. However, if the scope capacitance is much smaller than the filter capacitance, this simple test can get results within a couple percent of your design target. For large capacitance the response will be slew rate limited by the 260 μ A charge pump.

A 20 MHz spectrum analyzer could be used to further analyze the loop filter noise, but it is faster just to skip over to the RF output with an RF spectrum analyzer. These RF tests have to be done anyway to pass radiation regulations and they do not modify the PLL filter with probe loading. The loop bandwidth can be seen in Figure 6, as approximately the distance from the carrier frequency in the center to the noise shoulder on either side.

This setup can also reveal other noise sources that create unwanted spurs. The difference of the noise spur frequency from the carrier is the frequency of the noise


source on your circuit board. For example, there will be spurs at integer multiples of the crystal frequency which are amplified by board leakage. To see this effect put a 100 k Ω resistor in parallel with either C1 or C2. There may also be spurs at multiples of the crystal frequency divided by 4 from the CLKOUT signal.

To find the source of the noise spur measure the frequency offset from the carrier and probe your circuit for other traces carrying that frequency. Disable or modify the frequency of that signal to see if the RF spur changes. Once you identify the source of the noise you can reduce it to acceptable levels with solutions like moving traces, shielding with ground traces, filtering, by-pass capacitors, or modifying its frequency.

The PLL filter will determine the transmitted phase noise and spurs near the carrier frequency. Microchip has other application notes such as AN826 and AN831 to help with the crystal selection and antenna matching.

If your transmitter circuit is working satisfactorily then you are ready to get it packaged and tested for regulatory compliance. The next section lists some resources for studying PLL filters in more depth. There is also lots of free material available online with a little search of the web.

FIGURE 8: MEASURING PHASE MARGIN FROM OVERSHOOT WITH AN OSCILLOSCOPE

 

Additional Information

Phase-Locked Loops, Design, Simulations, & Testing 3rd Ed; Roland E Best; McGraw-Hill; ISBN 0-07-006051-7

PLL Performance, Simulation, and Design, Dean Banerjee, ISBN 0-9708207-0-4

“Radio Systems, Part 1, Design of Short-Range Radio Systems”, (Microwaves & RF [September 2001] 73-80)

“Radio Systems, Part 2, Understanding Regulations”, (Microwaves & RF [October 2001] 79-96)

“Radio Systems, Part 3, Constructing Circuits”, (Microwaves & RF [February 2002] 59-74)

“Radio Systems, Part 4, Tracking Phase Noise”, (Microwaves & RF [March 2002] 57-64),
Penton Media, www.mwrf.com

APPENDIX A: MATHEMATICAL DERIVATIONS

This appendix will show how the equations for R1, C1, and C2 are derived. The solution will be described physically, where possible, to avoid losing anyone in the Laplace transforms. For greater detail, read the references given in the previous section.

The open loop gain of the PLL circuit will be the product of the phase detector gain (K_ϕ), filter impedance (X_{total}), and VCO gain (K_{vco}) divided by N. The large frequency error detected in the open loop case causes the charge pump to push its maximum current. This current, times the filter impedance, is the voltage seen by the VCO input. The VCO then converts the voltage back to a frequency. The open loop frequency response poles and zeros are the same as for X_{total} because N and K_ϕ are constant and K_{vco} is approximately constant near the desired output frequency.

EQUATION 1:

$$\text{Gain}_{\text{openloop}} = \frac{K_\phi \cdot X_{\text{total}} \cdot K_{\text{vco}}}{N}$$

The combined impedance of the three filter components in the loop filter are:

EQUATION 2:

$$X_{\text{total}} = \frac{1}{\frac{1}{X_{C2}} + \frac{1}{R1 + X_{C1}}} = X_{C2} \cdot \frac{(R1 + X_{C1})}{(R1 + X_{C2} + X_{C1})}$$

The impedance can be defined in terms of frequency by replacing X_c with $1/j\omega C$, and then grouping the zero and poles:

EQUATION 3:

$$X_{\text{total}}(\omega) = \frac{1 + j \cdot \omega \cdot R1 \cdot C1}{j \cdot \omega \cdot (C1 + C2) \cdot \left(1 + j \cdot \omega \cdot R1 \cdot \frac{C1 \cdot C2}{C1 + C2} \right)}$$

The time constant for the zero will be defined as:

EQUATION 4:

$$\tau_z := R1 \cdot C1$$

The first pole is at zero and the time constant for the second pole will be defined as:

EQUATION 5:

$$\tau_p := R1 \cdot \frac{C1 \cdot C2}{C1 + C2}$$

Substituting Equation 4 and Equation 5 into Equation 3 simplifies it to:

EQUATION 6:

$$X_{\text{total}}(\omega) := \frac{1 + j \cdot \omega \cdot \tau_z}{j \cdot \omega \cdot (C1 + C2) \cdot (1 + j \cdot \omega \cdot \tau_p)}$$


Phase margin is the difference between 180 degrees and the actual phase shift at the frequency where the open loop gain equals 1. The phase response can be written as the sum of the vector angles originating at the poles minus the vector angle originating from the zero:

EQUATION 7:

$$\phi(\omega) := \pi + \text{atan}(\omega \cdot \tau_z) - \text{atan}(\omega \cdot \tau_p)$$

Figure 9 should make everything a little clearer. The graph is plotted against the frequency of the filter and not the final RF output frequency.

FIGURE 9:

 

Solving for the maximum phase margin by finding where the derivative of $\phi_m(\omega_c)$ equals 0 results in:

EQUATION 8:

$$\omega_c \cdot \tau_z = \frac{1}{\omega_c \cdot \tau_p}$$

Substituting Equation 8 back into Equation 7 and solving for τ_p finds the time constant of the pole in terms of the 3 dB loop bandwidth (ω_c) and maximum phase margin (ϕ_m):

EQUATION 9:

$$\tau_p = \frac{-\tan(\phi_m) + \sqrt{\tan(\phi_m)^2 + 1}}{\omega_c} = \frac{\sec(\phi_m) - \tan(\phi_m)}{\omega_c}$$

The time constant is easily derived from Equation 8 using Equation 9:

EQUATION 10:

$$\tau_z = \frac{1}{\omega_c \cdot \sec(\phi_m) - \omega_c \cdot \tan(\phi_m)}$$

The value of the sum of the 2 capacitors is found by setting the open loop gain to 1 and substituting Equation 9 and Equation 10 into Equation 1:

EQUATION 11:

$$C1 + C2 = \frac{K_\phi \cdot K_{VCO} \cdot \tau_z}{N \cdot \omega_c}$$

Equation 5 can now be used to find all the component values with the time constants from Equation 9 and Equation 10:

$$C2 = \frac{(C1 + C2) \cdot \tau_p}{\tau_z} = \frac{K_\phi \cdot K_{VCO}}{N \cdot \omega_c} \cdot \tau_p$$

EQUATION 12:

$$C1 = \frac{K_\phi \cdot K_{VCO}}{N \cdot \omega_c} \cdot (\tau_z - \tau_p)$$

EQUATION 13:

$$R1 = \frac{\tau_z}{C1}$$

NOTES:

Note the following details of the code protection feature on PICmicro® MCUs.

- The PICmicro family meets the specifications contained in the Microchip Data Sheet.
- Microchip believes that its family of PICmicro microcontrollers is one of the most secure products of its kind on the market today, when used in the intended manner and under normal conditions.
- There are dishonest and possibly illegal methods used to breach the code protection feature. All of these methods, to our knowledge, require using the PICmicro microcontroller in a manner outside the operating specifications contained in the data sheet. The person doing so may be engaged in theft of intellectual property.
- Microchip is willing to work with the customer who is concerned about the integrity of their code.
- Neither Microchip nor any other semiconductor manufacturer can guarantee the security of their code. Code protection does not mean that we are guaranteeing the product as “unbreakable”.
- Code protection is constantly evolving. We at Microchip are committed to continuously improving the code protection features of our product.

If you have any further questions about this matter, please contact the local sales office nearest to you.

Information contained in this publication regarding device applications and the like is intended through suggestion only and may be superseded by updates. It is your responsibility to ensure that your application meets with your specifications. No representation or warranty is given and no liability is assumed by Microchip Technology Incorporated with respect to the accuracy or use of such information, or infringement of patents or other intellectual property rights arising from such use or otherwise. Use of Microchip's products as critical components in life support systems is not authorized except with express written approval by Microchip. No licenses are conveyed, implicitly or otherwise, under any intellectual property rights.

Trademarks


The Microchip name and logo, the Microchip logo, FilterLab, KEELOQ, microID, MPLAB, MXDEV, PIC, PICmicro, PICMASTER, PICSTART, PRO MATE, SEEVAL and The Embedded Control Solutions Company are registered trademarks of Microchip Technology Incorporated in the U.S.A. and other countries.


dsPIC, dsPICDEM.net, ECONOMONITOR, FanSense, FlexROM, fuzzyLAB, In-Circuit Serial Programming, ICSP, ICEPIC, microPort, Migratable Memory, MPASM, MPLIB, MPLINK, MPSIM, MXLAB, PICC, PICDEM, PICDEM.net, rfPIC, Select Mode and Total Endurance are trademarks of Microchip Technology Incorporated in the U.S.A.

Serialized Quick Turn Programming (SQTP) is a service mark of Microchip Technology Incorporated in the U.S.A.

All other trademarks mentioned herein are property of their respective companies.

© 2002, Microchip Technology Incorporated, Printed in the U.S.A., All Rights Reserved.

 Printed on recycled paper.

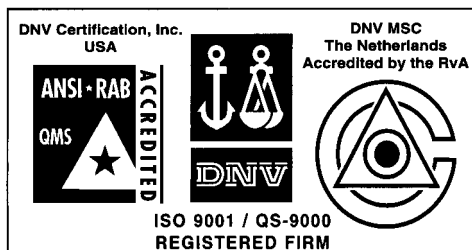

Microchip received QS-9000 quality system certification for its worldwide headquarters, design and wafer fabrication facilities in Chandler and Tempe, Arizona in July 1999 and Mountain View, California in March 2002. The Company's quality system processes and procedures are QS-9000 compliant for its PICmicro® 8-bit MCUs, KEELOQ® code hopping devices, Serial EEPROMs, microperipherals, non-volatile memory and analog products. In addition, Microchip's quality system for the design and manufacture of development systems is ISO 9001 certified.



MICROCHIP

WORLDWIDE SALES AND SERVICE

AMERICAS

Corporate Office

2355 West Chandler Blvd.
Chandler, AZ 85224-6199
Tel: 480-792-7200 Fax: 480-792-7277
Technical Support: 480-792-7627
Web Address: <http://www.microchip.com>

Rocky Mountain

2355 West Chandler Blvd.
Chandler, AZ 85224-6199
Tel: 480-692-7966 Fax: 480-792-4338

Atlanta

500 Sugar Mill Road, Suite 200B
Atlanta, GA 30350
Tel: 770-640-0034 Fax: 770-640-0307

Boston

2 Lan Drive, Suite 120
Westford, MA 01886
Tel: 978-692-3848 Fax: 978-692-3821

Chicago

333 Pierce Road, Suite 180
Itasca, IL 60143
Tel: 630-285-0071 Fax: 630-285-0075

Dallas

4570 Westgrove Drive, Suite 160
Addison, TX 75001
Tel: 972-818-7423 Fax: 972-818-2924

Detroit

Tri-Atria Office Building
32255 Northwestern Highway, Suite 190
Farmington Hills, MI 48334
Tel: 248-538-2250 Fax: 248-538-2260

Kokomo

2767 S. Albright Road
Kokomo, Indiana 46902
Tel: 765-864-8360 Fax: 765-864-8387

Los Angeles

18201 Von Karman, Suite 1090
Irvine, CA 92612
Tel: 949-263-1888 Fax: 949-263-1338

New York

150 Motor Parkway, Suite 202
Hauppauge, NY 11788
Tel: 631-273-5305 Fax: 631-273-5335

San Jose

Microchip Technology Inc.
2107 North First Street, Suite 590
San Jose, CA 95131
Tel: 408-436-7950 Fax: 408-436-7955

Toronto

6285 Northam Drive, Suite 108
Mississauga, Ontario L4V 1X5, Canada
Tel: 905-673-0699 Fax: 905-673-6509

ASIA/PACIFIC

Australia

Microchip Technology Australia Pty Ltd
Suite 22, 41 Rawson Street
Epping 2121, NSW
Australia
Tel: 61-2-9868-6733 Fax: 61-2-9868-6755

China - Beijing

Microchip Technology Consulting (Shanghai)
Co., Ltd., Beijing Liaison Office
Unit 915
Bei Hai Wan Tai Bldg.
No. 6 Chaoyangmen Beidajie
Beijing, 100027, No. China
Tel: 86-10-85282100 Fax: 86-10-85282104

China - Chengdu

Microchip Technology Consulting (Shanghai)
Co., Ltd., Chengdu Liaison Office
Rm. 2401, 24th Floor,
Ming Xing Financial Tower
No. 88 TIDU Street
Chengdu 610016, China
Tel: 86-28-86766200 Fax: 86-28-86766599

China - Fuzhou

Microchip Technology Consulting (Shanghai)
Co., Ltd., Fuzhou Liaison Office
Unit 28F, World Trade Plaza
No. 71 Wusi Road
Fuzhou 350001, China
Tel: 86-591-7503506 Fax: 86-591-7503521

China - Shanghai

Microchip Technology Consulting (Shanghai)
Co., Ltd.
Room 701, Bldg. B
Far East International Plaza
No. 317 Xian Xia Road
Shanghai, 200051
Tel: 86-21-6275-5700 Fax: 86-21-6275-5060

China - Shenzhen

Microchip Technology Consulting (Shanghai)
Co., Ltd., Shenzhen Liaison Office
Rm. 1315, 13/F, Shenzhen Kerry Centre,
Renminnan Lu
Shenzhen 518001, China
Tel: 86-755-2350361 Fax: 86-755-2366086

China - Hong Kong SAR

Microchip Technology Hongkong Ltd.
Unit 901-6, Tower 2, Metroplaza
223 Hing Fong Road
Kwai Fong, N.T., Hong Kong
Tel: 852-2401-1200 Fax: 852-2401-3431

India

Microchip Technology Inc.
India Liaison Office
Divyasree Chambers
1 Floor, Wing A (A3/A4)
No. 11, O'Shaugnessey Road
Bangalore, 560 025, India
Tel: 91-80-2290061 Fax: 91-80-2290062

Japan

Microchip Technology Japan K.K.
Benex S-1 6F
3-18-20, Shinyokohama
Kohoku-Ku, Yokohama-shi
Kanagawa, 222-0033, Japan
Tel: 81-45-471-6166 Fax: 81-45-471-6122

Korea

Microchip Technology Korea
168-1, Youngbo Bldg. 3 Floor
Samsung-Dong, Kangnam-Ku
Seoul, Korea 135-882
Tel: 82-2-554-7200 Fax: 82-2-558-5934

Singapore

Microchip Technology Singapore Pte Ltd.
200 Middle Road
#07-02 Prime Centre
Singapore, 188980
Tel: 65-6334-8870 Fax: 65-6334-8850

Taiwan

Microchip Technology (Barbados) Inc.,
Taiwan Branch
11F-3, No. 207
Tung Hua North Road
Taipei, 105, Taiwan
Tel: 886-2-2717-7175 Fax: 886-2-2545-0139

EUROPE

Austria

Microchip Technology Austria GmbH
Durisolstrasse 2
A-4600 Wels
Austria
Tel: 43-7242-2244-399
Fax: 43-7242-2244-393

Denmark

Microchip Technology Nordic ApS
Regus Business Centre
Lautrup høj 1-3
Ballerup DK-2750 Denmark
Tel: 45 4420 9895 Fax: 45 4420 9910

France

Microchip Technology SARL
Parc d'Activite du Moulin de Massy
43 Rue du Saule Trapu
Batiment A - 1er Etage
91300 Massy, France
Tel: 33-1-69-53-63-20 Fax: 33-1-69-30-90-79

Germany

Microchip Technology GmbH
Gustav-Heinemann Ring 125
D-81739 Munich, Germany
Tel: 49-89-627-144 0 Fax: 49-89-627-144-44

Italy

Microchip Technology SRL
Centro Direzionale Colleoni
Palazzo Taurus 1 V. Le Colleoni 1
20041 Agrate Brianza
Milan, Italy
Tel: 39-039-65791-1 Fax: 39-039-6899883

United Kingdom

Microchip Ltd.
505 Eskdale Road
Winkers Triangle
Wokingham
Berkshire, England RG41 5TU
Tel: 44 118 921 5869 Fax: 44-118 921-5820

05/16/02