

Stepper Motor Control Using the PIC16F684

Author: Reston Condit
Microchip Technology Inc.

INTRODUCTION

This application note describes how to drive a bipolar stepping motor with the PIC16F684. The Enhanced Capture Compare PWM (ECCP) module is used to implement a microstepping technique known as high-torque microstepping. The microcontroller's 8 MHz internal oscillator allows the signals generated by the ECCP module to achieve frequencies above the audible range.


Note: Please refer to AN907: *Stepping Motor Fundamentals* for information on the types of stepper motors, microstepping and current limiting techniques.

MICROSTEPPING

Single stepping, or turning a stepping motor at its rated step size, results in less than smooth movement. Microstepping is a technique used to smooth the motor's movement between full steps and to improve the step resolution of the motor. Microstepping also improves the efficiency of the system, because the current in the windings of the motor is manipulated in a controlled manner rather than being turned on and off abruptly.

A microstepping technique known as high torque microstepping alternately varies the current in the two windings of a stepping motor. Figure 1 shows a graph of the current in the windings vs. angular position using this technique.

FIGURE 1: HIGH TORQUE MICROSTEPPING

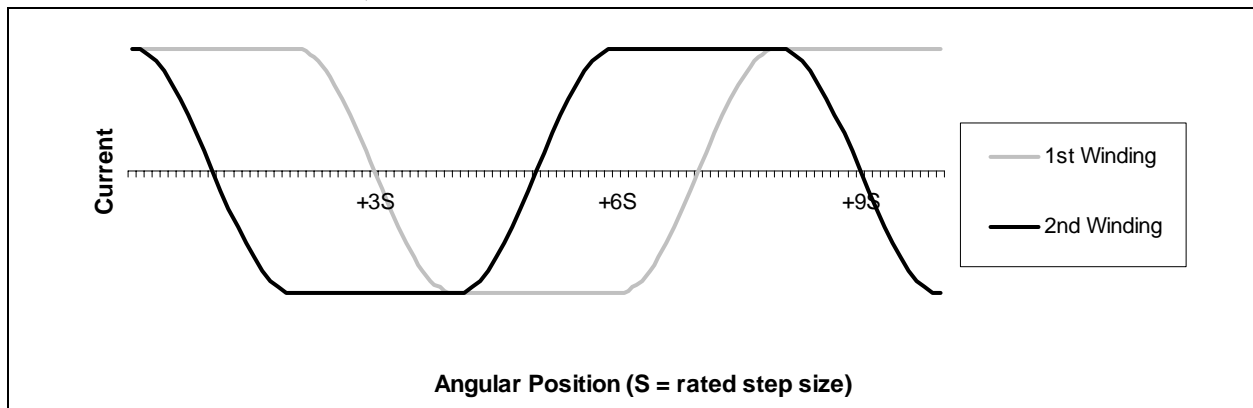

A brief description of what is happening is that one winding is powered while the current in the other winding is gradually dropped to zero, reversed, and then ramped up again. This sequence is then repeated for the other winding. Note that the transition between a winding being energized in one direction and then energized in the other direction has a sinusoidal shape (refer to Figure 1). This shape gives the smoothest transition between the motor's rated step increments (i.e., 7.5 degrees). The way this shape is achieved using a microcontroller is through the use of pulse-width modulation. Modulating the input to the drive circuitry for a particular winding will result in a current that is proportional to the duty cycle of the modulated waveform.

For instance, if a 5V stepping motor is rated at 1 amp, then modulating a 5V supply across the winding at 50% will result in a current of 1/2 amp (assuming a low inductance motor). Equation 1 shows this relationship:

EQUATION 1:

$$I = D \times I_{MAX}$$

where I_{MAX} is the rated current of the motor and D is the duty cycle.

AN906

In order to achieve the sinusoidal transition from a positive to negative charge in a winding, numerous microsteps are needed. The number of microsteps typically ranges from 4 to 32 microsteps per rated step size. Rather than calculating the duty cycle for a particular microstep on the fly, a duty cycle look-up table is implemented in firmware. The number of table values is equal to the number of steps desired for a particular microstepping sequence. Equation 2 is used to obtain the duty cycle values for the top half of the table. The second half of the table is simply the top half in reverse order.

EQUATION 2:

$$D(\text{step number}) = \cos((\text{step number} \times \pi) / ((\text{number of steps} + 1)) \times ((2^{\text{bits resolution}}) - 1))$$

Using Equation 2, the following duty cycle values were calculated for a 16 microsteps per full step sequence using an 8-bit resolution PWM waveform:

TABLE 1: DUTY CYCLE VALUES FOR MICROSTEPPING

Step Number	D	Step Number	D
1	251	9	24
2	238	10	70
3	217	11	114
4	188	12	154
5	154	13	188
6	114	14	217
7	70	15	238
8	24	16	251

PWM Generation Using the ECCP Module


The ECCP module on the PIC16F684 is well suited for generating the PWM signal required for microstepping. The module is capable of generating a 10-bit resolution PWM waveform at frequencies ranging up to 7.81 kHz using the microcontroller's 8 MHz internal oscillator. Higher frequencies are more practical in motor control applications because a motor will typically produce undesirable audible noise at frequencies less than 16 kHz. Only 8-bit resolution is needed for this application, which means frequencies up to 31.2 kHz can be achieved with the ECCP module.

The ECCP module has four modes of operation:

- 1) Single Output
- 2) Half-bridge Output
- 3) Full-bridge Forward Output
- 4) Full-bridge Reverse Output

In Half-bridge mode, the module modulates two pins simultaneously, pins P1A and P1B. For this application, these two outputs are used to drive the two windings of a stepping motor. Only one pin is set active at a time. Enabling and disabling one pin or the other is done by modifying the TRISC register. The following circuit diagram shows how these pins are connected to a bipolar drive circuit.

FIGURE 2: BIPOLAR DRIVE CIRCUIT

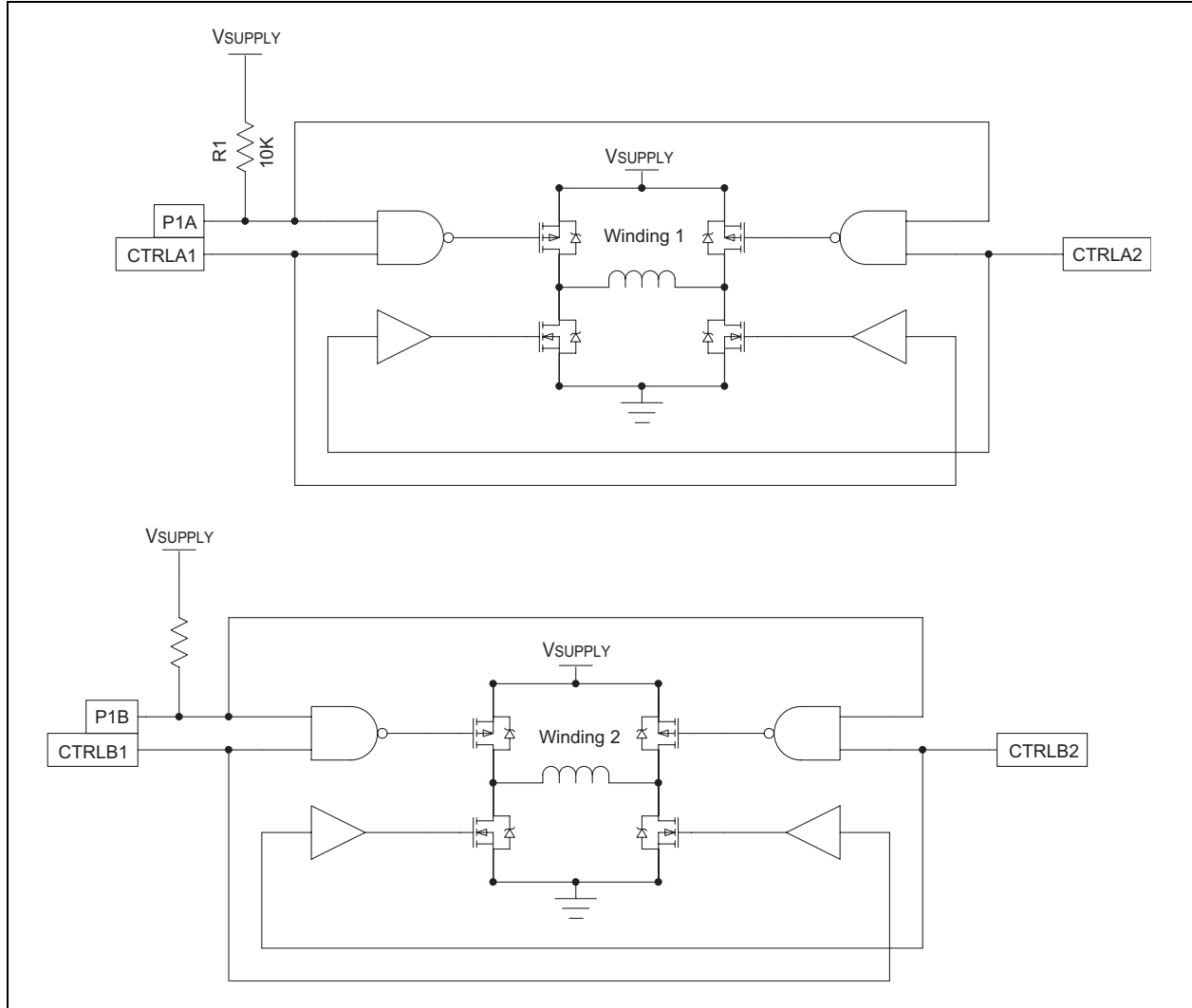

AN906

Note the pull-up resistor on pins P1A and P1B. These resistors clamp the respective line high when the pin is tristated. It is important that the non-modulated line be clamped high so that the NAND gates on either end of the winding can turn on the adjacent MOSFET when the respective control line is enabled.

The ECCP module is set up so that the waveforms on pins P1A and P1B are identical. This is done by configuring the CCP1CON register so that P1A is active high and P1B is active low. With no dead band delay, these pins will behave identically. Configuring the module in this way enables each winding control block to use the same duty cycle look-up table values for its transition sequence. The following table shows all eight winding states.

TABLE 2: WINDING STATES

STATE	0	1	2	3	4	5	6	7
Winding 1 Polarity	+ to 0	0 to -	-	-	- to 0	0 to +	+	+
Winding 2 Polarity	+	+	+ to 0	0 to -	-	-	- to 0	0 to +
P1A Duty Cycle	100% to 0	0 to 100%	100%*	100%*	100% to 0	0 to 100%	100%*	100%*
P1B Duty Cycle	100%*	100%*	100% to 0	0 to 100%	100%*	100%*	100% to 0	0 to 100%
TRISC, P1A	0	0	1	1	0	0	1	1
TRISC, P1B	1	1	0	0	1	1	0	0
CTRLA1	1	0	0	0	0	1	1	1
CTRLA2	0	1	1	1	1	0	0	0
CTRLB1	1	1	1	0	0	0	0	1
CTRLB2	0	0	0	1	1	1	1	0

* Pin is tristated and the pull-up resistor is clamping the line high.

In states 0, 2, 4 and 6, the first half of the duty cycle sine look-up table (decreasing values) is referenced. In states 1, 3, 5 and 7, the second half of the duty cycle sine look-up table (increasing values) is referenced.

EXAMPLE APPLICATION

This example application demonstrates how to drive a 3.6 degree-per-step stepping motor. The motor used is a bipolar stepping motor rated to draw 1/2 amp at 12V.

Hardware

Appendix A shows a schematic for the example application included with this application note. The drive circuit is composed of four Fairchild® Semiconductor half-bridge MOSFET ICs (part number FDC6420C). Two Microchip logic-input CMOS quad drivers are used to drive the MOSFET ICs and to provide the logic necessary for the implementation described in this application note. The TC4467 has four on-chip NAND gates and the TC4468 has four on-chip AND gates. The inputs to each of the AND gates on the TC4468 are tied together because this IC is used as a non-inverting quad MOSFET driver for this implementation.

Firmware

A flowchart illustrating the microstepping firmware implementation of this example is in Appendix B. The source code for this application note is included with this application note on Microchip's web site, www.microchip.com.

Operation

There are five modes of operation in the example that are sequenced through with single button presses. The modes of operation are:

1. Motor Off
2. Single-step mode
3. Half-step mode
4. Microstep mode
5. Position Control mode

In modes 2, 3 and 4, the speed of the stepping motor is controlled by turning the potentiometer. Mode 5 uses the potentiometer as a position dial. Turning the potentiometer will cause the motor to microstep in one direction or the other for a distance proportional to the distance the potentiometer was turned.

CONCLUSION


The PIC16F684 has an ideal set of features for low-cost stepper motor control. High torque microstepping can be implemented using its ECCP module and very few external logic components. The PIC16F684's 8 MHz internal oscillator will allow the ECCP module to drive the transitioning phase of the bipolar stepping motor at a frequency of 31.2 kHz and still provide 8-bits of duty cycle resolution. This frequency effectively eliminates unwanted audible noise generated by the motor.

REFERENCES


AN907: "Stepper Motor Fundamentals"

AN906


APPENDIX A:

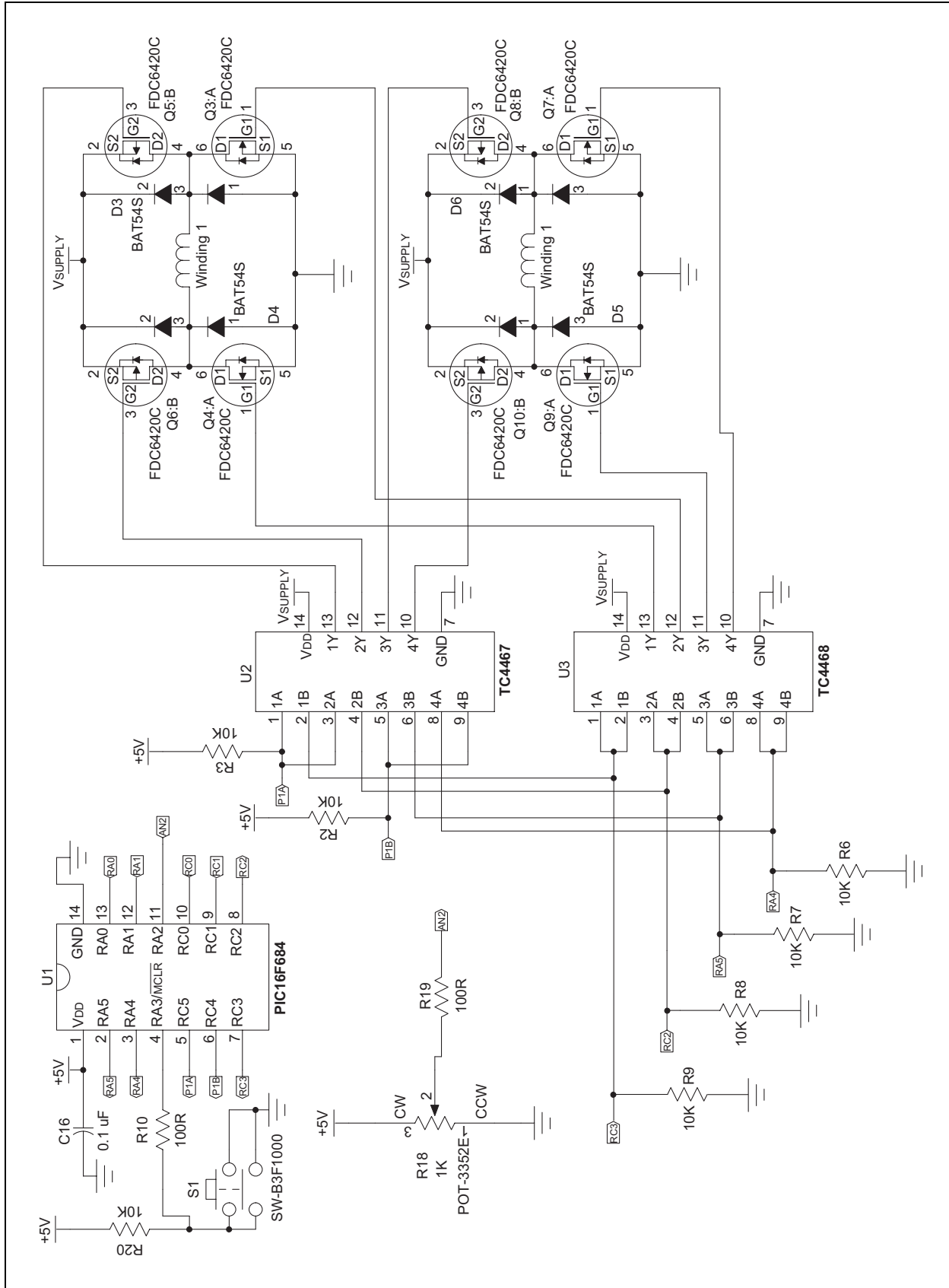


APPENDIX A: (CONTINUED)

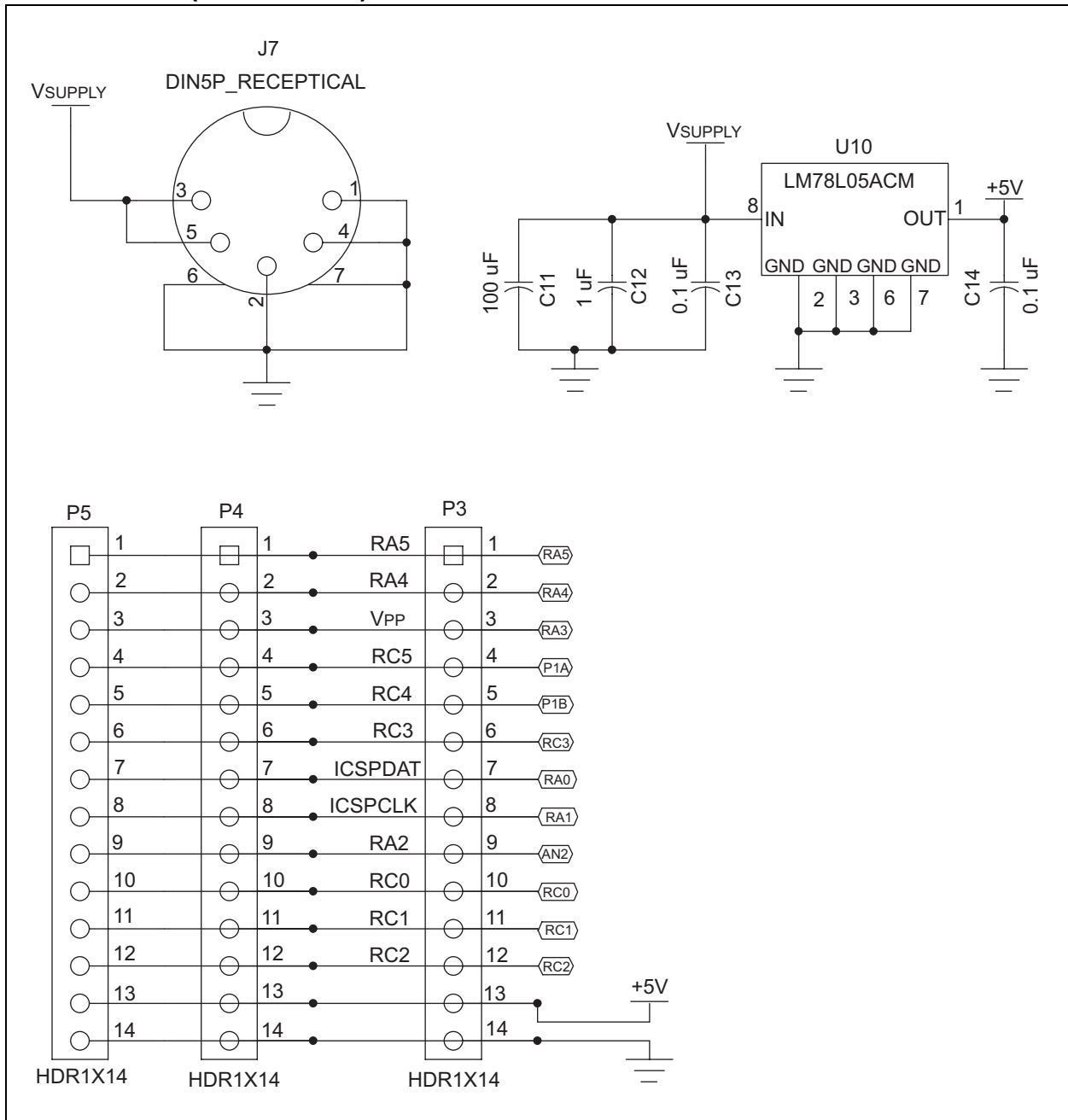


APPENDIX B:

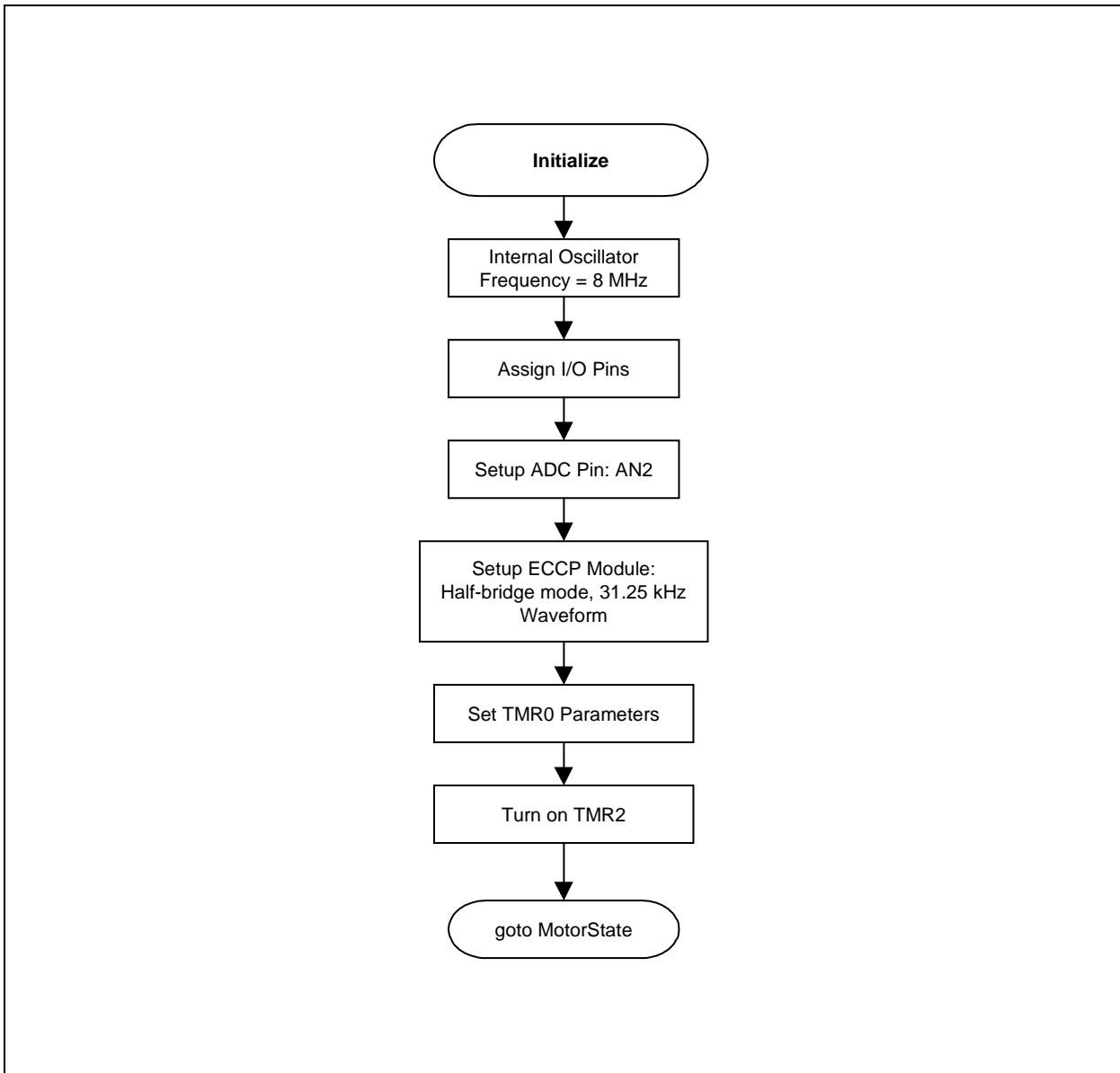

APPENDIX B: (CONTINUED)

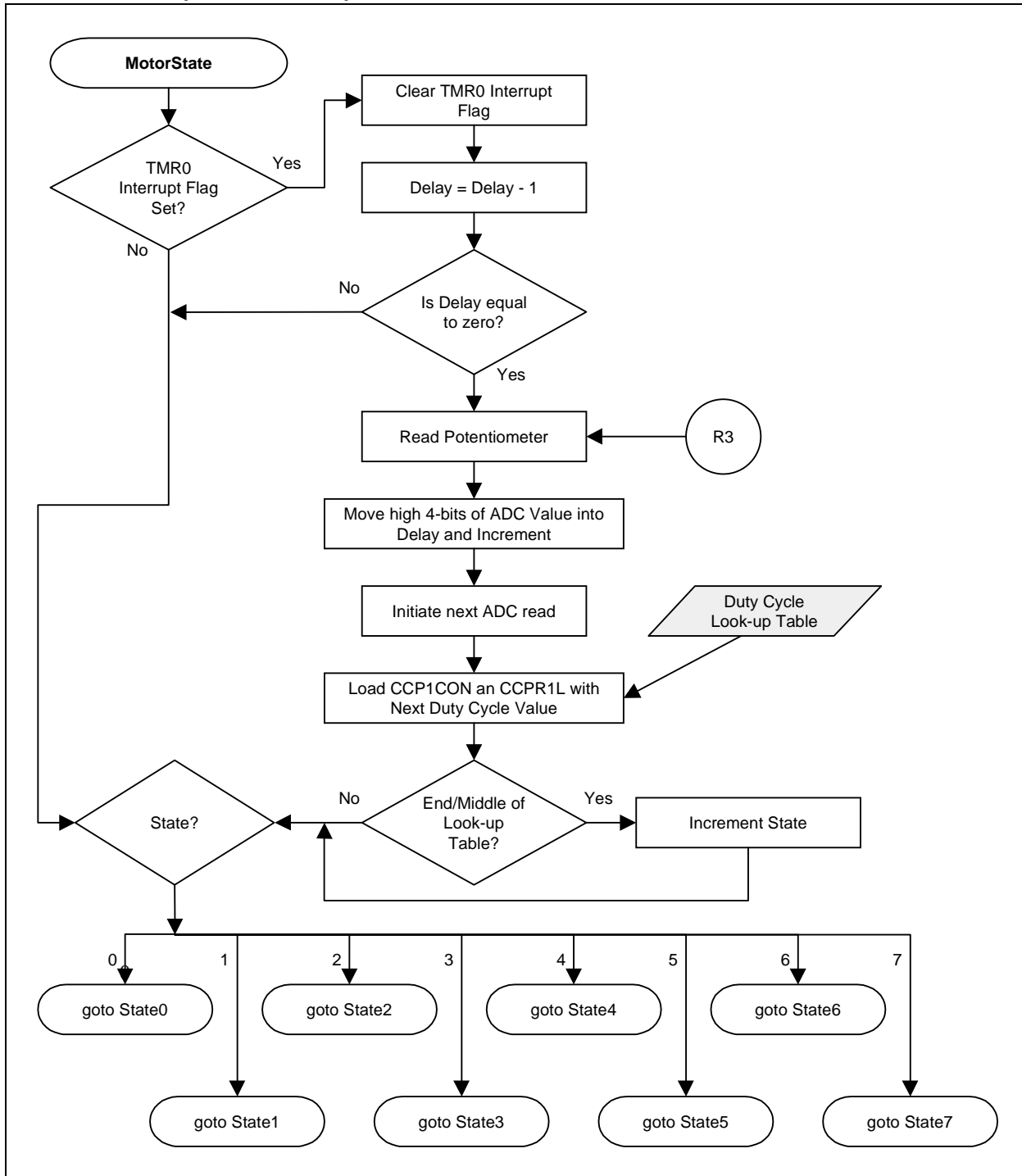

APPENDIX B: (CONTINUED)

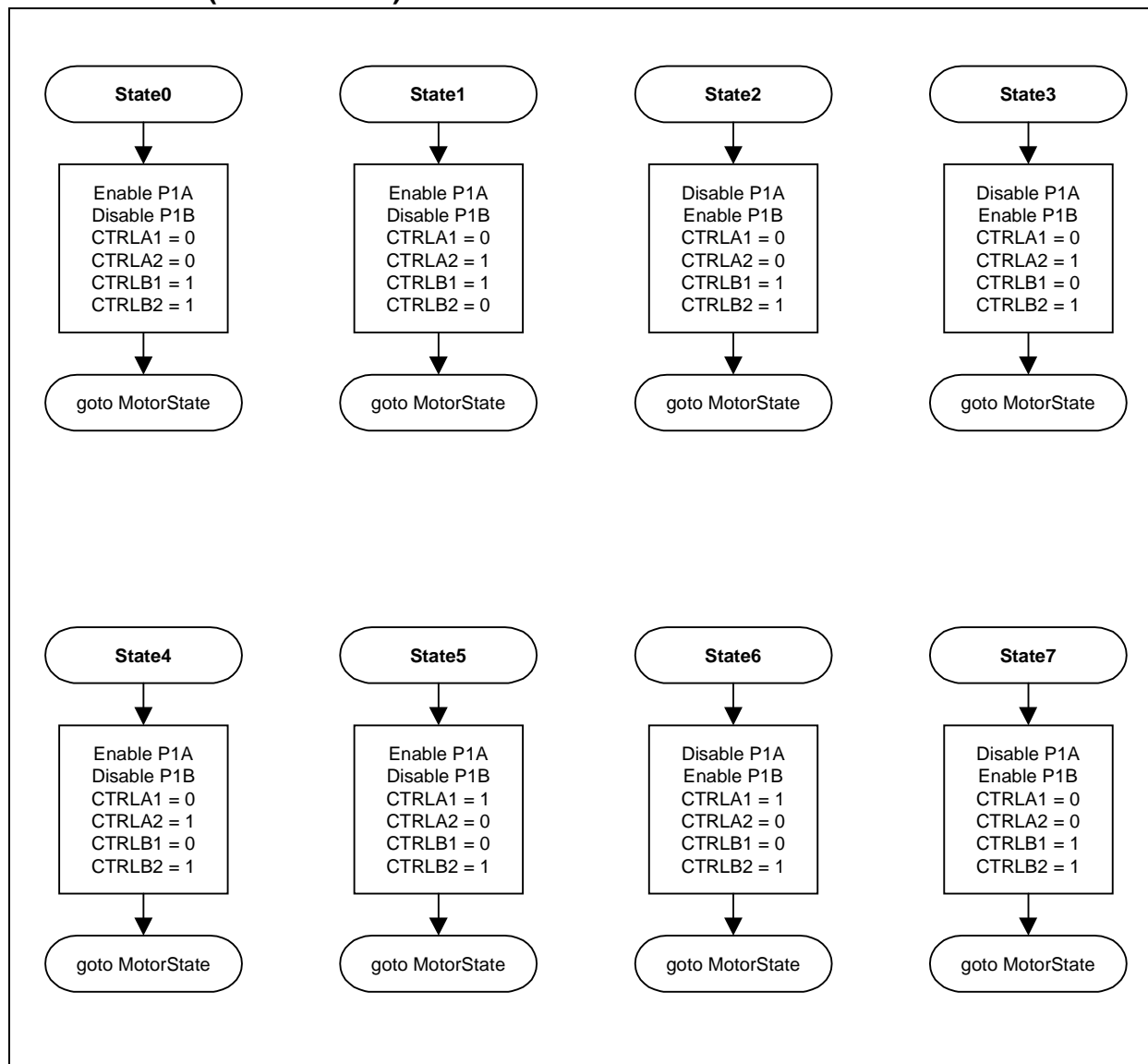

Note the following details of the code protection feature on Microchip devices:

- Microchip products meet the specification contained in their particular Microchip Data Sheet.
- Microchip believes that its family of products is one of the most secure families of its kind on the market today, when used in the intended manner and under normal conditions.
- There are dishonest and possibly illegal methods used to breach the code protection feature. All of these methods, to our knowledge, require using the Microchip products in a manner outside the operating specifications contained in Microchip's Data Sheets. Most likely, the person doing so is engaged in theft of intellectual property.
- Microchip is willing to work with the customer who is concerned about the integrity of their code.
- Neither Microchip nor any other semiconductor manufacturer can guarantee the security of their code. Code protection does not mean that we are guaranteeing the product as "unbreakable."

Code protection is constantly evolving. We at Microchip are committed to continuously improving the code protection features of our products. Attempts to break Microchip's code protection feature may be a violation of the Digital Millennium Copyright Act. If such acts allow unauthorized access to your software or other copyrighted work, you may have a right to sue for relief under that Act.

Information contained in this publication regarding device applications and the like is intended through suggestion only and may be superseded by updates. It is your responsibility to ensure that your application meets with your specifications. No representation or warranty is given and no liability is assumed by Microchip Technology Incorporated with respect to the accuracy or use of such information, or infringement of patents or other intellectual property rights arising from such use or otherwise. Use of Microchip's products as critical components in life support systems is not authorized except with express written approval by Microchip. No licenses are conveyed, implicitly or otherwise, under any intellectual property rights.

Trademarks

The Microchip name and logo, the Microchip logo, Accuron, dsPIC, KEELoQ, MPLAB, PIC, PICmicro, PICSTART, PRO MATE, PowerSmart and rPIC are registered trademarks of Microchip Technology Incorporated in the U.S.A. and other countries.


AmpLab, FilterLab, microID, MXDEV, MXLAB, PICMASTER, SEEVAL, SmartShunt and The Embedded Control Solutions Company are registered trademarks of Microchip Technology Incorporated in the U.S.A.

Application Maestro, dsPICDEM, dsPICDEM.net, dsPICworks, ECAN, ECONOMONITOR, FanSense, FlexROM, fuzzyLAB, In-Circuit Serial Programming, ICSP, ICEPIC, Migratable Memory, MPASM, MPLIB, MPLINK, MPSIM, PICKit, PICDEM, PICDEM.net, PICtail, PowerCal, PowerInfo, PowerMate, PowerTool, rLAB, Select Mode, SmartSensor, SmartTel and Total Endurance are trademarks of Microchip Technology Incorporated in the U.S.A. and other countries.

Serialized Quick Turn Programming (SQTP) is a service mark of Microchip Technology Incorporated in the U.S.A.

All other trademarks mentioned herein are property of their respective companies.

© 2004, Microchip Technology Incorporated, Printed in the U.S.A., All Rights Reserved.

 Printed on recycled paper.

**QUALITY MANAGEMENT SYSTEM
CERTIFIED BY DNV
== ISO/TS 16949:2002 ==**

Microchip received ISO/TS-16949:2002 quality system certification for its worldwide headquarters, design and wafer fabrication facilities in Chandler and Tempe, Arizona and Mountain View, California in October 2003. The Company's quality system processes and procedures are for its PICmicro® 8-bit MCUs, KEELoQ® code hopping devices, Serial EEPROMs, microperipherals, nonvolatile memory and analog products. In addition, Microchip's quality system for the design and manufacture of development systems is ISO 9001:2000 certified.



WORLDWIDE SALES AND SERVICE

AMERICAS

Corporate Office

2355 West Chandler Blvd.
Chandler, AZ 85224-6199
Tel: 480-792-7200
Fax: 480-792-7277
Technical Support: 480-792-7627
Web Address: <http://www.microchip.com>

Atlanta

3780 Mansell Road, Suite 130
Alpharetta, GA 30022
Tel: 770-640-0034
Fax: 770-640-0307

Boston

2 Lan Drive, Suite 120
Westford, MA 01886
Tel: 978-692-3848
Fax: 978-692-3821

Chicago

333 Pierce Road, Suite 180
Itasca, IL 60143
Tel: 630-285-0071
Fax: 630-285-0075

Dallas

4570 Westgrove Drive, Suite 160
Addison, TX 75001
Tel: 972-818-7423
Fax: 972-818-2924

Detroit

Tri-Atria Office Building
32255 Northwestern Highway, Suite 190
Farmington Hills, MI 48334
Tel: 248-538-2250
Fax: 248-538-2260

Kokomo

2767 S. Albright Road
Kokomo, IN 46902
Tel: 765-864-8360
Fax: 765-864-8387

Los Angeles

18201 Von Karman, Suite 1090
Irvine, CA 92612
Tel: 949-263-1888
Fax: 949-263-1338

San Jose

1300 Terra Bella Avenue
Mountain View, CA 94043
Tel: 650-215-1444
Fax: 650-961-0286

Toronto

6285 Northam Drive, Suite 108
Mississauga, Ontario L4V 1X5, Canada
Tel: 905-673-0699
Fax: 905-673-6509

ASIA/PACIFIC

Australia

Suite 22, 41 Rawson Street
Epping 2121, NSW
Australia
Tel: 61-2-9868-6733
Fax: 61-2-9868-6755

China - Beijing

Unit 706B
Wan Tai Bei Hai Bldg.
No. 6 Chaoyangmen Bei Str.
Beijing, 100027, China
Tel: 86-10-85282100
Fax: 86-10-85282104

China - Chengdu

Rm. 2401-2402, 24th Floor,
Ming Xing Financial Tower
No. 88 TIDU Street
Chengdu 610016, China
Tel: 86-28-86766200
Fax: 86-28-86766599

China - Fuzhou

Unit 28F, World Trade Plaza
No. 71 Wusi Road
Fuzhou 350001, China
Tel: 86-591-7503506
Fax: 86-591-7503521

China - Hong Kong SAR

Unit 901-6, Tower 2, Metroplaza
223 Hing Fong Road
Kwai Fong, N.T., Hong Kong
Tel: 852-2401-1200
Fax: 852-2401-3431

China - Shanghai

Room 701, Bldg. B
Far East International Plaza
No. 317 Xian Xia Road
Shanghai, 200051
Tel: 86-21-6275-5700
Fax: 86-21-6275-5060

China - Shenzhen

Rm. 1812, 18/F, Building A, United Plaza
No. 5022 Binhe Road, Futian District
Shenzhen 518033, China
Tel: 86-755-82901380
Fax: 86-755-8295-1393

China - Shunde

Room 401, Hongjian Building, No. 2
Fengxiangnan Road, Ronggui Town, Shunde
District, Foshan City, Guangdong 528303, China
Tel: 86-757-28395507 Fax: 86-757-28395571

China - Qingdao

Rm. B505A, Fullhope Plaza,
No. 12 Hong Kong Central Rd.
Qingdao 266071, China
Tel: 86-532-5027355 Fax: 86-532-5027205

India

Divyasree Chambers
1 Floor, Wing A (A3/A4)
No. 11, O'Shaughnessy Road
Bangalore, 560 025, India
Tel: 91-80-22290061 Fax: 91-80-22290062

Japan

Benex S-1 6F
3-18-20, Shinyokohama
Kohoku-Ku, Yokohama-shi
Kanagawa, 222-0033, Japan
Tel: 81-45-471- 6166 Fax: 81-45-471-6122

Korea

168-1, Youngbo Bldg. 3 Floor
Samsung-Dong, Kangnam-Ku
Seoul, Korea 135-882
Tel: 82-2-554-7200 Fax: 82-2-558-5932 or
82-2-558-5934

Singapore

200 Middle Road
#07-02 Prime Centre
Singapore, 188980
Tel: 65-6334-8870 Fax: 65-6334-8850

Taiwan

Kaohsiung Branch
30F - 1 No. 8
Min Chuan 2nd Road
Kaohsiung 806, Taiwan
Tel: 886-7-536-4818
Fax: 886-7-536-4803

Taiwan

Taiwan Branch
11F-3, No. 207
Tung Hua North Road
Taipei, 105, Taiwan
Tel: 886-2-2717-7175 Fax: 886-2-2545-0139

EUROPE

Austria

Durisolstrasse 2
A-4600 Wels
Austria
Tel: 43-7242-2244-399
Fax: 43-7242-2244-393

Denmark

Regus Business Centre
Lautrup høj 1-3
Ballerup DK-2750 Denmark
Tel: 45-4420-9895 Fax: 45-4420-9910

France

Parc d'Activite du Moulin de Massy
43 Rue du Saule Trapu
Batiment A - Ier Etage
91300 Massy, France
Tel: 33-1-69-53-63-20
Fax: 33-1-69-30-90-79

Germany

Steinheilstrasse 10
D-85737 Ismaning, Germany
Tel: 49-89-627-144-0
Fax: 49-89-627-144-44

Italy

Via Quasimodo, 12
20025 Legnano (MI)
Milan, Italy
Tel: 39-0331-742611
Fax: 39-0331-466781

Netherlands

P. A. De Biesbosch 14
NL-5152 SC Drunen, Netherlands
Tel: 31-416-690399
Fax: 31-416-690340

United Kingdom

505 Eskdale Road
Winnersh Triangle
Wokingham
Berkshire, England RG41 5TU
Tel: 44-118-921-5869
Fax: 44-118-921-5820

02/17/04