

Simple Synchronous Buck Converter Design - MCP1612

Author: *Cliff Ellison*
Microchip Technology Inc.

INTRODUCTION

The density of portable electronic equipment requires the design engineer to pay particular attention to a number of important design parameters. For the power conversion circuitry, two of these parameters are the efficiency and the total circuitry footprint. Keeping the efficiency high extends battery life and controls the temperature rise of the equipment. Limiting the circuitry footprint helps minimize the size of the Printed Circuit Board (PCB) and, ultimately, the total cost of the device.

The MCP1612 is an ideal choice for such a design. Since both the switching and synchronous MOSFETs are internal and switching is 1.4 MHz, the inductor, input and output capacitor size is minimized. The output voltage is set by using a simple resistor divider, with a high-bandwidth loop being accomplished by a series resistor capacitor to ground. Efficiencies of 90% and a typical shutdown current of 0.01 μ A help to extend battery life.

This Application Note contains all of the information needed to design a synchronous buck converter using the MCP1612. It also contains a real-world design example with measured laboratory data.

POWER COMPONENT DESIGN

The design of the power components for the MCP1612 is made easier because the switching and synchronous MOSFETs are internal. The output filter inductor and capacitor are the only two power components that need to be selected.

Buck Inductor

The inductance and current-carrying capability of the buck inductor or output filter inductor is very easy and straightforward to calculate. The size of the inductor is selected such that a certain ripple current is achieved. As will be shown later, the amount of allowable ripple current determines the amount of output ripple voltage present at the converter load.

Solving the standard inductor equation for inductor ripple current (ΔI_L) yields:

$$\Delta I_L = \frac{V_L}{L} \times \Delta T$$

Where:

V_L = voltage across the inductor ($V_{IN} - V_{OUT}$)

L = value of inductance

ΔT = on-time of switching MOSFET

When operating in Continuous Conduction mode (meaning the inductor current never goes to zero), the on-time (ΔT) of the P-channel MOSFET is determined by multiplying the duty cycle by the switching period. Using the output voltage (V_{OUT}) to input voltage (V_{IN}) relationship, the duty cycle yields:

$$DutyCycle = \frac{V_{OUT}}{V_{IN}}$$

Therefore, it follows that ΔT is:

$$\Delta T = DutyCycle \times \frac{1}{F_{SW}}$$

Where:

F_{SW} = switching frequency

Most inductor manufacturers specify the peak current that an inductor can support before the inductance drops by a given percentage. ΔI_L should be re-evaluated if the inductance drops by a large percentage because of its peak current. The peak inductor current is calculated by:

$$I_{L(PEAK)} = I_{OUT(MAX)} + \left(\frac{1}{2} \times \Delta I_L\right)$$

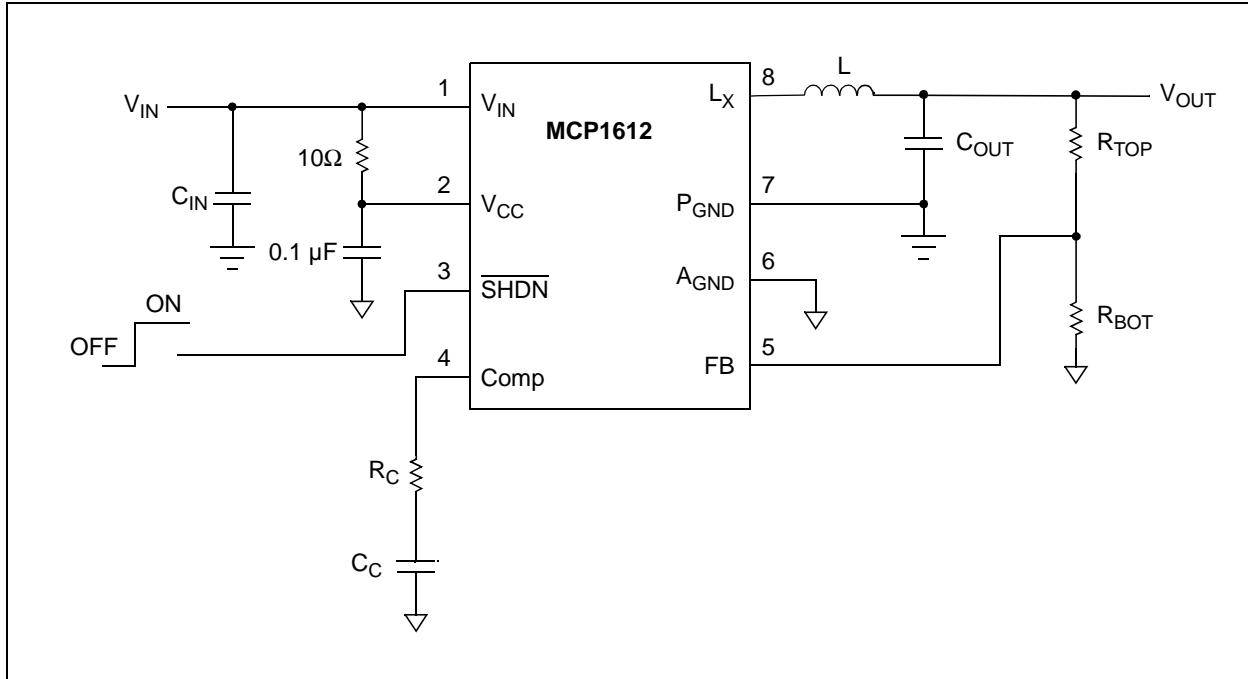


FIGURE 1: Typical Application Schematic.

Output Capacitor

The MCP1612 is designed to allow the use of ceramic, tantalum or aluminum electrolytic capacitors as output filter capacitors. The output capacitor is chosen to meet the output ripple specification and to provide storage for load transients. The value of the capacitance is not the only parameter of the capacitor that determines ripple voltage. All capacitors have an Equivalent Series Resistance (ESR) that contributes to the ripple voltage. Ceramic capacitors have the lowest ESR, but increase in cost with higher capacitance values. Aluminum electrolytic and tantalum capacitors are relatively inexpensive in higher capacitance values, but they also have a much higher ESR.

Solving the standard capacitor equation for the output ripple voltage (ΔV_C) yields:

$$\Delta V_C = \frac{I_C \times \Delta T}{C_{OUT}}$$

Where:

I_C = peak-to-peak ripple current

ΔT = on-time of P-channel MOSFET

ΔV_C = output ripple voltage

As previously stated, the capacitor ESR also contributes to the output ripple voltage. This ripple voltage ($V_{ESRRIPPLE}$) is defined as:

$$V_{ESRRIPPLE} = I_C \times ESR$$

SETTING OUTPUT VOLTAGE

The output voltage of the MCP1612 is easily set by the use of an external resistor divider network. The divided-down output voltage is internally compared to a 0.8V reference. The output voltage can be set to any voltage between 0.8V and V_{IN} .

A resistor value of 200 k Ω or lower is recommended for R_{BOT} , the lower end of the resistor divider. If a higher-value resistor is used, the circuit will become more susceptible to noise at the feedback pin. The top resistor (R_{TOP}) of the resistor divider is easily calculated by using the following equation:

$$R_{TOP} = R_{BOT} \times \left(\frac{V_{OUT}}{V_{FB}} - 1 \right)$$

Where:

V_{OUT} = desired output voltage

V_{FB} = MCP1612 internal reference voltage

R_{TOP} = top resistor value

R_{BOT} = bottom resistor value

INPUT AND V_{CC} FILTER

Input Capacitor

The input current in a buck topology is pulled from the source and input capacitor in pulses. The size of the input capacitor determines the amount of peak current that is pulled from the source. The input capacitor also reduces the amount of voltage ripple present at the input to the converter.

The value of the input capacitor can be calculated the same way as the output capacitor. A capacitance value is chosen and the corresponding ripple voltage is calculated. For most applications, a 10 μF ceramic capacitor connected between the V_{IN} and P_{GND} pins of the MCP1612 is recommended to filter the current pulses. A lower-value capacitor can be used in applications that have a low source impedance. Ceramic or aluminum electrolytic capacitors can be used, but the capacitor ripple current rating should not be exceeded.

V_{CC} Filter

The V_{CC} pin provides bias for the internal analog circuitry. It is important that this voltage stay free of line transients and, therefore, it is recommended that a separate filter be used for this voltage. Placing a 10 Ω resistor between V_{IN} and AV_{CC} and a 0.1 μF capacitor between V_{CC} and $AGND$ is sufficient to filter any high-frequency line transients on V_{IN} caused by the MCP1612 switching.

COMPENSATION COMPONENTS

The MCP1612 is a peak current mode buck controller and, therefore, it does not exhibit the second-order effects associated with the L-C output filter as with a voltage mode controller. Since a transconductance error amplifier is used, a simple resistor and capacitor connected from the output of the amplifier to ground is all that is needed to provide a stable, high-bandwidth control loop.

Table 1 shows values for R_C and C_C for standard circuit parameters. The values provide a stable control loop over the entire MCP1612 input voltage, output voltage and output current range.

TABLE 1: GENERAL CIRCUIT PARAMETERS

L	C_{OUT}	R_C	C_C
3.3 μH	10.0 μF	22 $\text{k}\Omega$	1000 pF
2.2 μH	4.7 μF	12 $\text{k}\Omega$	1000 pF

JUNCTION TEMPERATURE RISE

The MCP1612 is packaged in both an 8-pin MSOP and a thermally-enhanced, 8-pin DFN. The junction temperature rise above ambient of the MCP1612 is determined by multiplying the internal power dissipation by the thermal resistance of the package as shown:

$$T_{RISE} = P_{INT} \times \theta_{JA}$$

Where:

P_{INT} = MCP1612 internal power dissipation

θ_{JA} = package thermal resistance

It is important to note that the package thermal resistance is specified for an assumed PCB layout consisting of four layers with 1 oz. copper on the internal layers, 2 oz. copper on the external layers and exposed vias connecting the layers. The thermal resistance will be higher for a PCB that is constructed with less layers, less copper weight or fewer vias.

It can be assumed that the difference between the input power (P_{IN}) and the output power (P_{OUT}) is the power lost in the MCP1612 (P_{INT}) and in the buck inductor, P_{IND} . Neglecting the small amount of core loss, the power lost in the buck inductor is defined by the following equation:

$$P_{IND} = I_{I(PEAK)}^2 \times R_{IND}$$

Where:

R_{IND} = inductor winding resistance

PORTABLE/LOAD-SHED APPLICATIONS

The switching frequency, efficiency, package size and extremely low shutdown current make the MCP1612 perfectly suited for portable applications or load-shed applications. Couple the 1.4 MHz switching frequency that allows the use of small inductors, and filter capacitors with the 8-pin MSOP or the space-saving 8-pin DFN package and a 1A buck converter that fits into the most space constrained designs is achievable.

When the MCP1612 is disabled by grounding the shutdown pin ($\overline{\text{SHDN}}$), the current draw is only 0.01 μA , typical. If the load cannot be shed, the quiescent current (I_Q ($I_{OUT} = 0 \text{ mA}$)) is only 5 mA, typical. Both of these low-current draw modes, along with the high efficiency, extend battery life.

PRACTICAL DESIGN EXAMPLE

A buck converter with the following design parameters will be designed using the MCP1612. A schematic of the circuit appears in Figure 1.

$$V_{IN} = 2.7V - 4.5V$$

$$V_{OUT} = 1.8V$$

$$V_{OUT_RIPPLE} < 15 \text{ mV}$$

$$I_{OUT} = 0 - 1A$$

The switching frequency (F_{SW}) of the MCP1612 is 1.4 MHz. The worst-case inductor ripple current is when V_{IN} is at its maximum. The inductor and output capacitor must be sized for this worst-case condition. Therefore:

$$\text{Duty Cycle} = \frac{1.8}{4.5} = 0.400$$

$$\Delta T = 0.40 * 1/1.4 \text{ MHz} = 286 \text{ ns}$$

Select $L = 3.3 \mu\text{H}$:

$$\Delta I_L = ((4.5-1.8)/3.3 \mu\text{H}) * 286 \text{ ns} = 234 \text{ mA}$$

$$I_{L(\text{PEAK})} = 1 + (1/2 * 234 \text{ mA}) = 1.12A$$

The $3.3 \mu\text{H}$ inductor yields an acceptable ripple current of about 20% at maximum I_{OUT} . The inductor must be able to withstand a peak current of 1.12A.

Using an output capacitor (C_{OUT}) of $10 \mu\text{F}$ yields an approximate output ripple voltage of:

$$\Delta V_C = (234 \text{ mA} * 286 \text{ ns})/10 \mu\text{F} = 6.68 \text{ mV}$$

$$V_{ESRRIPPLE} = 234 \text{ mA} * 10 \text{ m}\Omega = 2.34 \text{ mV}$$

$$\Delta V_{OUT} = 6.68 \text{ mV} + 2.34 \text{ mV} = 9.02 \text{ mV}$$

Since the output voltage is compared to the 0.8V internal reference voltage, a resistor divider needs to be designed. Selecting $R_{BOT} = 200 \text{ k}\Omega$, the top resistor (R_{TOP}) is:

$$R_{TOP} = 200 \text{ k}\Omega * (1.8/0.8 - 1) = 250 \text{ k}\Omega$$

The input capacitor (C_{IN}) is selected to be $10 \mu\text{F}$. This provides adequate filtering on the input.

Figure 2 through Figure 5 show lab performance of the buck converter built with the components selected above and compensation values for R_C and C_C of $22 \text{ k}\Omega$ and 1000 pF , respectively. Unless otherwise noted, $V_{IN} = 3.3V$, $V_{OUT} = 1.8V$ and $I_{OUT} = 500 \text{ mA}$.

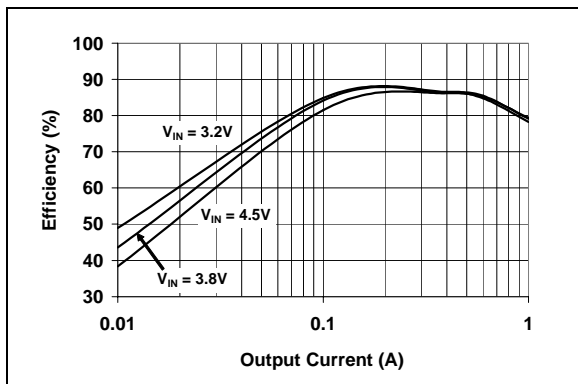


FIGURE 2: Converter Efficiency.

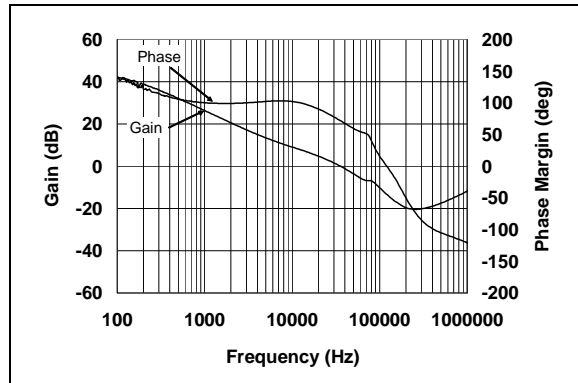


FIGURE 3: System Bode Plot.

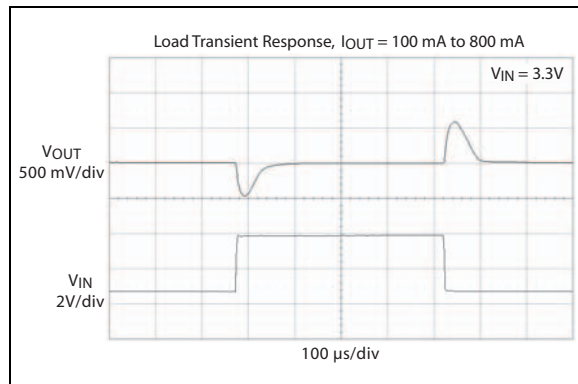


FIGURE 4: Load Transient Response.

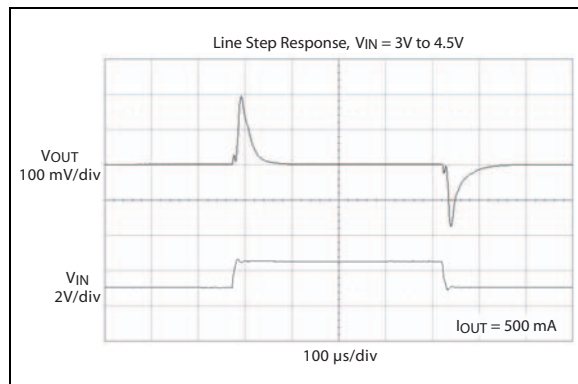


FIGURE 5: Line Step Response.

CONCLUSION

Designing with the MCP1612 is very simple and straightforward. The buck inductor, output filter capacitor and resistor divider network are the only components that need to be calculated.

The integrated switching and synchronous MOSFETs, as well as the 1.4 MHz switching speed, make the MCP1612 buck controller an ideal solution for a space-contained design. The output voltage is set by a simple resistor divider and a series resistor capacitor is all that is required for a high-bandwidth control loop.

Note the following details of the code protection feature on Microchip devices:

- Microchip products meet the specification contained in their particular Microchip Data Sheet.
- Microchip believes that its family of products is one of the most secure families of its kind on the market today, when used in the intended manner and under normal conditions.
- There are dishonest and possibly illegal methods used to breach the code protection feature. All of these methods, to our knowledge, require using the Microchip products in a manner outside the operating specifications contained in Microchip's Data Sheets. Most likely, the person doing so is engaged in theft of intellectual property.
- Microchip is willing to work with the customer who is concerned about the integrity of their code.
- Neither Microchip nor any other semiconductor manufacturer can guarantee the security of their code. Code protection does not mean that we are guaranteeing the product as "unbreakable."

Code protection is constantly evolving. We at Microchip are committed to continuously improving the code protection features of our products. Attempts to break Microchip's code protection feature may be a violation of the Digital Millennium Copyright Act. If such acts allow unauthorized access to your software or other copyrighted work, you may have a right to sue for relief under that Act.

Information contained in this publication regarding device applications and the like is provided only for your convenience and may be superseded by updates. It is your responsibility to ensure that your application meets with your specifications. MICROCHIP MAKES NO REPRESENTATIONS OR WARRANTIES OF ANY KIND WHETHER EXPRESS OR IMPLIED, WRITTEN OR ORAL, STATUTORY OR OTHERWISE, RELATED TO THE INFORMATION, INCLUDING BUT NOT LIMITED TO ITS CONDITION, QUALITY, PERFORMANCE, MERCHANTABILITY OR FITNESS FOR PURPOSE. Microchip disclaims all liability arising from this information and its use. Use of Microchip's products as critical components in life support systems is not authorized except with express written approval by Microchip. No licenses are conveyed, implicitly or otherwise, under any Microchip intellectual property rights.

Trademarks

The Microchip name and logo, the Microchip logo, Accuron, dsPIC, KEELOQ, microID, MPLAB, PIC, PICmicro, PICSTART, PRO MATE, PowerSmart, rfPIC, and SmartShunt are registered trademarks of Microchip Technology Incorporated in the U.S.A. and other countries.


AmpLab, FilterLab, Migratable Memory, MXDEV, MXLAB, PICMASTER, SEEVAL, SmartSensor and The Embedded Control Solutions Company are registered trademarks of Microchip Technology Incorporated in the U.S.A.

Analog-for-the-Digital Age, Application Maestro, dsPICDEM, dsPICDEM.net, dsPICworks, ECAN, ECONOMONITOR, FanSense, FlexROM, fuzzyLAB, In-Circuit Serial Programming, ICSP, ICEPIC, MPASM, MPLIB, MPLINK, MPSIM, PICkit, PICDEM, PICDEM.net, PICLAB, PICtail, PowerCal, PowerInfo, PowerMate, PowerTool, rFLAB, rfPICDEM, Select Mode, Smart Serial, SmartTel and Total Endurance are trademarks of Microchip Technology Incorporated in the U.S.A. and other countries.

SQTP is a service mark of Microchip Technology Incorporated in the U.S.A.

All other trademarks mentioned herein are property of their respective companies.

© 2005, Microchip Technology Incorporated, Printed in the U.S.A., All Rights Reserved.

 Printed on recycled paper.

QUALITY MANAGEMENT SYSTEM
CERTIFIED BY DNV
== ISO/TS 16949:2002 ==

Microchip received ISO/TS-16949:2002 quality system certification for its worldwide headquarters, design and wafer fabrication facilities in Chandler and Tempe, Arizona and Mountain View, California in October 2003. The Company's quality system processes and procedures are for its PICmicro® 8-bit MCUs, KEELOQ® code hopping devices, Serial EEPROMs, microperipherals, nonvolatile memory and analog products. In addition, Microchip's quality system for the design and manufacture of development systems is ISO 9001:2000 certified.



WORLDWIDE SALES AND SERVICE

AMERICAS

Corporate Office
2355 West Chandler Blvd.
Chandler, AZ 85224-6199
Tel: 480-792-7200
Fax: 480-792-7277
Technical Support:
<http://support.microchip.com>
Web Address:
www.microchip.com

Atlanta
Alpharetta, GA
Tel: 770-640-0034
Fax: 770-640-0307

Boston
Westford, MA
Tel: 978-692-3848
Fax: 978-692-3821

Chicago
Itasca, IL
Tel: 630-285-0071
Fax: 630-285-0075

Dallas
Addison, TX
Tel: 972-818-7423
Fax: 972-818-2924

Detroit
Farmington Hills, MI
Tel: 248-538-2250
Fax: 248-538-2260

Kokomo
Kokomo, IN
Tel: 765-864-8360
Fax: 765-864-8387

Los Angeles
Mission Viejo, CA
Tel: 949-462-9523
Fax: 949-462-9608

San Jose
Mountain View, CA
Tel: 650-215-1444
Fax: 650-961-0286

Toronto
Mississauga, Ontario,
Canada
Tel: 905-673-0699
Fax: 905-673-6509

ASIA/PACIFIC

Australia - Sydney
Tel: 61-2-9868-6733
Fax: 61-2-9868-6755

China - Beijing
Tel: 86-10-8528-2100
Fax: 86-10-8528-2104

China - Chengdu
Tel: 86-28-8676-6200
Fax: 86-28-8676-6599

China - Fuzhou
Tel: 86-591-8750-3506
Fax: 86-591-8750-3521

China - Hong Kong SAR
Tel: 852-2401-1200
Fax: 852-2401-3431

China - Shanghai
Tel: 86-21-5407-5533
Fax: 86-21-5407-5066

China - Shenyang
Tel: 86-24-2334-2829
Fax: 86-24-2334-2393

China - Shenzhen
Tel: 86-755-8203-2660
Fax: 86-755-8203-1760

China - Shunde
Tel: 86-757-2839-5507
Fax: 86-757-2839-5571

China - Qingdao
Tel: 86-532-502-7355
Fax: 86-532-502-7205

ASIA/PACIFIC

India - Bangalore
Tel: 91-80-2229-0061
Fax: 91-80-2229-0062

India - New Delhi
Tel: 91-11-5160-8631
Fax: 91-11-5160-8632

Japan - Kanagawa
Tel: 81-45-471- 6166
Fax: 81-45-471-6122

Korea - Seoul
Tel: 82-2-554-7200
Fax: 82-2-558-5932 or
82-2-558-5934

Singapore
Tel: 65-6334-8870
Fax: 65-6334-8850

Taiwan - Kaohsiung
Tel: 886-7-536-4818
Fax: 886-7-536-4803

Taiwan - Taipei
Tel: 886-2-2500-6610
Fax: 886-2-2508-0102

Taiwan - Hsinchu
Tel: 886-3-572-9526
Fax: 886-3-572-6459

EUROPE

Austria - Weis
Tel: 43-7242-2244-399
Fax: 43-7242-2244-393

Denmark - Ballerup
Tel: 45-4450-2828
Fax: 45-4485-2829

France - Massy
Tel: 33-1-69-53-63-20
Fax: 33-1-69-30-90-79

Germany - Ismaning
Tel: 49-89-627-144-0
Fax: 49-89-627-144-44

Italy - Milan
Tel: 39-0331-742611
Fax: 39-0331-466781

Netherlands - Drunen
Tel: 31-416-690399
Fax: 31-416-690340

England - Berkshire
Tel: 44-118-921-5869
Fax: 44-118-921-5820