

Contrast Control Circuits for the PIC16F91X

*Author: Joseph Julicher
Microchip Technology Inc.*

INTRODUCTION


The PIC16F91X is a low-cost flash-based PICmicro[®] microcontroller that has the ability to drive LCD glass. This device also has a wide operational voltage range and low power, making it an ideal candidate for many battery powered applications. To get the most use from the battery, the device must operate over a wide voltage range. The wide voltage range can cause contrast problems with the LCD glass, so a solution is needed that will maintain constant LCD voltage and be very cost effective. In this technical brief we will discuss three different contrast control systems; external voltage regulator, comparator buck regulator and comparator buck/boost regulator.

SYSTEM REQUIREMENTS

LCD glass requires a specific RMS voltage applied between a segment and a common to create the required polarization shift. Different pieces of glass are designed for different voltages with the most common type of glass being 5.0V glass. Lower voltage glass is available, though as the voltage gets below 3V, it is more difficult to create large panels with acceptable contrast.

The PIC16F91X has a series of analog switches to connect the segment and common pins to 4 voltages. Three of the voltages are applied to the VLCD<3:0> pins. The fourth voltage is internally connected to VSS. To operate the LCD module, correct voltages must be applied to these pins. The voltages applied depend upon the type of LCD drive and the type of glass.

FIGURE 1: VOLTAGE APPLICATION

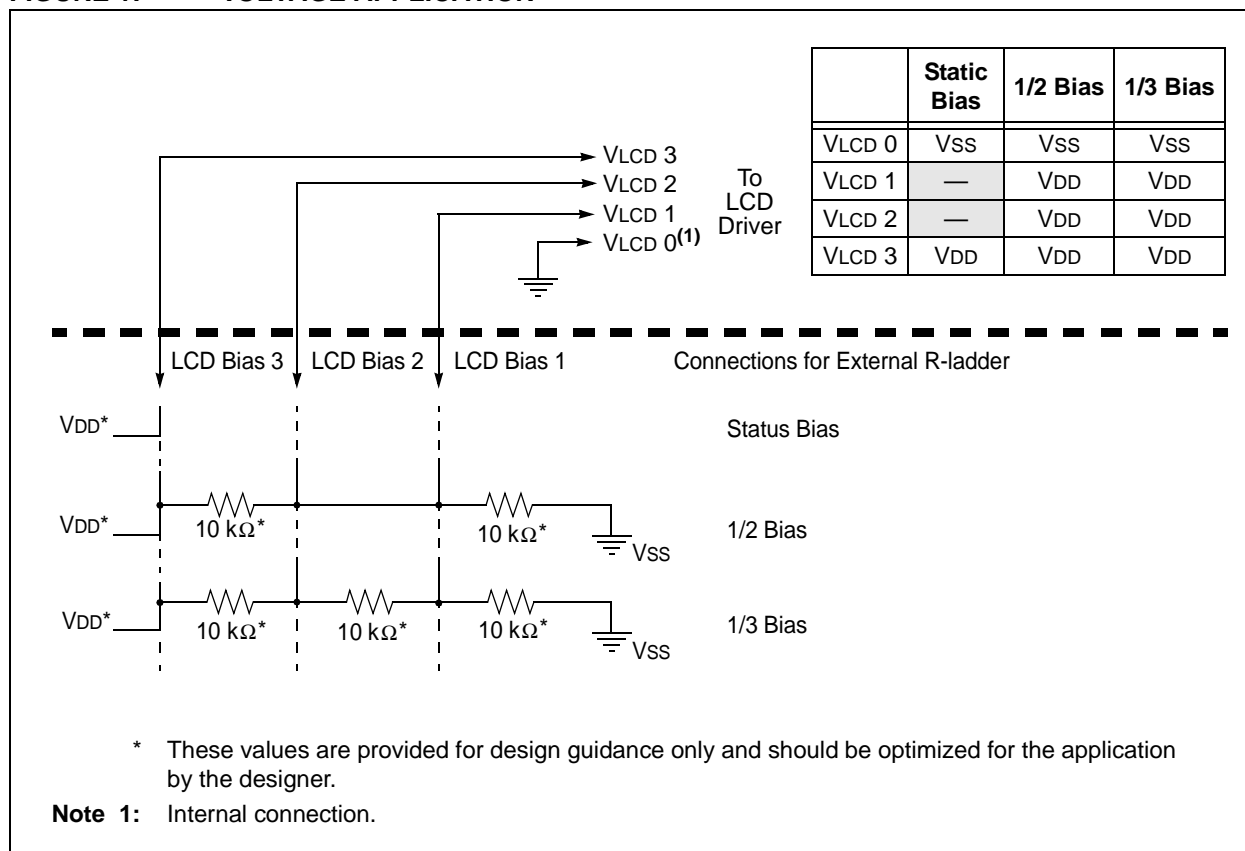


EXTERNAL VOLTAGE REGULATOR

A simple solution for contrast control is to use an external voltage regulator to generate the required glass voltage. If low voltage glass is used, the voltage regulator simply steps the power supply down to the required glass voltage.

Circuit Description

The basic format for the external regulator voltage generator is as shown in Figure 2. The regulator must be chosen to satisfy the requirements of glass voltage and power usage.

FIGURE 2: EXTERNAL VOLTAGE REGULATOR GENERATOR

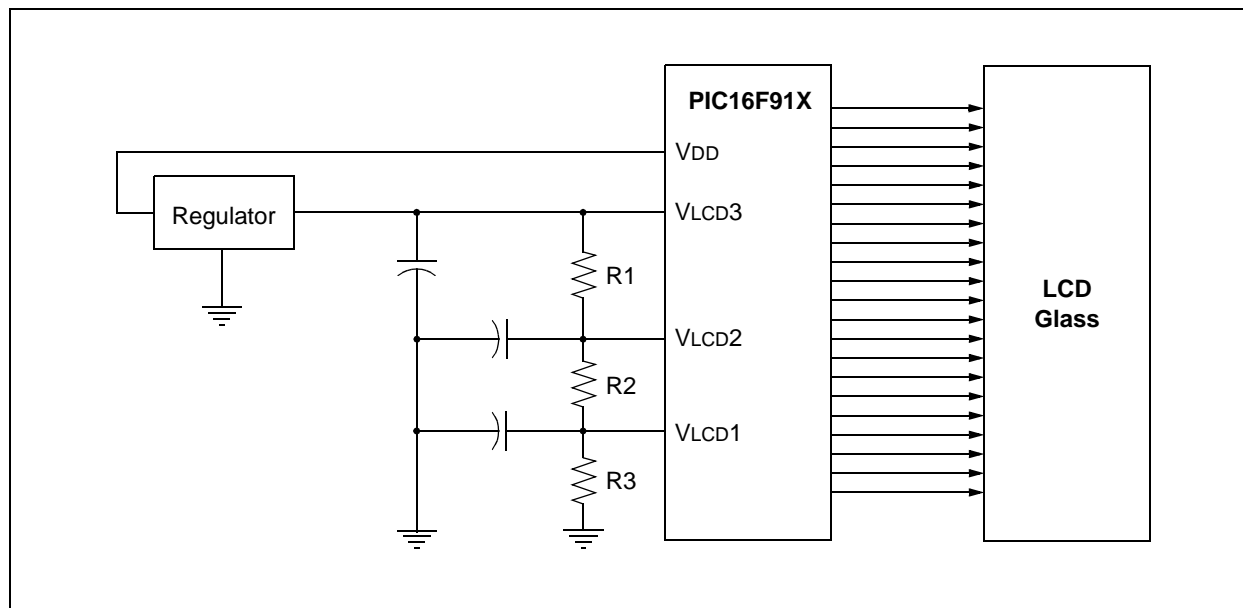

COMPARATOR BUCK REGULATOR

The external comparator solution is a simple one, but not without its issues. The first issue is that most battery applications are cost sensitive, so the addition of a regulator IC may not be practical. Another one is the regulator's dropout voltage. Linear regulators require a higher input voltage than their output. This difference may be very small, but it will limit the useful battery life of a product. The last issue is power consumption. The linear regulator will burn a small amount of current to provide its function. These problems can be solved with a PFM switched capacitor regulator, if it can use features already present in the microcontroller. Fortunately, the comparator in the PIC16F91X devices is designed to accommodate this function.

When Comparator mode 5 (CMCON<2:0> = 101) is used, it is possible to use an internal 0.6V band gap as the voltage reference. With this mode, creating a PFM buck regulator is simple.

Circuit Description

The circuit in Figure 4 uses the internal comparator to create a PFM buck power supply. The voltage between R4 and R5 is compared to the internal 0.6V reference. The comparator output is filtered by the capacitors and R6. R1-R3 divide the output voltage to an appropriate value for the VLCD inputs.

Software Description

No software is required for running this system, but the comparator must be initialized into the correct mode. The following code can be used to initialize this circuit.


EXAMPLE 1: INITIALIZATION CODE

```
banksel    CMCON0
    MOVLW  0x0D
    MOVWF  CMCON0    ;enter the contrast
                    ;control mode
```

FIGURE 3: COMPARATOR MODE 5 DETAIL


One Independent Comparator with Reference Option

CM<2:0> = 101

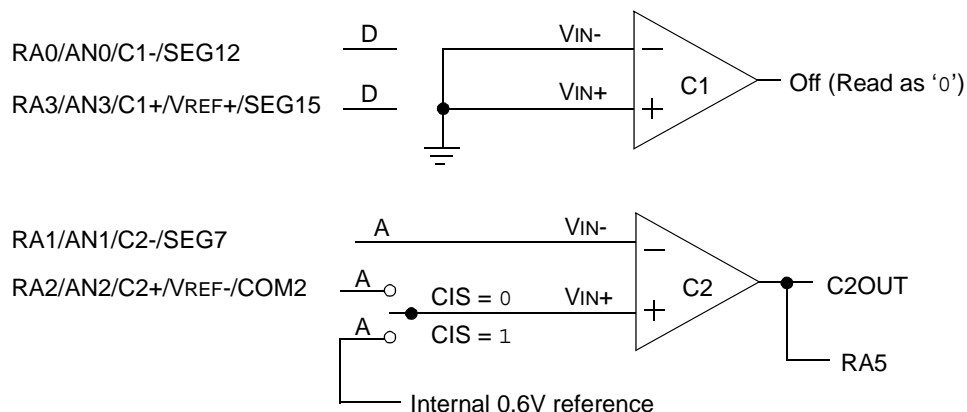

Legend: A = Analog Input, port reads zeros always CIS = Comparator Input Switch (CMCON0<3>)

D = Digital Input

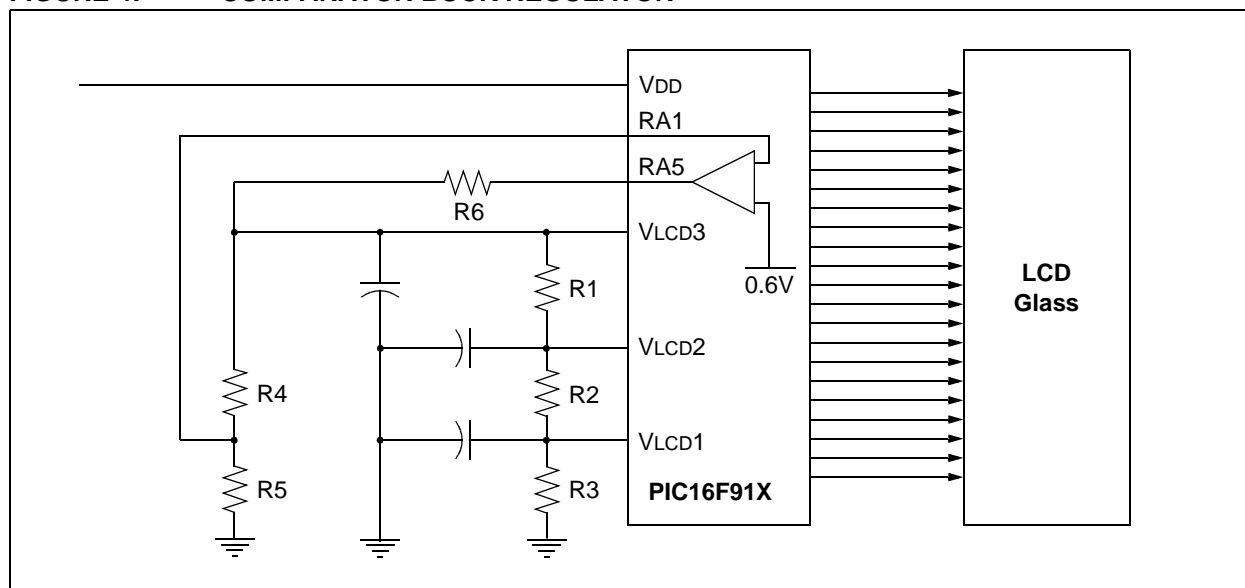FIGURE 4: COMPARATOR BUCK REGULATOR

COMPARATOR BUCK/BOOST REGULATOR


A comparator buck circuit is beneficial for many applications, but if the V_{DD} is too low for the glass, a boost converter may be a better option. Fortunately, it is possible to use the internal comparators to build a simple buck/boost.

There are many trade-offs with a boost circuit, but the primary issue is the voltage limits of the I/O pins. The data sheet specifies that the input range of the VLCD pins is V_{SS} to V_{DD} . Therefore, if the voltage to the LCD is to be boosted, then that boosted voltage must also be applied to V_{DD} . With an increase in V_{DD} comes an increase in current consumption so software must be used to control when the boosted voltage is to be used. Also, the device must be powered before the boost is active so the minimum battery voltage is still 2.0V.

Circuit Description

There are two basic methods to boost a voltage. Fortunately, it is easy to use the on-board comparators to regulate both methods of boosting voltage. The basic architecture of the circuit is shown in Figure 5. Comparator C1 is used to build an oscillator that drives the boost circuit. Comparator C2 is used to regulate the activity of C1 by shutting off the oscillator when the voltage exceeds the limit programmed by R6 and R7. R5 and D3 create a simple voltage reference for the entire system. C2 is a bulk capacitor that is maintained at the desired voltage level by the entire regulator. D1 allows the rise and fall time of the oscillator to be tuned independently by adjusting R2 and R4.

FIGURE 5: COMPARATOR BUCK/BOOST REGULATOR

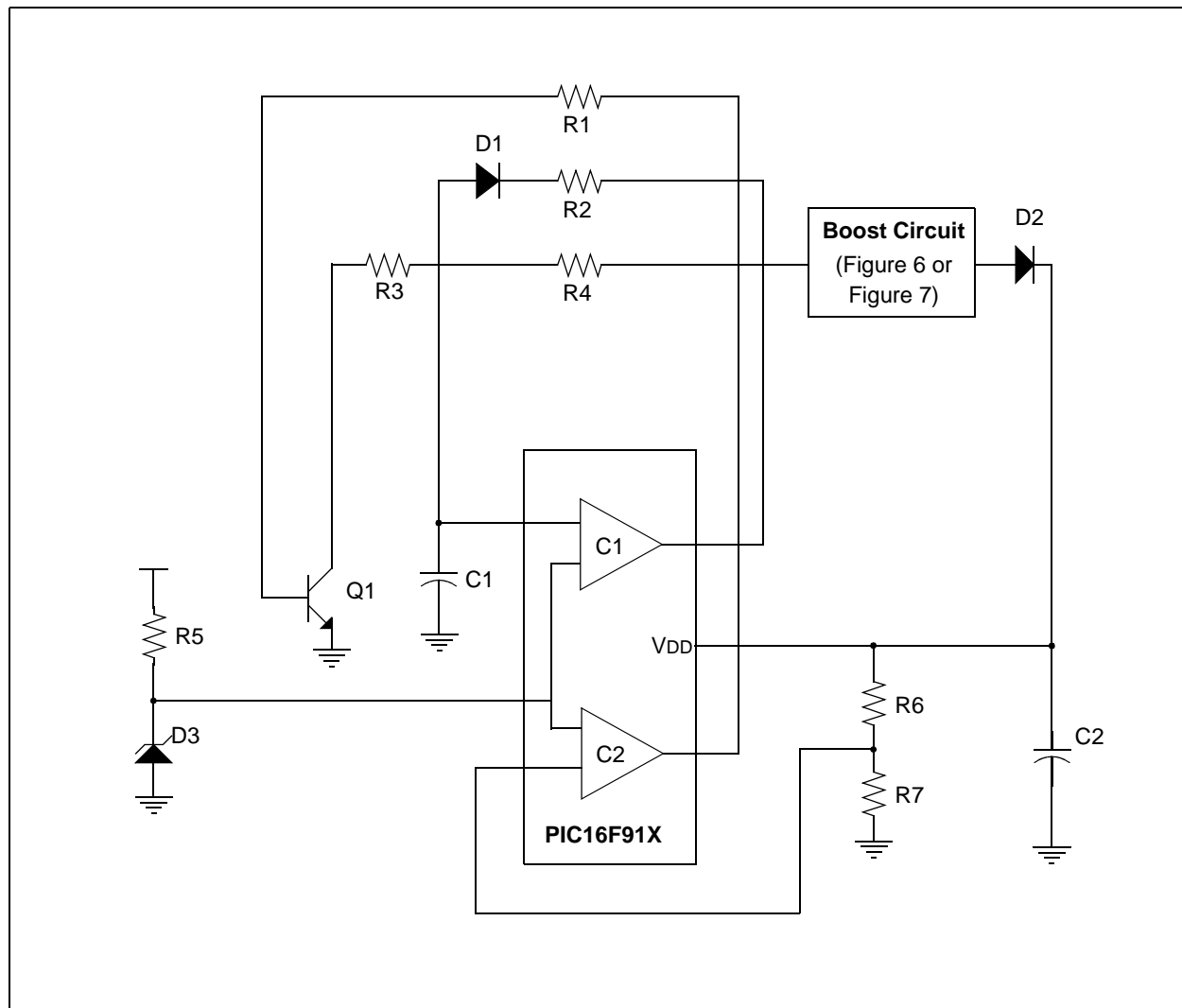

There are two boost circuits that can be easily inserted into the boost block as shown in Figure 5. The first circuit is a simple switched capacitor doubler.

The capacitor and diode work with the circuit as drawn in Figure 6 to produce a doubler. This circuit works best with a 50% duty cycle. Therefore, a few components can be removed from the first schematic. To meet the start-up requirement, the minimum V_{BAT} is 2 diode drops over 2.0V. Assuming schottky diodes, this circuit will convert 2.6V to any voltage from 2.6-5.2V. If a slightly lower minimum voltage is required, then an inductor-based switcher is required (Figure 7).

To adjust the amount of energy transferred to the output capacitor, the duty cycle of Q2 must be tuned. This is done by adjusting the values of R2 and R4 in the first schematic.

Software Description

There is no special software required for this application. Simply initialize the comparators by writing 0x06 to the CMCON0 register.

CONCLUSION

Managing the contrast of an LCD in an environment with a wide range of voltages can be challenging. The designs presented in this technical brief provide a good basis to start designing low-cost, low-voltage systems. The PIC16F91X device provides all the features necessary to ensure excellent low-power performance.

FIGURE 6: SIMPLE SWITCHED CAPACITOR DOUBLER


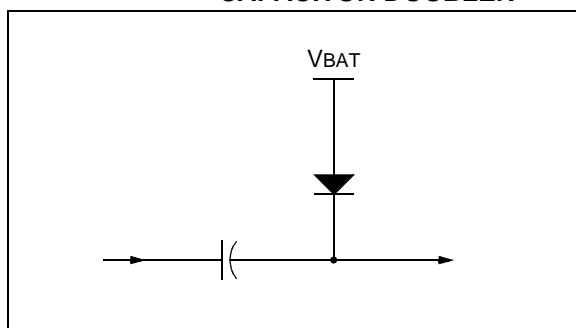


FIGURE 7: INDUCTOR BASED SWITCHER

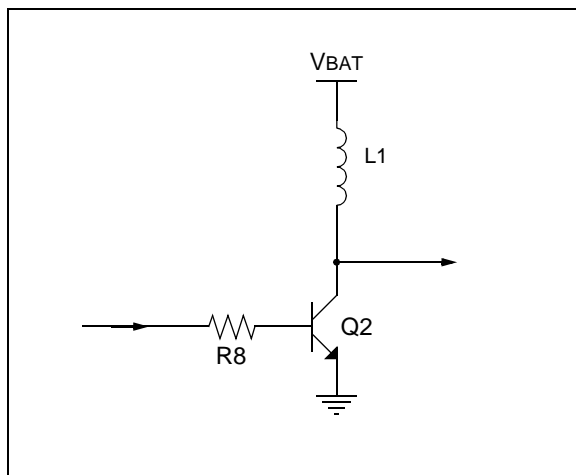

TB084

NOTES:

Note the following details of the code protection feature on Microchip devices:

- Microchip products meet the specification contained in their particular Microchip Data Sheet.
- Microchip believes that its family of products is one of the most secure families of its kind on the market today, when used in the intended manner and under normal conditions.
- There are dishonest and possibly illegal methods used to breach the code protection feature. All of these methods, to our knowledge, require using the Microchip products in a manner outside the operating specifications contained in Microchip's Data Sheets. Most likely, the person doing so is engaged in theft of intellectual property.
- Microchip is willing to work with the customer who is concerned about the integrity of their code.
- Neither Microchip nor any other semiconductor manufacturer can guarantee the security of their code. Code protection does not mean that we are guaranteeing the product as "unbreakable."

Code protection is constantly evolving. We at Microchip are committed to continuously improving the code protection features of our products. Attempts to break Microchip's code protection feature may be a violation of the Digital Millennium Copyright Act. If such acts allow unauthorized access to your software or other copyrighted work, you may have a right to sue for relief under that Act.

Information contained in this publication regarding device applications and the like is provided only for your convenience and may be superseded by updates. It is your responsibility to ensure that your application meets with your specifications. MICROCHIP MAKES NO REPRESENTATIONS OR WARRANTIES OF ANY KIND WHETHER EXPRESS OR IMPLIED, WRITTEN OR ORAL, STATUTORY OR OTHERWISE, RELATED TO THE INFORMATION, INCLUDING BUT NOT LIMITED TO ITS CONDITION, QUALITY, PERFORMANCE, MERCHANTABILITY OR FITNESS FOR PURPOSE. Microchip disclaims all liability arising from this information and its use. Use of Microchip's products as critical components in life support systems is not authorized except with express written approval by Microchip. No licenses are conveyed, implicitly or otherwise, under any Microchip intellectual property rights.

Trademarks

The Microchip name and logo, the Microchip logo, Accuron, dsPIC, KEELoQ, microID, MPLAB, PIC, PICmicro, PICSTART, PRO MATE, PowerSmart, rfPIC, and SmartShunt are registered trademarks of Microchip Technology Incorporated in the U.S.A. and other countries.


AmpLab, FilterLab, Migratable Memory, MXDEV, MXLAB, PICMASTER, SEEVAL, SmartSensor and The Embedded Control Solutions Company are registered trademarks of Microchip Technology Incorporated in the U.S.A.

Analog-for-the-Digital Age, Application Maestro, dsPICDEM, dsPICDEM.net, dsPICworks, ECAN, ECONOMONITOR, FanSense, FlexROM, fuzzyLAB, In-Circuit Serial Programming, ICSP, ICEPIC, MPASM, MPLIB, MPLINK, MPSIM, PICkit, PICDEM, PICDEM.net, PICLAB, PICtail, PowerCal, PowerInfo, PowerMate, PowerTool, rfLAB, rfPICDEM, Select Mode, Smart Serial, SmartTel and Total Endurance are trademarks of Microchip Technology Incorporated in the U.S.A. and other countries.

SQTP is a service mark of Microchip Technology Incorporated in the U.S.A.

All other trademarks mentioned herein are property of their respective companies.

© 2004, Microchip Technology Incorporated, Printed in the U.S.A., All Rights Reserved.

 Printed on recycled paper.

QUALITY MANAGEMENT SYSTEM
CERTIFIED BY DNV
== ISO/TS 16949:2002 ==

Microchip received ISO/TS-16949:2002 quality system certification for its worldwide headquarters, design and wafer fabrication facilities in Chandler and Tempe, Arizona and Mountain View, California in October 2003. The Company's quality system processes and procedures are for its PICmicro® 8-bit MCUs, KEELoQ® code hopping devices, Serial EEPROMs, microperipherals, nonvolatile memory and analog products. In addition, Microchip's quality system for the design and manufacture of development systems is ISO 9001:2000 certified.



WORLDWIDE SALES AND SERVICE

AMERICAS

Corporate Office
2355 West Chandler Blvd.
Chandler, AZ 85224-6199
Tel: 480-792-7200
Fax: 480-792-7277
Technical Support:
<http://support.microchip.com>
Web Address:
www.microchip.com

Atlanta

Alpharetta, GA
Tel: 770-640-0034
Fax: 770-640-0307

Boston

Westford, MA
Tel: 978-692-3848
Fax: 978-692-3821

Chicago

Itasca, IL
Tel: 630-285-0071
Fax: 630-285-0075

Dallas

Addison, TX
Tel: 972-818-7423
Fax: 972-818-2924

Detroit

Farmington Hills, MI
Tel: 248-538-2250
Fax: 248-538-2260

Kokomo

Kokomo, IN
Tel: 765-864-8360
Fax: 765-864-8387

Los Angeles

Mission Viejo, CA
Tel: 949-462-9523
Fax: 949-462-9608

San Jose

Mountain View, CA
Tel: 650-215-1444
Fax: 650-961-0286

Toronto

Mississauga, Ontario,
Canada
Tel: 905-673-0699
Fax: 905-673-6509

ASIA/PACIFIC

Australia - Sydney
Tel: 61-2-9868-6733
Fax: 61-2-9868-6755

China - Beijing
Tel: 86-10-8528-2100
Fax: 86-10-8528-2104

China - Chengdu
Tel: 86-28-8676-6200
Fax: 86-28-8676-6599

China - Fuzhou
Tel: 86-591-8750-3506
Fax: 86-591-8750-3521

China - Hong Kong SAR

Tel: 852-2401-1200
Fax: 852-2401-3431

China - Shanghai
Tel: 86-21-5407-5533
Fax: 86-21-5407-5066

China - Shenyang
Tel: 86-24-2334-2829
Fax: 86-24-2334-2393

China - Shenzhen
Tel: 86-755-8203-2660
Fax: 86-755-8203-1760

China - Shunde
Tel: 86-757-2839-5507
Fax: 86-757-2839-5571

China - Qingdao
Tel: 86-532-502-7355
Fax: 86-532-502-7205

ASIA/PACIFIC

India - Bangalore
Tel: 91-80-2229-0061
Fax: 91-80-2229-0062

India - New Delhi
Tel: 91-11-5160-8631
Fax: 91-11-5160-8632

Japan - Kanagawa
Tel: 81-45-471- 6166
Fax: 81-45-471-6122

Korea - Seoul
Tel: 82-2-554-7200
Fax: 82-2-558-5932 or
82-2-558-5934

Singapore
Tel: 65-6334-8870
Fax: 65-6334-8850

Taiwan - Kaohsiung
Tel: 886-7-536-4818
Fax: 886-7-536-4803

Taiwan - Taipei
Tel: 886-2-2500-6610
Fax: 886-2-2508-0102

Taiwan - Hsinchu
Tel: 886-3-572-9526
Fax: 886-3-572-6459

EUROPE

Austria - Weis
Tel: 43-7242-2244-399
Fax: 43-7242-2244-393

Denmark - Ballerup
Tel: 45-4450-2828
Fax: 45-4485-2829

France - Massy
Tel: 33-1-69-53-63-20
Fax: 33-1-69-30-90-79

Germany - Ismaning
Tel: 49-89-627-144-0
Fax: 49-89-627-144-44

Italy - Milan
Tel: 39-0331-742611
Fax: 39-0331-466781

Netherlands - Drunen
Tel: 31-416-690399
Fax: 31-416-690340

England - Berkshire
Tel: 44-118-921-5869
Fax: 44-118-921-5820