



# Discrete Logic Replacement

## Logic Switch with Clock Generator

Author: Marc Lemay  
Quebec, Canada  
email:  
[MLemay@CollegeShawinigan.qc.ca](mailto:MLemay@CollegeShawinigan.qc.ca)

### APPLICATION OPERATION

The first application of my Logic Switch is to help prototypes of digital circuit. There are two main functions:


#### 1 – Logic Level Generator

The momentary switch acts as a debounced switch. Each time you press the switch the outputs toggle. There are also two led indicators to show the state of the outputs Q and 'Q.

#### 2 – Clock Generator

To enter or exit this mode you need to press the switch at least 2 seconds. The first time you enter this mode the outputs oscillate at 1 Hz. Pressing again will change frequency to 10 Hz (LED L5 On). Pressing a second time for 100 Hz (LED L2 On) and a third time for 1 KHz (LED L1 On). Pressing the switch again will reset frequency to 1 Hz. Note that duty cycle is 50% for all frequencies.

### BLOCK DIAGRAM

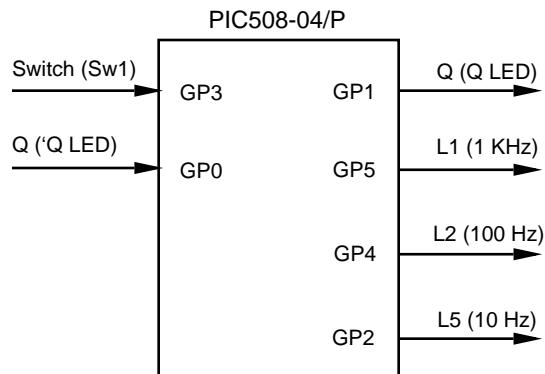

### MICROCHIP HARDWARE DEVELOPMENT TOOLS USED

Assemble/Complier version:

MPLab 3.22, MPasm 1.5

### BILL OF MATERIAL

Part	Description
C1	Ceramic Capacitor 0.1uF 50v
R1-R2 R4-R6	680 Ohms resistor 1/4 watt
R3	4.7 K Ohms resistor 1/4 watt
L1-L2-L5	Rectangular LED (2mm x 5mm)
L3-L4	Round LED T1 3/4
SW1	Momentary Switch E-Switch #520-03-1
U1	PIC12C508-04/P

Microchip Technology Incorporated, has been granted a nonexclusive, worldwide license to reproduce, publish and distribute all submitted materials, in either original or edited form. The author has affirmed that this work is an original, unpublished work and that he/she owns all rights to such work. All property rights, such as patents, copyrights and trademarks remain with author.

# Discrete Logic Replacement

---

## APPENDIX A: SOURCE CODE

```
;*****  
;  
;   Marc Lemay  
;   Electro Technician  
;   221 St-Isidore  
;   St-Etienne-des-Gres  
;   Quebec, Canada  
;   G0X 2P0  
;  
;   Tel: (819) 535-4117  
;  
;   Project: Logic Switch  
;   date   : august 23 1997  
;  
;*****  
  
list p=12c508, f=inhx8m ;uC number  
                                ;and inhx8m output format file  
  
decfreq    equ 0x07      ;low register use for frequency generation  
decfrequh  equ 0x0e      ;high register use for frequency generation  
freqscale  equ 0x08      ;low prescale value for frequency generation  
freqscaleh equ 0x0f      ;high prescale value for frequency generation  
                  ;1 = 1 KHz  
                  ;10 = 100 Hz  
                  ;100= 10 Hz  
                  ;1000= 1 Hz      3e8 hexa  
timeswp    equ 0x09      ;switch time pressed  
                                ;each unit = 16 msec  
swcourte   equ 0x0a      ;1 = switch pressed detected  
swprescale equ 0x0b      ;switch prescale 0 to 31 = 16 msec  
funct      equ 0x0c      ;0 = 0 logic output (stable)  
                                ;1 = 1 logic output (stable)  
                  ;2 = output = freq 1 Hz  
                  ;3 = output = freq 10 Hz  
                  ;4 = output = freq 100 Hz  
                  ;5 = output = freq 1 KHz  
  
functtmp   equ 0x0d      ;temp register  
  
gpio        equ 0x06      ;adrs io  
tmr0        equ 0x01;adrs timer  
status      equ 0x03      ;status register adrs  
osccal      equ 0x05;oscillator calibration register  
  
          org      0000  
;begin init  
  
begin  
    movwf    osccal           ;save oscillator calibration value  
    movlw    0x08      ;gp0 gp1 gp2 gp4 gp5 output gp3 input  
    tris     6  
    movlw    0xd1      ;prescale =1/4 for RC internal  
    option   ;  
    clrf    decfrequh;  
    clrf    decfreq ;  
    clrf    freqscaleh;0 = freq. stop  
    clrf    freqscale;0 = freq. stop  
    clrf    timeswp ;time switch pressed = 0  
    clrf    swcourte  
    clrf    funct    ;function = 0 = ouput = 0
```

# Discrete Logic Replacement

---

```
        movlw  0x1f      ;31 decimal
        movwf  swprescale;init prescale switch pressed to 31
        movlw  0x36          ;logic 0 on gpi0 and 1 on gpi1
                            ;gp2, gp4 et gp5 at 1 log ->led freq. off
        movwf  gpio
        movlw  0x05          ;init value for timer0
        movwf  tmr0
        ;end init

        ;begin master prog
princ  btfss tmr0,07    ;test bit 7 of tmr0
        goto   princ           ;wait until tmr0 = 128

        ;each 500 Usec the program will go here
        movlw  0x05          ;init value of tmr0 to 5 to give a good 500 usec
                            ;for time base
        movwf  tmr0
        movf   freqscale,0;mov freqscale in w
        btfss  status,2;check the z bit in status
        goto   freqact ;if freqscale <> 0 the freq. is running

        ;here the freq. is off and a logic 0 or 1 is steady to the output

suite   btfss  gpio,3          ;test switch pressed=1 log  open=0 log.
        goto   open             ;
        ;goto here if switch pressed ---> gp3 = 1 log.
        decfsz swprescale,1;var decrement from 31 to 0
        goto   princ           ;if <> 0 we return to princ

        ;here the switch is pressed since 16 msec
        movlw  0x1f          ;value 31 decimal
        movwf  swprescale;re-init swprescale to 31
        incf   timeswp         ;inc value time switch pressed
        btfsc  timeswp,2;test if timeswp = 4 (64 msec pressed ?)
        goto   rendu4          ;branch if timeswp = 4 (from 4 to 7 it's ok)

        ;here we check the 2 second switch pressed
        movlw  0x80          ;w <-- 128 for 2 sec.
        subwf  timeswp,0;compare w and timeswp
        btfss  status,2;skip if z bit = 1
        goto   princ           ;if z bit = 0 the switch not pressed for 2 second

        ;here the switch is pressed since 2 second
        movf   freqscale,1;move to affect the z flag
        btfss  status,2;skip if z flag is 1
        goto   tologic;if z is 0 then freqscale<>0 then freq is running

        ;here the logic mode is on... we stop it to make a freq. running
        bcf    gpio,5          ;led 1 KHz on
        movlw  0x05          ;5 = 1 KHz
        movwf  funct           ;funct = 5 = 1 KHz
        movlw  0xc8          ;c8 = 200 dec. prescale before output toggle
        movwf  freqscale
        movwf  decfreq
        clrf   freqscaleh
        clrf   decfreqh

scansw
        btfsc  gpio,3          ;test if switch open
        goto   scansw          ;scan while sw not open
        movlw  0x1f          ;31 decimal
        movwf  swprescale;re-init prescale
        clrf   timeswp         ;time switch pressed

        goto   princ           ;return to princ to scan tmr0
```

# Discrete Logic Replacement

---

```
tologic                                ;here the freq. will be stopped and
                                         ;a steady logic 0 will be at the output
    clrf      funct          ;function = 0
    clrf      freqscale;deactive the frequency
    clrf      freqscaleh;
    movlw     0x36          ;output gpi0 = 0      gpi1 (inverse)= 1
                                         ;and frequency led OFF
    goto     princ          ;return to master program to scan tmr0

rendu4                                ;branch here when the switch is pressed for 64 msec
    movlw     0x01          ;
    movwf     swcourte;init variable swcourte to 1 (the switch is good)
    goto     princ          ;return to master program to scan tmr0

;-----  
open                                ;jump here when the switch is not pressed
    movlw     0x1f          ;31 decimal
    movwf     swprescale;re-init prescale for switch
    clrf      timeswp       ;reset timeswp because switch is open
    movf      swcourte,1;check if swcourte=0
    btfsc    status,2;test le z flag si 0 logique
    goto     princ          ;branch if z flag equal 1 log.

                                         ;here swcourte = 1 log. then switch good
    clrf      swcourte;reset swcourte to 0
    movf      funct,0        ;move funct in w register
    movwf     functtmp;put a copy of funct in functtmp
    btfsc    status,2;check the z flag
    goto     funct1          ;if z = 1 then branch to funct1
    decf      functtmp,1
    btfsc    status,2;check z flag
    goto     funct0          ;if z = 1 then branch to funct0
    decf      functtmp,1
    btfsc    status,2;check z flag
    goto     funct3          ;if z = 1 then branch to funct3
    decf      functtmp,1
    btfsc    status,2;check z flag
    goto     funct4          ;if z = 1 then branch to funct4
    decf      functtmp,1
    btfsc    status,2;check z flag
    goto     funct5          ;if z = 1 then branch to funct5

                                         ;here the function is 5
                                         ;here the next funct will be 2 --> 1 Hz
    movlw     0x02          ;function = 2 now
    movwf     funct          ;3e8 = 1000 dec
    movlw     0xe8          ;freqscale
    movwf     decfreq
    movlw     0x03          ;decfreqh;
    movwf     freqscaleh
    bsf      gpi0,5          ;led 500-1000 Hz off. no led for 1 Hz rate
    goto     princ          ;return to main program to scan tmr0

funct1                                ;here the active function will be 1
    incf      funct,1        ;funct = 1
    movlw     0x35          ;output = 1 and leds off
    movwf     gpi0
    goto     princ          ;return to main program to scan tmr0

funct0                                ;here the active function will be 0
```

# Discrete Logic Replacement

---

```
        clrf      funct          ;funct = 0
        movlw    0x36          ;output q= 0
        movwf    gpio           ;
        goto    princ          ;return to main program to scan tmr0

funct3          ;here the active function will be 3   10 Hz
        incf      funct          ;incremente funct --> 3
        movlw    0x64          ;64 = 100 dec
        movwf    freqscale
        movwf    decfreq
        clrf      freqscaleh
        clrf      decfreqh;reset high byte
        bcf      gpio,2          ;led 10 Hz on
        goto    princ          ;return to main program to scan tmr0

funct4          ;here the active function will be 4   100Hz
        incf      funct          ;incremente funct --> 4
        movlw    0x0a          ;0a = 10 dec
        movwf    freqscale
        movwf    decfreq
        clrf      freqscaleh
        clrf      decfreqh;reset high byte
        bsf      gpio,2          ;led 10Hz off
        bcf      gpio,4          ;led 100 Hz on
        goto    princ          ;return to main program to scan tmr0

funct5          ;here the active function will be 5   1000 Hz
        incf      funct          ;incremente funct --> 5
        movlw    0x01          ;01 = 1 dec = 1 KHz
        movwf    freqscale
        movwf    decfreq
        clrf      freqscaleh
        clrf      decfreqh;reset high byte
        bsf      gpio,4          ;led 100 Hz off
        bcf      gpio,5          ;led 1000 Hz on
        goto    princ          ;return to main program to scan tmr0

;-----  

freqact          ;here frequency mode is active
        decf      decfreq,1;decremente decfreq
        btfss    status,2;test z flag
        goto    suite          ;branche if z <> 0

        movf      decfreqh,0;check high byte if = 0
        btfss    status,2;check z flag
        goto    decfreqhigh;branch if > 0

        ;here we toggle the output
        movf      gpio,0          ;load w with gpio : clock out
        xorlw    0x03          ;2 last bits to toggle
        movwf    gpio           ;
        movf      freqscale,0;freqscale --> w
        movwf    decfreq          ;re-init decfreq for next toggle
        movf      freqscaleh,0
        movwf    decfreqh;init byte high
        goto    suite

decfreqhigh
        decf      decfreqh,1;decremente byte high
        goto    suite

end
```

# **Discrete Logic Replacement**

---

---

**NOTES:**